

Chapter 2

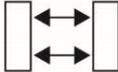
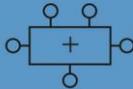
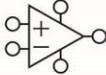
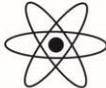
Professor Brendan Morris, SEB 3216, brendan.morris@unlv.edu
<http://www.ee.unlv.edu/~b1morris/cpe100/>

CPE100: Digital Logic Design I

Section 1004: Dr. Morris
Combinational Logic Design

Chapter 2 :: Topics


- Introduction
- Boolean Equations
- Boolean Algebra
- From Logic to Gates
- Multilevel Combinational Logic
- X's and Z's, Oh My
- Karnaugh Maps
- Combinational Building Blocks
- Timing

Application Software	
Operating Systems	
Architecture	
Micro-architecture	
Logic	
Digital Circuits	
Analog Circuits	
Devices	
Physics	

Introduction


A logic circuit is composed of:

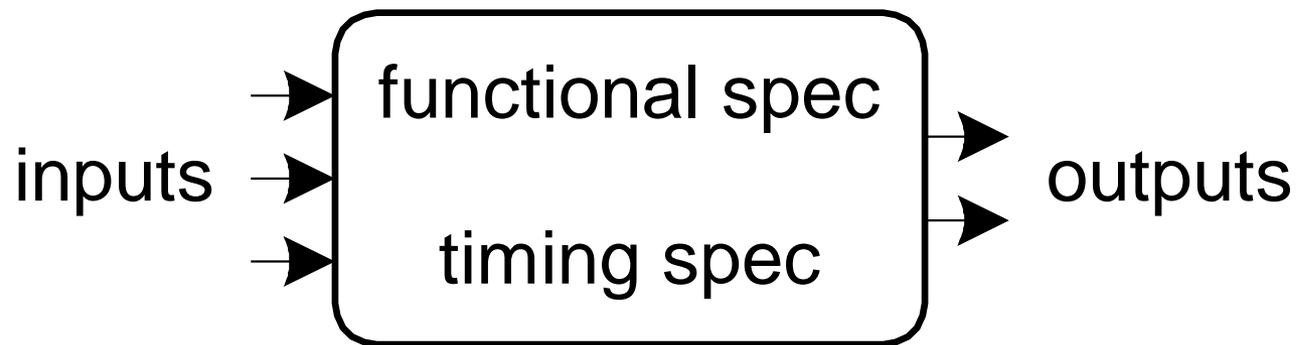- Inputs
- Outputs
- Functional specification
- Timing specification




Circuits

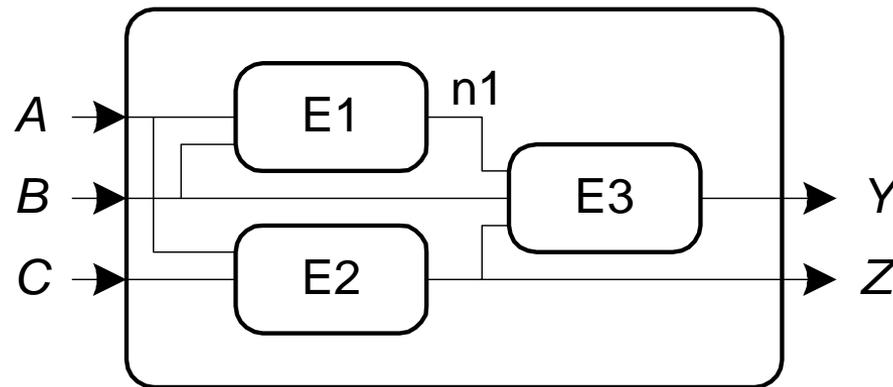- Nodes
 - Inputs: A, B, C
 - Outputs: Y, Z
 - Internal: $n1$
- Circuit elements
 - $E1, E2, E3$
 - Each a circuit



Types of Logic Circuits

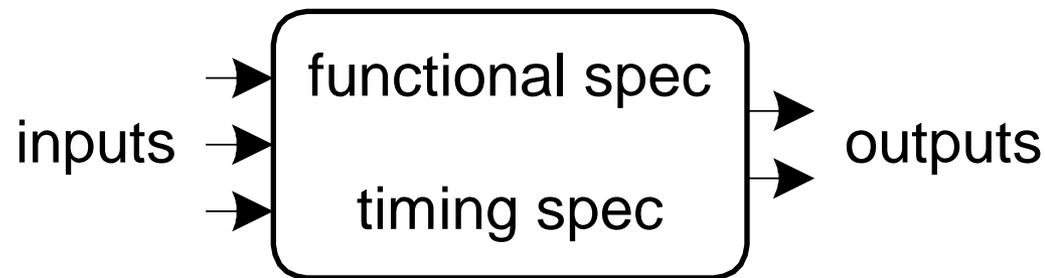
- Combinational Logic (Ch 2)
 - Memoryless
 - Outputs determined by current values of inputs
- Sequential Logic (Ch 3)
 - Has memory
 - Outputs determined by previous and current values of inputs



Rules of Combinational Composition

- Every element is combinational
- Every node is either an input or connects to *exactly one* output
- The circuit contains no cyclic paths
 - E.g. no connection from output to internal node


- Example:

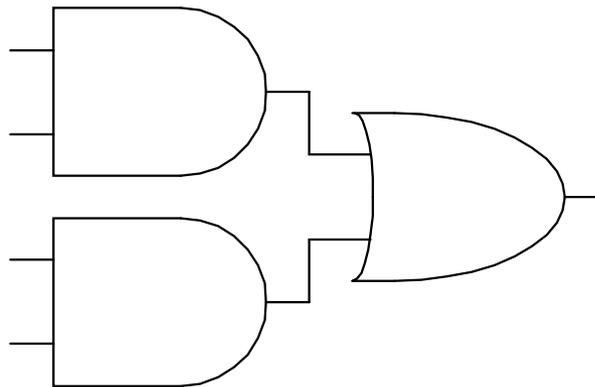

Boolean Equations

- Functional specification of outputs in terms of inputs

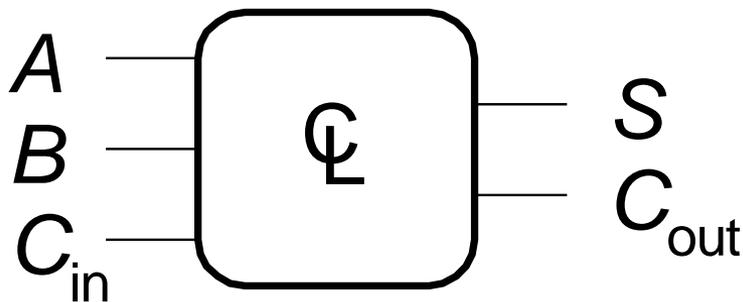- **Example:** $S = F(A, B, C_{in})$
 $C_{out} = F(A, B, C_{in})$



$$S = A \oplus B \oplus C_{in}$$

$$C_{out} = AB + AC_{in} + BC_{in}$$

A	B	C _{in}	S	C _{out}



Functional specification

Goals:

- Systematically express logical functions using Boolean equations
- To simplify Boolean equations

Some Definitions

- Complement: variable with a bar over it
 $\bar{A}, \bar{B}, \bar{C}$
- Literal: variable or its complement
 $A, \bar{A}, B, \bar{B}, C, \bar{C}$
- Implicant: product (AND) of literals
 ABC, AC, BC
- Minterm: product that includes all input variables
 $\bar{A}\bar{B}\bar{C}, \bar{A}\bar{B}C, \bar{A}B\bar{C}, \bar{A}BC, A\bar{B}\bar{C}, A\bar{B}C, AB\bar{C}, ABC$
- Maxterm: sum (OR) that includes all input variables
 $(A+B+C), (A+B+\bar{C}), (A+\bar{B}+C)$

Canonical Sum-of-Products (SOP) Form

- All equations can be written in SOP form
- Each row has a **minterm**
- A minterm is a product (AND) of literals
- Each minterm is TRUE for that row (and only that row)

A	B	Y	minterm	minterm name
0	0	0	$\overline{A} \overline{B}$	m_0
0	1	1	$\overline{A} B$	m_1
1	0	0	$A \overline{B}$	m_2
1	1	1	$A B$	m_3



Canonical Sum-of-Products (SOP) Form

- All equations can be written in SOP form
- Each row has a **minterm**
- A minterm is a product (AND) of literals
- Each minterm is TRUE for that row (and only that row)
- Form function by ORing minterms where the output is TRUE

A	B	Y	minterm	minterm name
0	0	0	$\bar{A} \bar{B}$	m_0
0	1	1	$\bar{A} B$	m_1
1	0	0	$A \bar{B}$	m_2
1	1	1	$A B$	m_3

$$Y = F(A, B) =$$

Canonical Sum-of-Products (SOP) Form

- All equations can be written in SOP form
- Each row has a **minterm**
- A minterm is a product (AND) of literals
- Each minterm is TRUE for that row (and only that row)
- Form function by ORing minterms where the output is TRUE
- Thus, a sum (OR) of products (AND terms)

A	B	Y	minterm	minterm name
0	0	0	$\bar{A} \bar{B}$	m_0
0	1	1	$\bar{A} B$	m_1
1	0	0	$A \bar{B}$	m_2
1	1	1	$A B$	m_3

$$Y = F(A, B) = \bar{A}B + AB = \Sigma(m_1, m_3)$$

SOP Example

- Steps:
- Find minterms that result in $Y=1$
- Sum “TRUE” minterms

A	B	Y
0	0	1
0	1	1
1	0	0
1	1	0

$$Y = F(A, B) =$$

Aside: Precedence

- AND has precedence over OR
- In other words:
 - AND is performed **before** OR
- Example:
 - $Y = \bar{A} \cdot B + A \cdot B$
 - Equivalent to:
 - $Y = (\bar{A}B) + (AB)$

Canonical Product-of-Sums (POS) Form

- All Boolean equations can be written in POS form
- Each row has a **maxterm**
- A maxterm is a sum (OR) of literals
- Each maxterm is FALSE for that row (and only that row)

A	B	Y	maxterm	maxterm name
0	0	0	$A + B$	M_0
0	1	1	$A + \overline{B}$	M_1
1	0	0	$\overline{A} + B$	M_2
1	1	1	$\overline{A} + \overline{B}$	M_3

Canonical Product-of-Sums (POS) Form

- All Boolean equations can be written in POS form
- Each row has a **maxterm**
- A maxterm is a sum (OR) of literals
- Each maxterm is FALSE for that row (and only that row)
- Form function by ANDing the maxterms for which the output is FALSE
- Thus, a product (AND) of sums (OR terms)

A	B	Y	maxterm	maxterm name
0	0	0	$A + B$	M_0
0	1	1	$A + \overline{B}$	M_1
1	0	0	$\overline{A} + B$	M_2
1	1	1	$\overline{A} + \overline{B}$	M_3

$$Y = M_0 \cdot M_2 = (A + B) \cdot (\overline{A} + B)$$

SOP and POS Comparison

- Sum of Products (SOP)
 - Implement the “ones” of the output
 - Sum all “one” terms \rightarrow OR results in “one”
- Product of Sums (POS)
 - Implement the “zeros” of the output
 - Multiply “zero” terms \rightarrow AND results in “zero”

Boolean Equations Example

- You are going to the cafeteria for lunch
 - You will eat lunch ($E=1$)
 - If it's open ($O=1$) **and**
 - If they're not serving corndogs ($C=0$)
- Write a truth table for determining if you will eat lunch (E).

O	C	E
0	0	
0	1	
1	0	
1	1	

Boolean Equations Example

- You are going to the cafeteria for lunch
 - You will eat lunch ($E=1$)
 - If it's open ($O=1$) **and**
 - If they're not serving corndogs ($C=0$)
- Write a truth table for determining if you will eat lunch (E).

O	C	E
0	0	0
0	1	0
1	0	1
1	1	0

SOP & POS Form

- SOP – sum-of-products

O	C	E	minterm	
0	0		\overline{O}	\overline{C}
0	1		\overline{O}	C
1	0		O	\overline{C}
1	1		O	C

- POS – product-of-sums

O	C	E	maxterm		
0	0		O	+	C
0	1		O	+	\overline{C}
1	0		\overline{O}	+	C
1	1		\overline{O}	+	\overline{C}

SOP & POS Form

- SOP – sum-of-products

O	C	E	minterm
0	0	0	$\overline{O} \overline{C}$
0	1	0	$\overline{O} C$
1	0	1	$O \overline{C}$
1	1	0	$O C$

$$E = O\overline{C}$$

$$= \Sigma(m_2)$$

- POS – product-of-sums

O	C	E	maxterm
0	0	0	$O + C$
0	1	0	$O + \overline{C}$
1	0	1	$\overline{O} + C$
1	1	0	$\overline{O} + \overline{C}$

$$E = (O + C)(O + \overline{C})(\overline{O} + \overline{C})$$

$$= \Pi(M_0, M_1, M_3)$$

SOP & POS Form

- SOP – sum-of-products

O	C	E	minterm
0	0	0	$\overline{O} \overline{C}$
0	1	0	$\overline{O} C$
1	0	1	$O \overline{C}$
1	1	0	$O C$

$$E = O\overline{C}$$

$$= \Sigma(m_2)$$

- POS – product-of-sums

O	C	E	maxterm
0	0	0	$O + C$
0	1	0	$O + \overline{C}$
1	0	1	$\overline{O} + C$
1	1	0	$\overline{O} + \overline{C}$

SOP & POS Form

- SOP – sum-of-products

<i>O</i>	<i>C</i>	<i>E</i>	minterm
0	0	0	$\overline{O} \overline{C}$
0	1	0	$\overline{O} C$
1	0	1	$O \overline{C}$
1	1	0	$O C$

$$\begin{aligned} E &= O\overline{C} \\ &= \Sigma(m_2) \end{aligned}$$

- POS – product-of-sums

<i>O</i>	<i>C</i>	<i>E</i>	maxterm
0	0	0	$O + C$
0	1	0	$O + \overline{C}$
1	0	1	$\overline{O} + C$
1	1	0	$\overline{O} + \overline{C}$

$$\begin{aligned} E &= (O + C)(O + \overline{C})(\overline{O} + \overline{C}) \\ &= \Pi(M_0, M_1, M_3) \end{aligned}$$

Boolean Algebra

- Axioms and theorems to **simplify** Boolean equations
- Like regular algebra, but simpler: variables have only two values (1 or 0)
- **Duality** in axioms and theorems:
 - ANDs and ORs, 0's and 1's interchanged

Boolean Axioms

Axiom

$$A1 \quad B = 0 \text{ if } B \neq 1$$

$$A2 \quad \bar{0} = 1$$

$$A3 \quad 0 \bullet 0 = 0$$

$$A4 \quad 1 \bullet 1 = 1$$

$$A5 \quad 0 \bullet 1 = 1 \bullet 0 = 0$$

Duality

Duality in Boolean axioms and theorems:

- ANDs and ORs, 0's and 1's interchanged

Boolean Axioms

Axiom	
A1	$B = 0$ if $B \neq 1$
A2	$\bar{0} = 1$
A3	$0 \bullet 0 = 0$
A4	$1 \bullet 1 = 1$
A5	$0 \bullet 1 = 1 \bullet 0 = 0$

Boolean Axioms

	Axiom		Dual
A1	$B = 0$ if $B \neq 1$	A1'	$B = 1$ if $B \neq 0$
A2	$\overline{0} = 1$	A2'	$\overline{1} = 0$
A3	$0 \bullet 0 = 0$	A3'	$1 + 1 = 1$
A4	$1 \bullet 1 = 1$	A4'	$0 + 0 = 0$
A5	$0 \bullet 1 = 1 \bullet 0 = 0$	A5'	$1 + 0 = 0 + 1 = 1$

Dual: Exchange: \bullet and $+$
 0 and 1

Boolean Axioms

	Axiom		Dual	Name
A1	$B = 0$ if $B \neq 1$	A1'	$B = 1$ if $B \neq 0$	Binary field
A2	$\bar{0} = 1$	A2'	$\bar{1} = 0$	NOT
A3	$0 \bullet 0 = 0$	A3'	$1 + 1 = 1$	AND/OR
A4	$1 \bullet 1 = 1$	A4'	$0 + 0 = 0$	AND/OR
A5	$0 \bullet 1 = 1 \bullet 0 = 0$	A5'	$1 + 0 = 0 + 1 = 1$	AND/OR

Dual: Exchange: \bullet and $+$
 0 and 1

Basic Boolean Theorems

Theorem	
T1	$B \bullet 1 = B$
T2	$B \bullet 0 = 0$
T3	$B \bullet B = B$
T4	$\overline{\overline{B}} = B$
T5	$B \bullet \overline{B} = 0$

Basic Boolean Theorems: Duals

	Theorem		Dual	Name
T1	$B \bullet 1 = B$	T1'	$B + 0 = B$	Identity
T2	$B \bullet 0 = 0$	T2'	$B + 1 = 1$	Null Element
T3	$B \bullet B = B$	T3'	$B + B = B$	Idempotency
T4		$\overline{\overline{B}} = B$		Involution
T5	$B \bullet \overline{B} = 0$	T5'	$B + \overline{B} = 1$	Complements

Dual: Exchange: \bullet and $+$
0 and 1