

Reminder

Midterm 1: Thursday, Oct. 5th

- In class: 1 hour and 15 minutes
- Chap 1 – 2.6
- Closed book, closed notes
- No calculator
- Boolean Theorems & Axioms document will be attached as last page of the exam for your convenience

Multiplying Out: SOP Form

An expression is in simplified **sum-of-products (SOP)** form when all products contain literals only.

- SOP form: $Y = AB + BC' + DE$
- **NOT** SOP form: $Y = DF + E(A' + B)$
- SOP form: $Z = A + BC + DE'F$

Multiplying Out: SOP Form

Example:

$$Y = (A + C + D + E)(A + B)$$

Apply T8' first when possible: $W + XZ = (W + X)(W + Z)$



Multiplying Out: SOP Form

Example:

$$Y = (A + C + D + E)(A + B)$$

Apply T8' first when possible: $W+XZ = (W+X)(W+Z)$

Make: $X = (C+D+E)$, $Z = B$ and rewrite equation

$$Y = (A+X)(A+Z)$$

substitution ($X=(C+D+E)$, $Z=B$)

$$= A + XZ$$

T8': Distributivity

$$= A + (C+D+E)B$$

substitution

$$= A + BC + BD + BE$$

T8: Distributivity

or

$$Y = AA+AB+AC+BC+AD+BD+AE+BE$$

T8: Distributivity

$$= A+AB+AC+AD+AE+BC+BD+BE$$

T3: Idempotency

$$= A + BC + BD + BE$$

T9': Covering

Canonical SOP & POS Form

- SOP – sum-of-products

O	C	E	minterm
0	0	0	$\overline{O} \overline{C}$
0	1	0	$\overline{O} C$
1	0	1	$O \overline{C}$
1	1	0	$O C$

$$E = O\overline{C}$$

$$= \Sigma(m_2)$$

- POS – product-of-sums

O	C	E	maxterm
0	0	0	$O + C$
0	1	0	$O + \overline{C}$
1	0	1	$\overline{O} + C$
1	1	0	$\overline{O} + \overline{C}$

$$E = (O + C)(O + \overline{C})(\overline{O} + \overline{C})$$

$$= \Pi(M_0, M_1, M_3)$$

Factoring: POS Form

An expression is in simplified **product-of-sums (POS)** form when all sums contain literals only.

- POS form: $Y = (A+B)(C+D)(E'+F)$
- **NOT** POS form: $Y = (D+E)(F'+GH)$
- POS form: $Z = A(B+C)(D+E')$

Factoring: POS Form

Example 1:

$$Y = (A + B' CDE)$$

Apply T8' first when possible: $W + XZ = (W + X)(W + Z)$

Factoring: POS Form

Example 1:

$$Y = (A + B'CDE)$$

Apply T8' first when possible: $W+XZ = (W+X)(W+Z)$

Make: $X = B'C$, $Z = DE$ and rewrite equation

$$Y = (A+XZ)$$

substitution ($X=B'C$, $Z=DE$)

$$= (A+B'C)(A+DE)$$

T8': Distributivity

$$= (A+B')(A+C)(A+D)(A+E)$$

T8': Distributivity

Factoring: POS Form

Example 2:

$$Y = AB + C'DE + F$$

Apply T8' first when possible: $W+XZ = (W+X)(W+Z)$

Factoring: POS Form

Example 2:

$$Y = AB + C'DE + F$$

Apply T8' first when possible: $W+XZ = (W+X)(W+Z)$

Make: $W = AB$, $X = C'$, $Z = DE$ and rewrite equation

$$\begin{aligned} Y &= (W+XZ) + F && \text{substitution } W = AB, X = C', Z = DE \\ &= (W+X)(W+Z) + F && \text{T8': Distributivity} \\ &= (AB+C')(AB+DE)+F && \text{substitution} \\ &= (A+C')(B+C')(AB+D)(AB+E)+F && \text{T8': Distributivity} \\ &= (A+C')(B+C')(A+D)(B+D)(A+E)(B+E)+F && \text{T8': Distributivity} \\ &= (A+C'+F)(B+C'+F)(A+D+F)(B+D+F)(A+E+F)(B+E+F) && \text{T8': Distributivity} \end{aligned}$$

Boolean Thms of Several Vars: Duals

#	Theorem	Dual	Name
T6	$B \bullet C = C \bullet B$	$B + C = C + B$	Commutativity
T7	$(B \bullet C) \bullet D = B \bullet (C \bullet D)$	$(B + C) + D = B + (C + D)$	Associativity
T8	$B \bullet (C + D) = (B \bullet C) + (B \bullet D)$	$B + (C \bullet D) = (B + C) (B + D)$	Distributivity
T9	$B \bullet (B + C) = B$	$B + (B \bullet C) = B$	Covering
T10	$(B \bullet C) + (B \bullet \bar{C}) = B$	$(B + C) \bullet (B + \bar{C}) = B$	Combining
T11	$(B \bullet C) + (B \bullet \bar{D}) + (C \bullet D) = (B \bullet C) + (B \bullet \bar{D})$	$(B + C) \bullet (B + \bar{D}) \bullet (C + D) = (B + C) \bullet (B + \bar{D})$	Consensus

Axioms and theorems are useful for *simplifying* equations.

Simplification methods

- **Distributivity (T8, T8')**

$$B(C+D) = BC + BD$$

$$B + CD = (B + C)(B + D)$$

- **Covering (T9')**

$$A + AP = A$$

- **Combining (T10)**

$$PA + \overline{PA} = P$$

- **Expansion**

$$P = PA + \overline{PA}$$

$$A = A + AP$$

- **Duplication**

$$A = A + A$$

- **A combination of Combining/Covering**

$$PA + \overline{A} = P + \overline{A}$$

DeMorgan's Theorem

Number	Theorem	Name
T12	$\overline{B_0 \bullet B_1 \bullet B_2 \dots} = \overline{B_0} + \overline{B_1} + \overline{B_2} \dots$	DeMorgan's Theorem

DeMorgan's Theorem

Number	Theorem	Name
T12	$\overline{B_0 \bullet B_1 \bullet B_2 \dots} = \overline{B_0} + \overline{B_1} + \overline{B_2} \dots$	DeMorgan's Theorem

The **complement of the product**
is the
sum of the complements

DeMorgan's Theorem: Dual

#	Theorem	Dual	Name
T12	$\overline{B_0 \bullet B_1 \bullet B_2 \dots} = \overline{B_0} + \overline{B_1} + \overline{B_2} \dots$	$\overline{B_0 + B_1 + B_2 \dots} = \overline{B_0} \bullet \overline{B_1} \bullet \overline{B_2} \dots$	DeMorgan's Theorem

DeMorgan's Theorem: Dual

#	Theorem	Dual	Name
T12	$\overline{B_0 \bullet B_1 \bullet B_2 \dots} = \overline{B_0} + \overline{B_1} + \overline{B_2} \dots$	$\overline{B_0 + B_1 + B_2 \dots} = \overline{B_0} \bullet \overline{B_1} \bullet \overline{B_2} \dots$	DeMorgan's Theorem

The complement of the product
is the
sum of the complements

DeMorgan's Theorem: Dual



#	Theorem	Dual	Name
T12	$\overline{B_0 \bullet B_1 \bullet B_2 \dots} = \overline{B_0 + B_1 + B_2 \dots}$	$\overline{B_0 + B_1 + B_2 \dots} = \overline{B_0 \bullet B_1 \bullet B_2 \dots}$	DeMorgan's Theorem

The complement of the product
is the
sum of the complements.



Dual: The complement of the sum
is the
product of the complements.

DeMorgan's Theorem

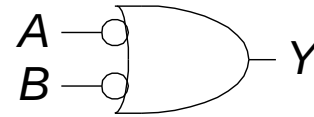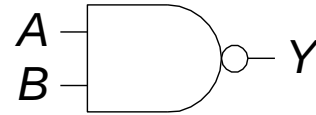- $Y = \overline{AB} = \overline{A} + \overline{B}$



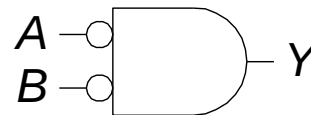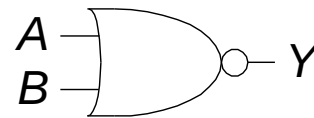- $Y = \overline{A + B} = \overline{A} \cdot \overline{B}$



DeMorgan's Theorem Example 1

$$Y = \overline{(A+BD)C}$$

DeMorgan's Theorem Example 1

$$\begin{aligned} Y &= \overline{(\overline{A+BD})\overline{C}} \\ &= \overline{(\overline{A+BD})} + \overline{\overline{C}} \\ &= (\overline{A} \bullet \overline{(\overline{BD})}) + C \\ &= (\overline{A} \bullet (BD)) + C \\ &= \overline{A}BD + C \end{aligned}$$

DeMorgan's Theorem Example 2

$$Y = \overline{(\overline{ACE} + \overline{D})} + B$$



DeMorgan's Theorem Example 2

$$\begin{aligned} Y &= \overline{(\overline{ACE + D})} + B \\ &= \overline{(\overline{ACE + D})} \bullet \overline{B} \\ &= \overline{(\overline{ACE} \bullet \overline{D})} \bullet \overline{B} \\ &= ((\overline{AC} + \overline{E}) \bullet D) \bullet \overline{B} \\ &= ((AC + \overline{E}) \bullet D) \bullet \overline{B} \\ &= (ACD + D\overline{E}) \bullet \overline{B} \\ &= \overline{A}\overline{B}CD + \overline{B}D\overline{E} \end{aligned}$$

Bubble Pushing



- **Backward:**

- Body changes
- Adds bubbles to inputs

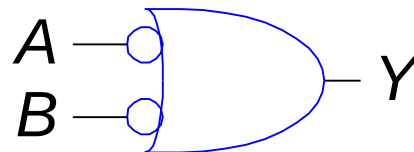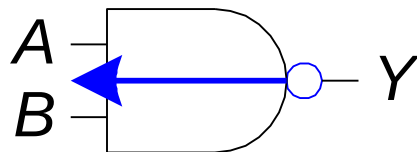


- **Forward:**

- Body changes
- Adds bubble to output

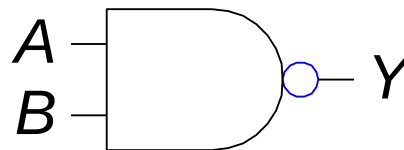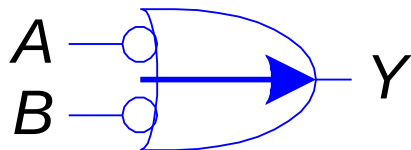


Bubble Pushing

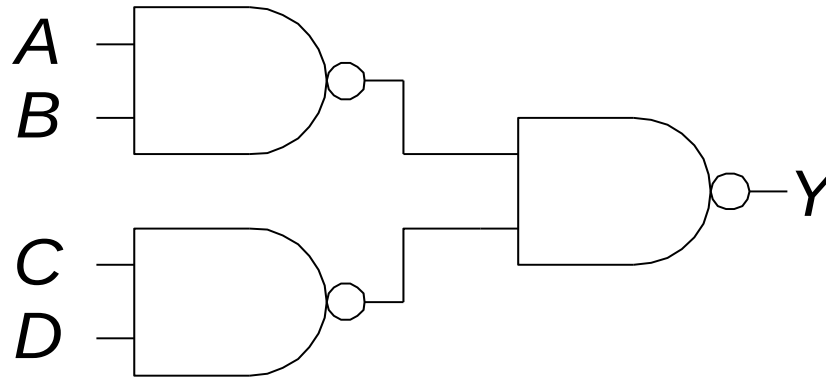- What is the Boolean expression for this circuit?



Bubble Pushing

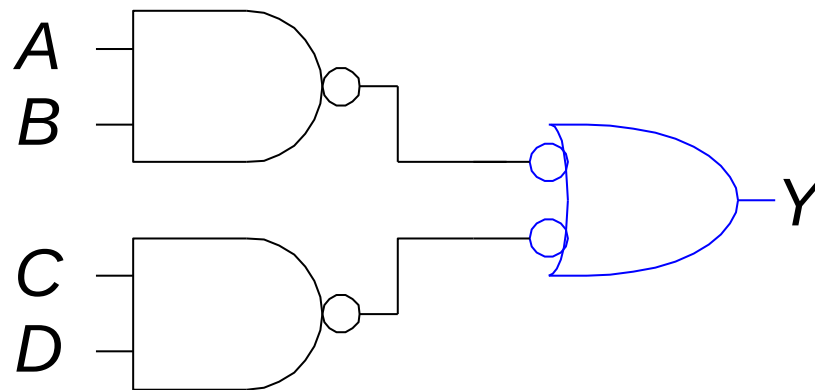
- What is the Boolean expression for this circuit?




$$Y = AB + CD$$

Bubble Pushing Rules

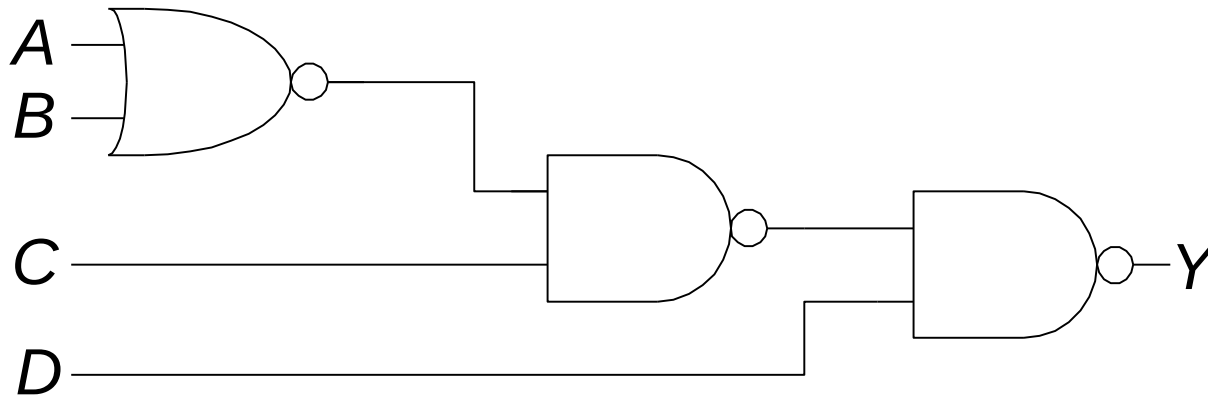
- Begin at output, then work toward inputs
- Push bubbles on final output back
- Draw gates in a form so bubbles cancel





Bubble Pushing Example

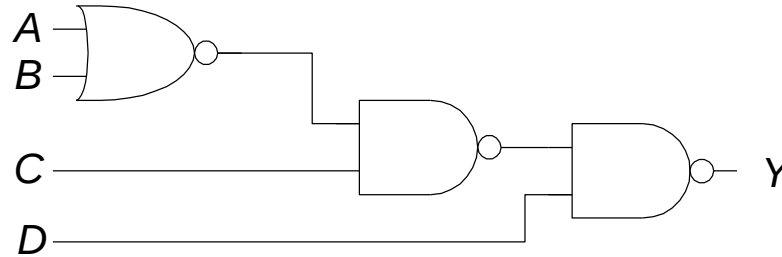




Bubble Pushing Example

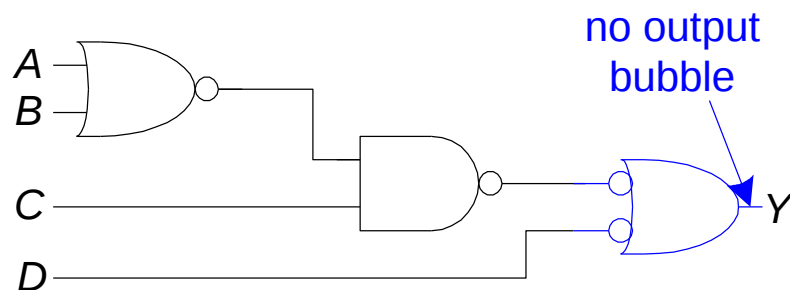

Bubble Pushing Example

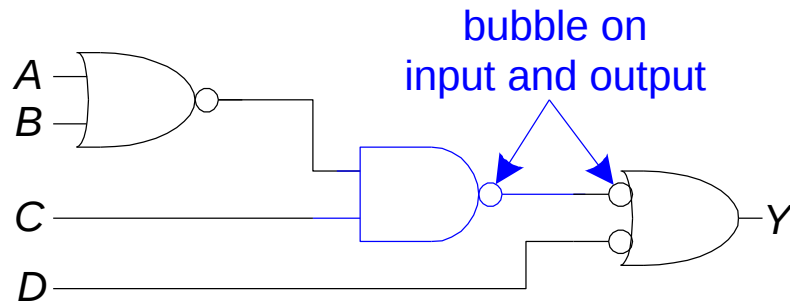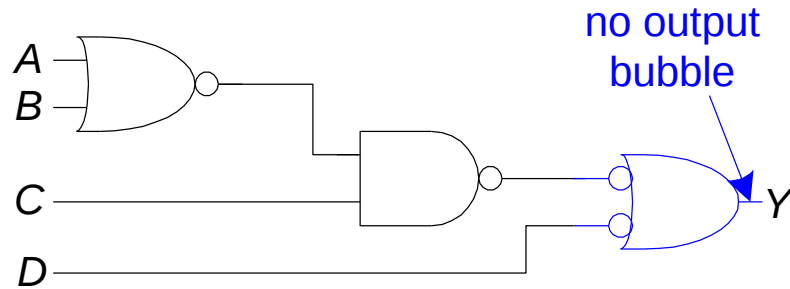

Bubble Pushing Example

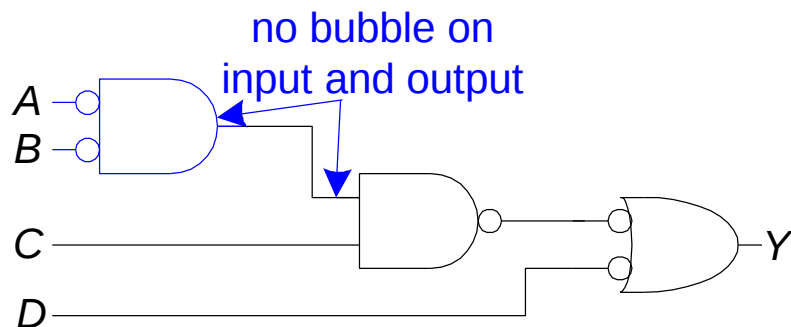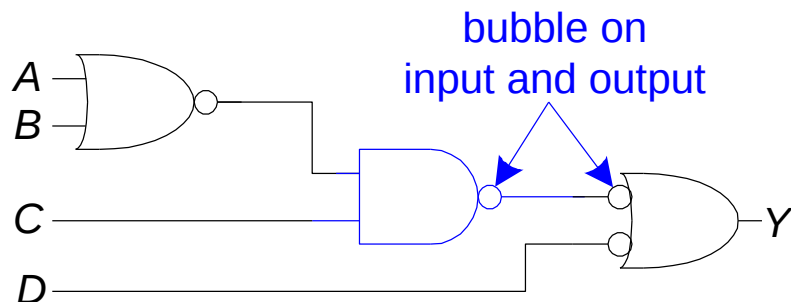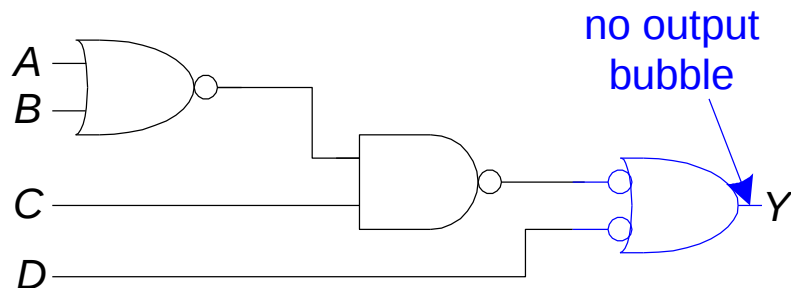

$$Y = \overline{A} \overline{B} C + \overline{D}$$

Canonical SOP & POS Form Revisited

- SOP – sum-of-products

O	C	E	minterm
0	0	0	$\overline{O} \overline{C}$
0	1	0	$\overline{O} C$
1	0	1	$O \overline{C}$
1	1	0	$O C$

How do we implement this logic function with gates?

$$E = O\overline{C}$$

$$= \Sigma(m_2)$$

- POS – product-of-sums


O	C	E	maxterm
0	0	0	$O + C$
0	1	0	$O + \overline{C}$
1	0	1	$\overline{O} + C$
1	1	0	$\overline{O} + \overline{C}$

$$E = (O + C)(O + \overline{C})(\overline{O} + \overline{C})$$

$$= \Pi(M_0, M_1, M_3)$$


From Logic to Gates

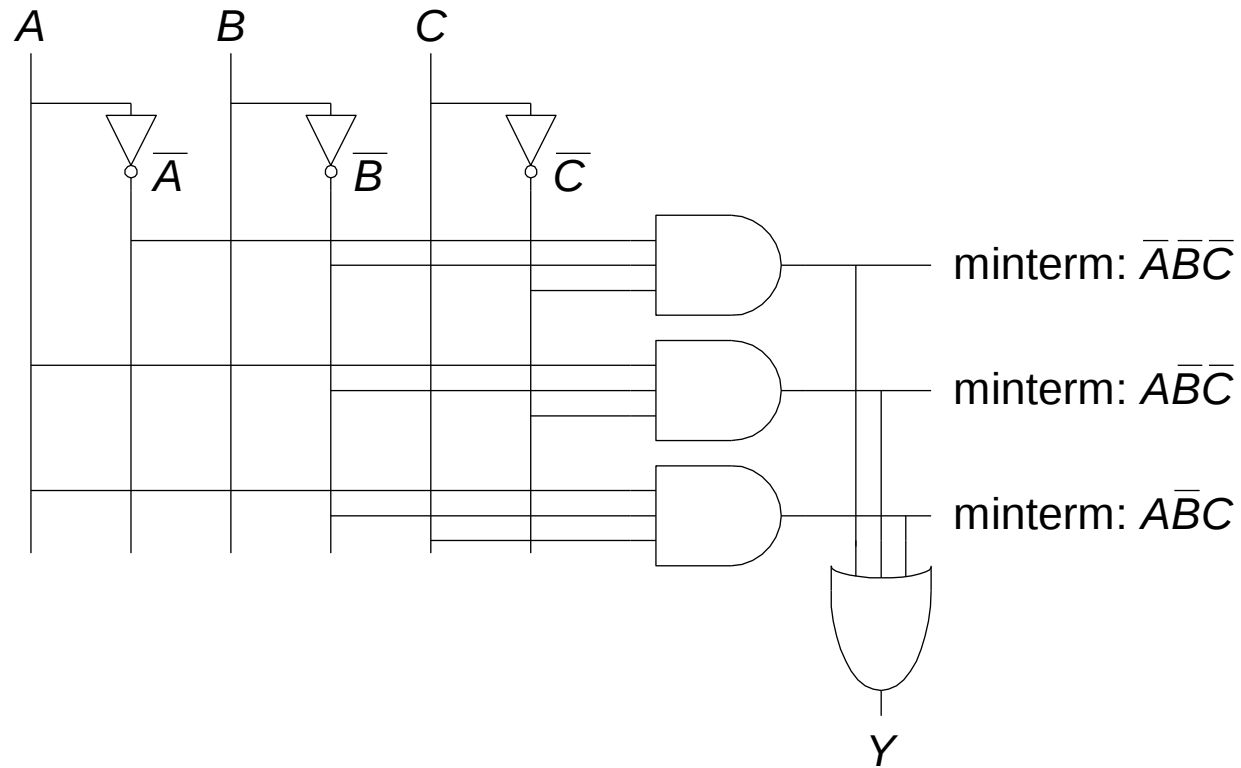- Two-level logic: ANDs followed by ORs
- Example: $Y = \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} + A\bar{B}C$



Circuit Schematics Rules

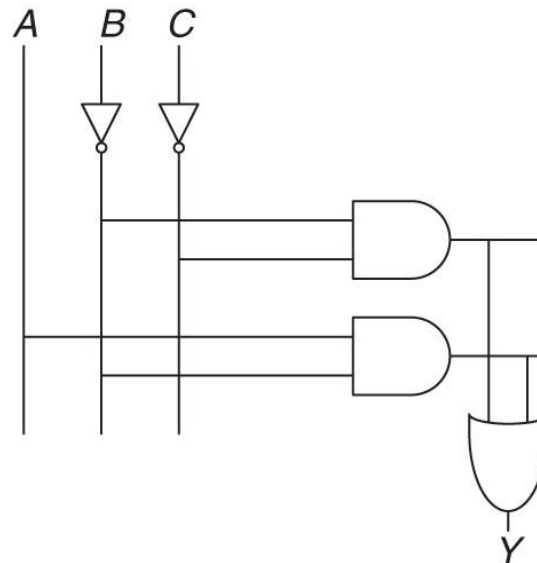- Inputs on the left (or top)
- Outputs on right (or bottom)
- Gates flow from left to right
- Straight wires are best




$$Y = \bar{B}\bar{C} + A\bar{B}$$


Circuit Schematic Rules (cont.)

- Wires always connect at a T junction
- A dot where wires cross indicates a connection between the wires
- Wires crossing *without* a dot make no connection


wires connect
at a T junction

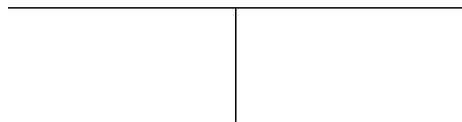

wires connect
at a dot

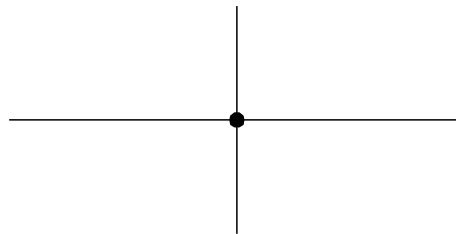

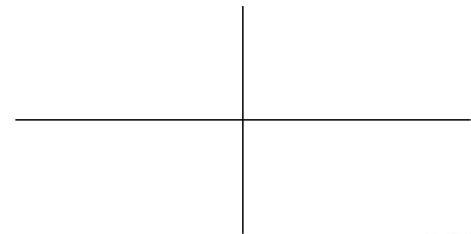
wires crossing
without a dot do
not connect



Multiple-Output Circuits

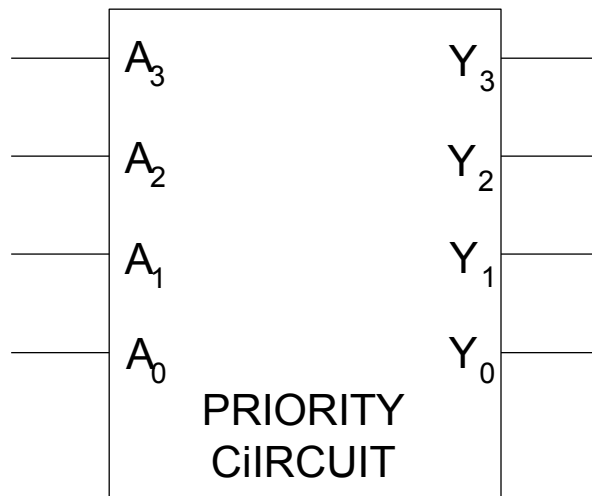- Example: Priority Circuit**

Output asserted
corresponding to
most significant
TRUE input




A_3	A_2	A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0				
0	0	0	1				1
0	0	1	0			1	
0	0	1	1			1	
0	1	0	0		1		
0	1	0	1		1		
0	1	1	0		1		
0	1	1	1		1		
1	0	0	0	1			
1	0	0	1	1			
1	0	1	0	1			
1	0	1	1	1			
1	1	0	0	1			
1	1	0	1	1			
1	1	1	0	1			
1	1	1	0	1			
1	1	1	1	1			
1	1	1	1	1			

Multiple-Output Circuits

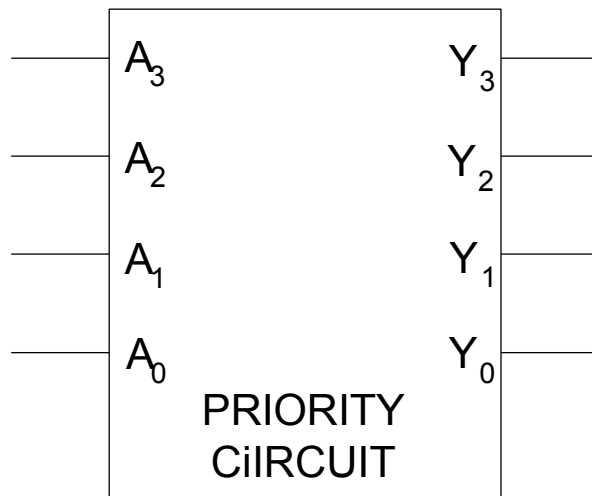- Example: Priority Circuit**


Output asserted
corresponding to
most significant
TRUE input



A_3	A_2	A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	0	1	0
0	1	0	0	0	1	0	0
0	1	0	1	0	1	0	0
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	0
1	0	0	0	1	0	0	0
1	0	0	1	1	0	0	0
1	0	1	0	1	0	0	0
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	0
1	1	1	0	1	0	0	0
1	1	1	1	1	0	0	0
1	1	1	1	1	0	0	0

Priority Circuit Hardware

A_3	A_2	A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	0	1	0
0	1	0	0	0	1	0	0
0	1	0	1	0	1	0	0
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	0
1	0	0	0	1	0	0	0
1	0	0	1	1	0	0	0
1	0	1	0	1	0	0	0
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	0
1	1	1	0	1	0	0	0
1	1	1	1	1	0	0	0

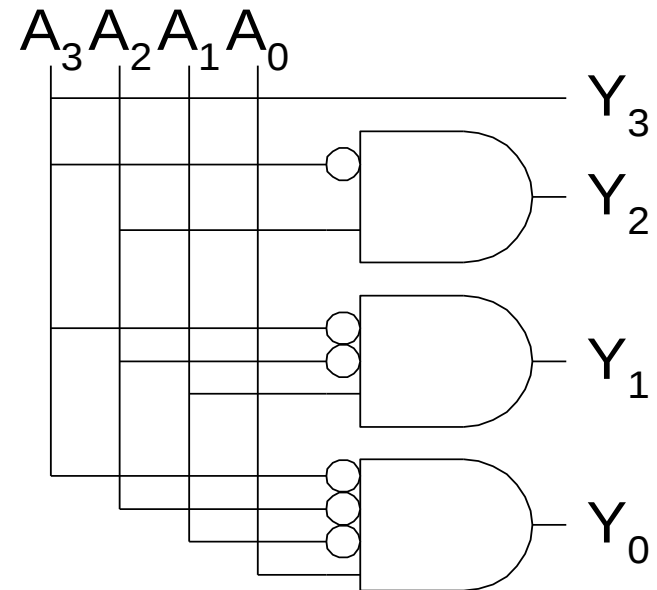


Don't Cares

- Simplify truth table by ignoring entries

A_3	A_2	A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	0	1	0
0	1	0	0	0	1	0	0
0	1	0	1	0	1	0	0
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	0
1	0	0	0	1	0	0	0
1	0	0	1	1	0	0	0
1	0	1	0	1	0	0	0
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	0
1	1	1	0	1	0	0	0
1	1	1	1	1	0	0	0


A_3	A_2	A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	X	0	0	1	0
0	1	X	X	0	1	0	0
1	X	X	X	1	0	0	0

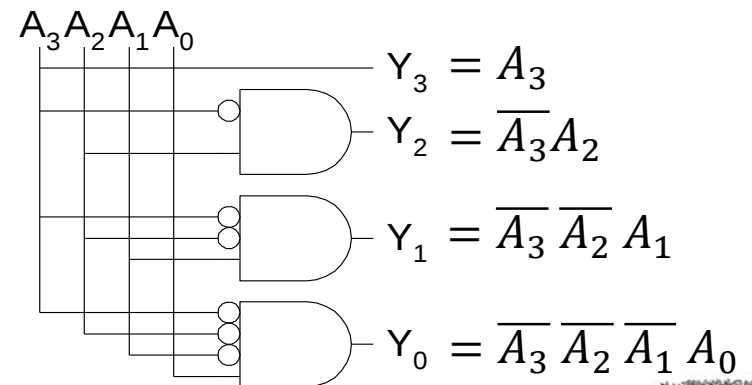Much easier to read off Boolean equations



Contention: X

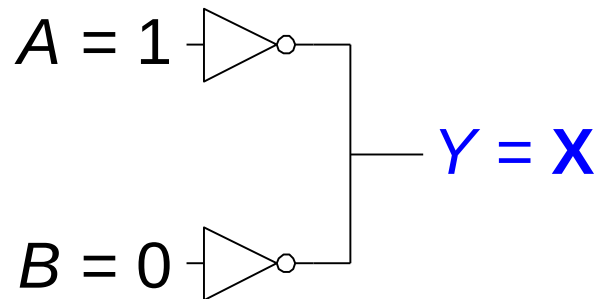- Contention: circuit tries to drive output to 1 **and** 0
 - Actual value somewhere in between
 - Could be 0, 1, or in forbidden zone
 - Might change with voltage, temperature, time, noise
 - Often causes excessive power dissipation




- **Warnings:**
 - Contention usually indicates a **bug**.
 - **X** is used for “don’t care” and contention - look at the context to tell them apart

Floating: Z

- Floating, high impedance, open, high Z
- Floating output might be 0, 1, or somewhere in between
 - A voltmeter won't indicate whether a node is floating

Tristate Buffer

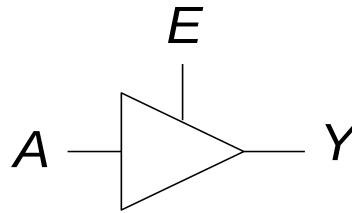

E	A	Y
0	0	Z
0	1	Z
1	0	0
1	1	1

Note: tristate buffer has an enable bit (E) to turn on the gate

Tristate Busses

- Floating nodes are used in tristate busses
 - Many different drivers
 - Exactly one is active at once

