

Karnaugh Maps (K-Maps)

- Boolean expressions can be minimized by combining terms
 - $PA + P\bar{A} = P$
- K-maps minimize equations graphically
 - Put terms to combine close to one another

A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

		AB			
		00	01	11	10
C	0	1	0	0	0
	1	1	0	0	0

		AB			
		00	01	11	10
C	0	$\bar{A}\bar{B}\bar{C}$	$\bar{A}B\bar{C}$	$AB\bar{C}$	$A\bar{B}\bar{C}$
	1	$\bar{A}\bar{B}C$	$\bar{A}BC$	ABC	$A\bar{B}C$

$$Y = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C = \bar{A}\bar{B}(C + \bar{C})$$



K-Map

- Circle 1's in adjacent squares
- In Boolean expression, include only literals whose true and complement form are **not** in the circle

A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

		AB			
C	Y	00	01	11	10
	0	1	0	0	0
1	1	1	0	0	0

$$Y = \bar{A}\bar{B}$$

C not included because both C and $\bar{C}$ included in circle



3-Input K-Map

Y C \ AB		00	01	11	10
0		$\bar{A}\bar{B}\bar{C}$	$\bar{A}B\bar{C}$	$A\bar{B}\bar{C}$	$AB\bar{C}$
		$\bar{A}\bar{B}C$	$\bar{A}BC$	ABC	$A\bar{B}C$

Truth Table

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

K-Map

Y C \ AB		00	01	11	10
0					
1					

K-Map Definitions

- **Complement:** variable with a bar over it
 $\bar{A}, \bar{B}, \bar{C}$
- **Literal:** variable or its complement
 $\bar{A}, A, \bar{B}, B, C, \bar{C}$
- **Implicant:** product of literals
 $\bar{A}\bar{B}C, \bar{A}C, BC$
- **Prime implicant:** implicant corresponding to the largest circle in a K-map

K-Map Rules

- Every **1 must be circled** at least once
- Each circle must span a **power of 2** (i.e. 1, 2, 4) squares in each direction
- Each **circle** must be **as large** as possible
- A circle may **wrap around the edges**
- A “don't care” (**X**) is **circled only if it helps** minimize the equation

4-Input K-Map

<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>Y</i>
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

		<i>AB</i>			
		00	01	11	10
<i>CD</i>	00				
	01				
	11				
	10				

4-Input K-Map

<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>Y</i>
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

<i>Y</i> <i>CD</i> \ <i>AB</i>		00	01	11	10
00		1	0	0	1
01		0	1	0	1
11		1	1	0	0
10		1	1	0	1

4-Input K-Map

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

		AB			
Y	CD	00	01	11	10
		00	01	11	10
	00	1	0	0	1
	01	0	1	0	1
	11	1	1	0	0
	10	1	1	0	1

$$Y = \bar{A}\bar{C} + \bar{A}BD + A\bar{B}\bar{C} + \bar{B}\bar{D}$$

K-Maps with Don't Cares

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	X
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

		AB			
Y	CD	00	01	11	10
	00				
	01				
	11				
	10				

K-Maps with Don't Cares

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	X
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

		AB			
Y	CD	00	01	11	10
	00	1	0	X	1
	01	0	X	X	1
	11	1	1	X	X
	10	1	1	X	X

K-Maps with Don't Cares

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	X
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

Y CD \ AB	00	01	11	10
00	1	0	X	1
01	0	X	X	1
11	1	1	X	X
10	1	1	X	X

$$Y = A + \bar{B}\bar{D} + C$$

4-Input K-Map: POS & SOP Form

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

		AB			
Y	CD	00	01	11	10
	00	1	0	0	1
	01	0	1	0	1
	11	1	1	0	0
	10	1	1	0	1

4-Input K-Map: POS Form

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

		AB			
Y	CD	00	01	11	10
		00	01	11	10
	00	1	0	0	1
	01	0	1	0	1
	11	1	1	0	0
	10	1	1	0	1

$$Y = \bar{A}C + \bar{A}BD + A\bar{B}\bar{C} + \bar{B}\bar{D}$$

4-Input K-Map: SOP Form

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

Y CD \ AB					
		00	01	11	10
00	1	0	0	1	
	0	1	0	1	
	1	1	0	0	
	1	1	0	1	

Canonical POS Expansion

- “Add” literal/complement terms to reverse simplification ($\rightarrow$ expand literal)
- Example
 - $Y = C$
 - $Y = C + A\bar{A}$
 - $Y = (C + A) \cdot (C + \bar{A})$
 - $Y = [(C + A) + B\bar{B}](C + \bar{A})$
 - $Y = [(C + A + B)(C + A + \bar{B})](C + \bar{A})$
 - ...

Combinational Building Blocks

- Multiplexers
- Decoders


Multiplexer (Mux)

- Selects between one of N inputs to connect to output
 - $\log_2 N$ -bit required to select input – control input S

- Example:

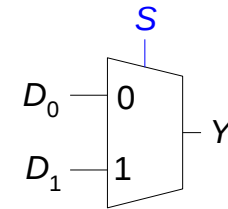2:1 Mux (2 inputs to 1 output)

- $N = 2$
- $\log_2 2 = 1$ control bit required



S	D_1	D_0	Y	S	Y
0	0	0	0	0	D_0
0	0	1	1	1	D_1
0	1	0	0		
0	1	1	1		
1	0	0	0		
1	0	1	0		
1	1	0	1		
1	1	1	1		

Multiplexer Implementations


- Logic gates

- Sum-of-products form

S	D ₁	D ₀	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1


Y	S	D ₀ D ₁			
		00	01	11	10
	0	0	0	1	1
	1	0	1	1	0

$$Y = D_0 \bar{S} + D_1 S$$

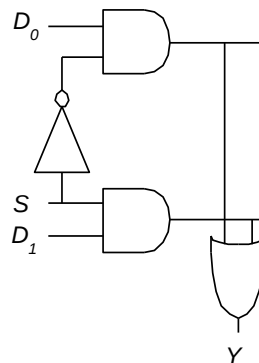

- Tristates

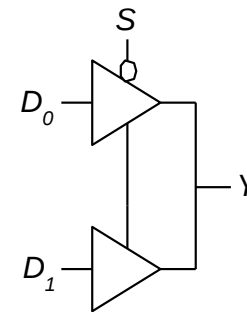- For an N-input mux, use N tristates
- Turn on exactly one to select the appropriate input




Logic using Multiplexers

- Using the mux as a lookup table
 - Zero outputs tied to GND
 - One output tied to VDD


A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

$$Y = AB$$

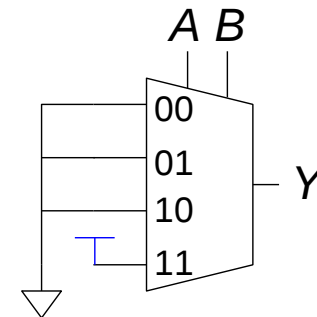


Logic using Multiplexers

- Reducing the size of the mux

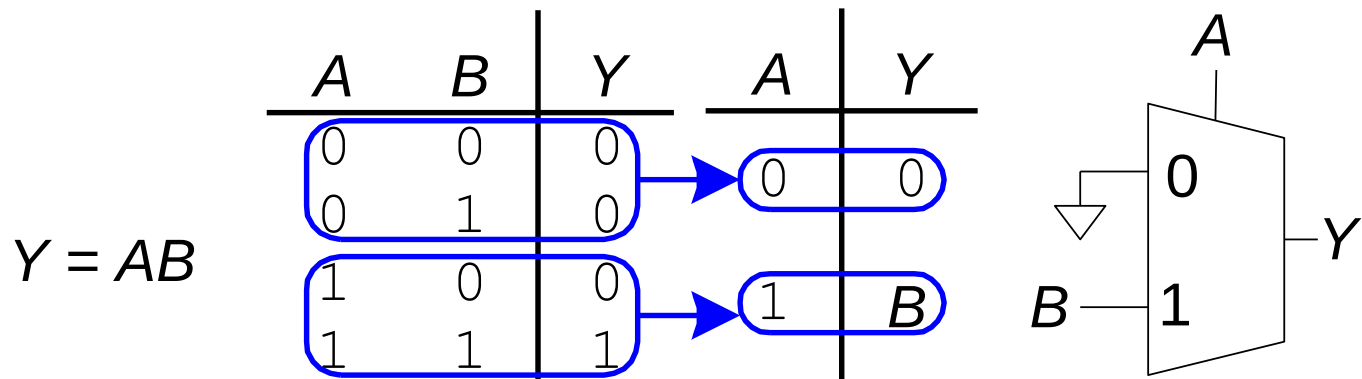

Decoders

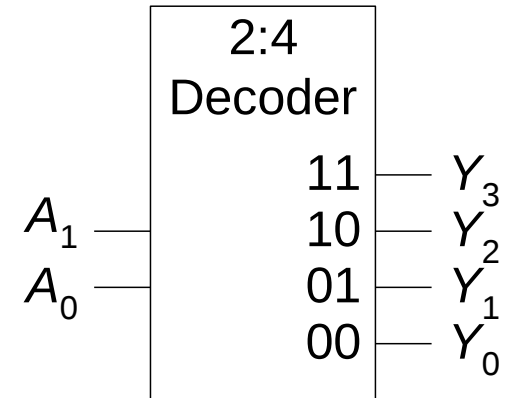- N inputs, 2^N outputs
- One-hot outputs: only one output HIGH at once



- Example


2:4 Decoder (2 inputs to 4 outputs)

- A_i decimal value selects the corresponding output

A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0




Decoder Implementation

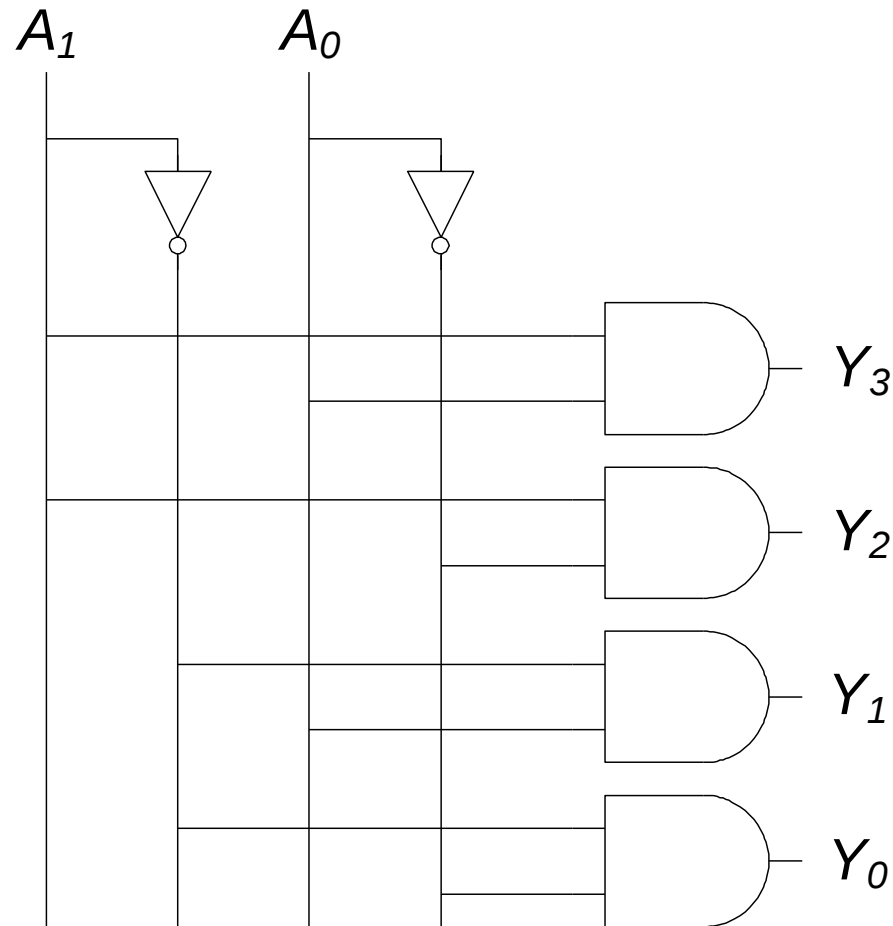


Logic Using Decoders

- OR minterms

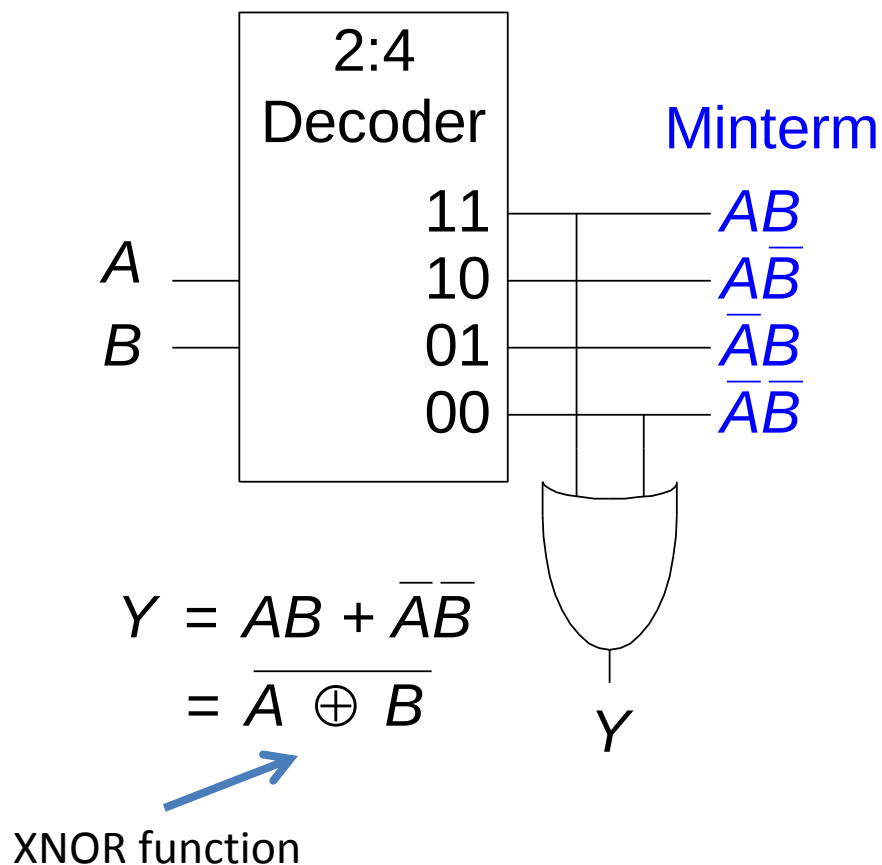

Timing

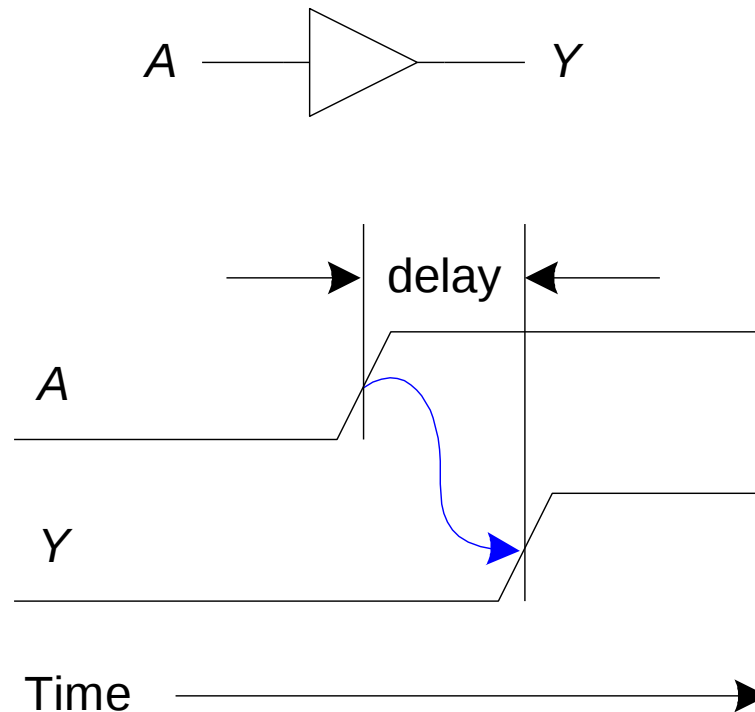
- Delay between input change and output changing



- How to build fast circuits?

Propagation & Contamination Delay

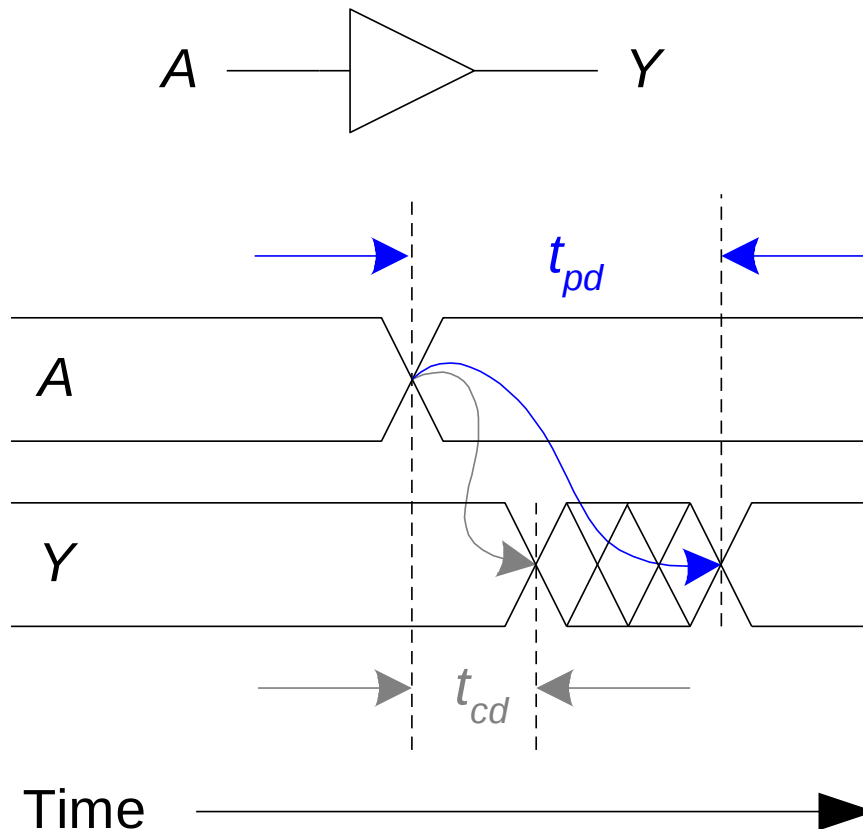- **Propagation delay:** t_{pd} = max delay from input to final output
- **Contamination delay:** t_{cd} = min delay from input to initial output change



Note: Timing diagram shows a signal with a high and low and transition time as an 'X'.


Cross hatch indicates unknown/changing values

Propagation & Contamination Delay

- Delay is caused by
 - Capacitance and resistance in a circuit
 - Speed of light limitation
- Reasons why t_{pd} and t_{cd} may be different:
 - Different rising and falling delays
 - Multiple inputs and outputs, some of which are faster than others
 - Circuits slow down when hot and speed up when cold



Critical (Long) & Short Paths

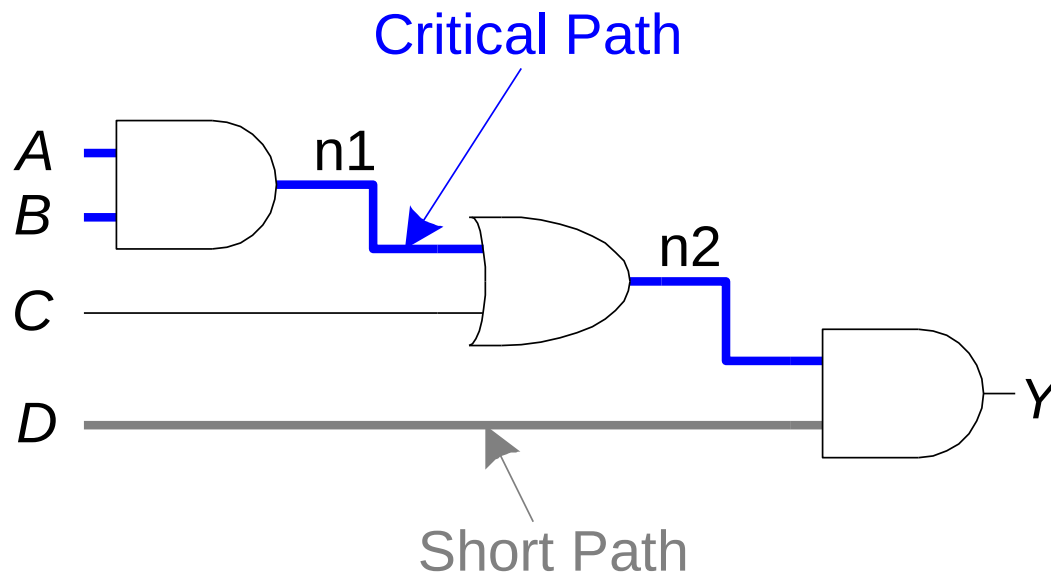

Critical (Long) Path: $t_{pd} = 2t_{pd_AND} + t_{pd_OR}$


Short Path: $t_{cd} = t_{cd_AND}$

Glitches

- When a single input change causes an output to change multiple times

Glitch Example


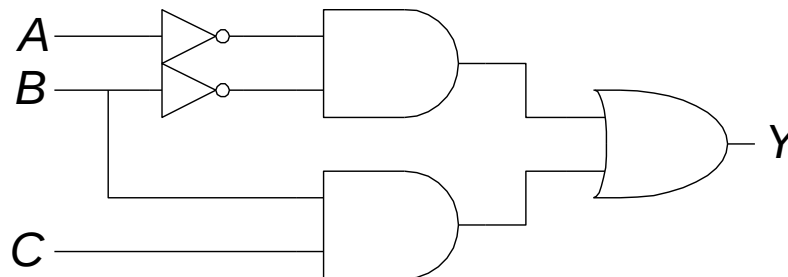
- What happens when $A = 0$, $C = 1$, B falls?



		AB			
		00	01	11	10
C	0	1	0	0	0
	1	1	1	1	0



$$Y = \bar{A}\bar{B} + BC$$

Glitch Example (cont.)

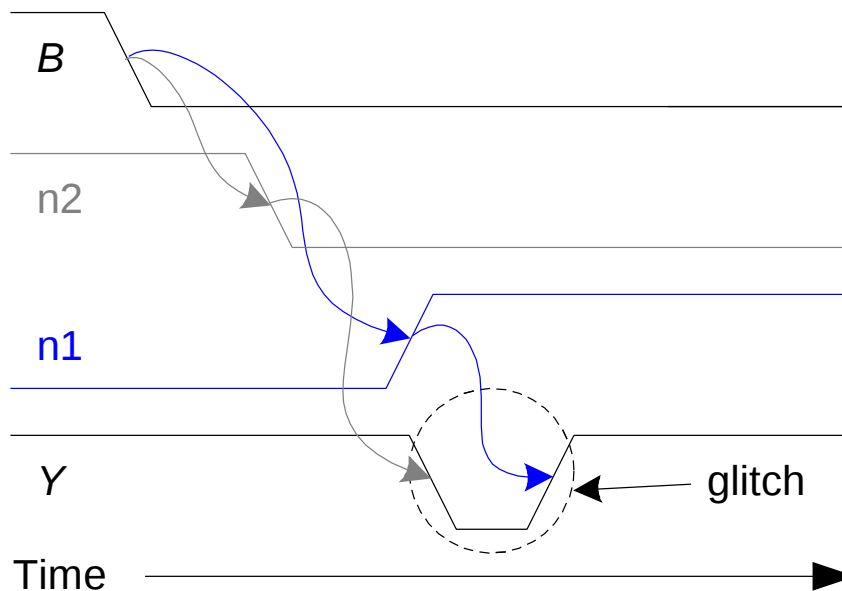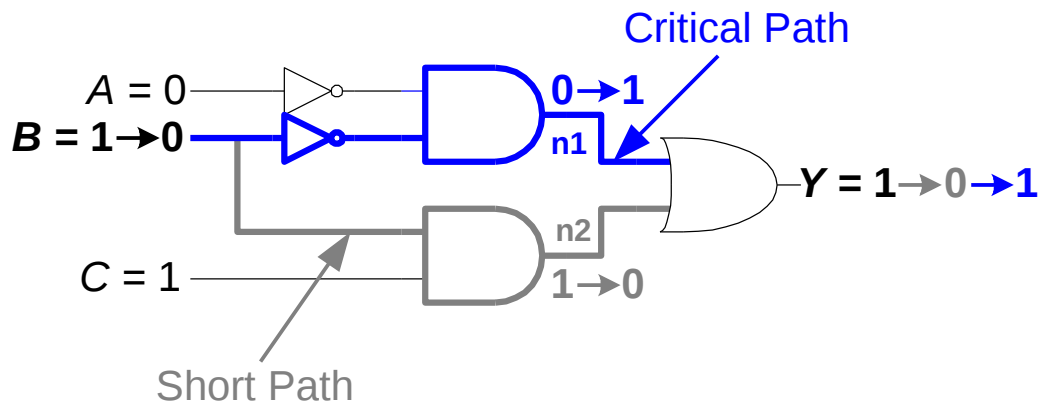

Note: $n1$ is slower than $n2$ because of the extra inverter for B to go through

Fixing the Glitch

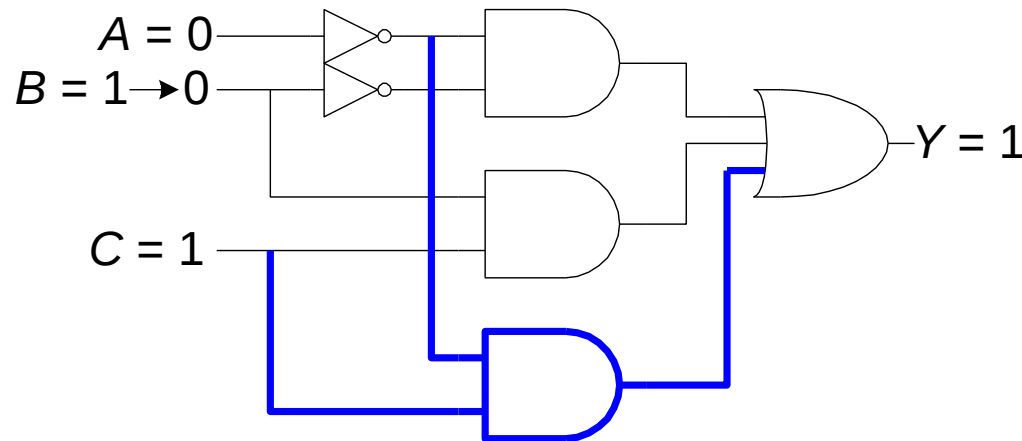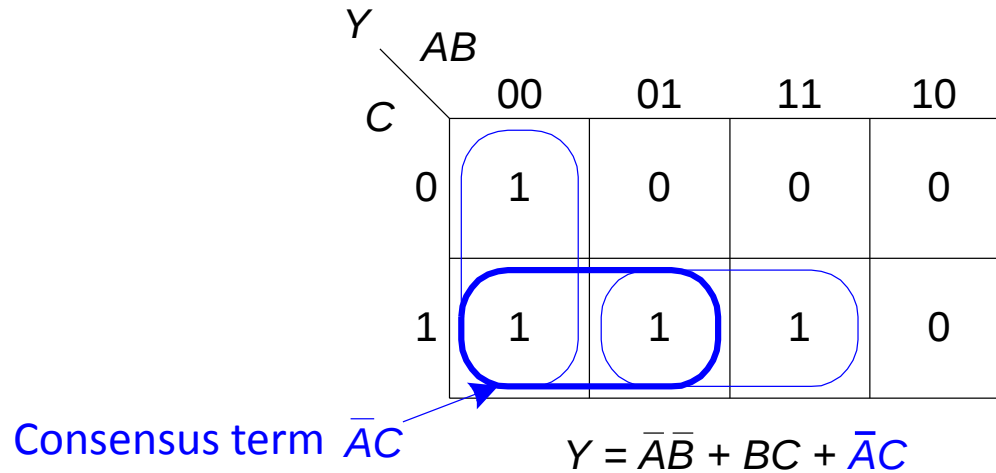

Why Understand Glitches?

- Glitches shouldn't cause problems because of **synchronous design** conventions (see Chapter 3)
- It's important to **recognize** a glitch: in simulations or on oscilloscope
- Can't get rid of all glitches – simultaneous transitions on multiple inputs can also cause glitches