

Combinational Building Blocks

- Multiplexers
- Decoders


Multiplexer (Mux)

- Selects between one of N inputs to connect to output
 - $\log_2 N$ -bit required to select input – control input S

- Example:

 2:1 Mux (2 inputs to 1 output)

- $N = 2$
- $\log_2 2 = 1$ control bit required



S	D_1	D_0	Y	S	Y
0	0	0	0	0	D_0
0	0	1	1	1	D_1
0	1	0	0		
0	1	1	1		
1	0	0	0		
1	0	1	0		
1	1	0	1		
1	1	1	1		

Multiplexer Implementations


- Logic gates

- Sum-of-products form

S	D ₁	D ₀	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1


Y	S	D ₀ D ₁			
		00	01	11	10
	0	0	0	1	1
	1	0	1	1	0

$$Y = D_0 \bar{S} + D_1 S$$

 

- Tristates

 - For an N-input mux, use N tristates
- Turn on exactly one to select the appropriate input




Logic using Multiplexers

- Using the mux as a lookup table
 - Zero outputs tied to GND
 - One output tied to VDD


A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

$$Y = AB$$

 


Logic using Multiplexers

- Reducing the size of the mux

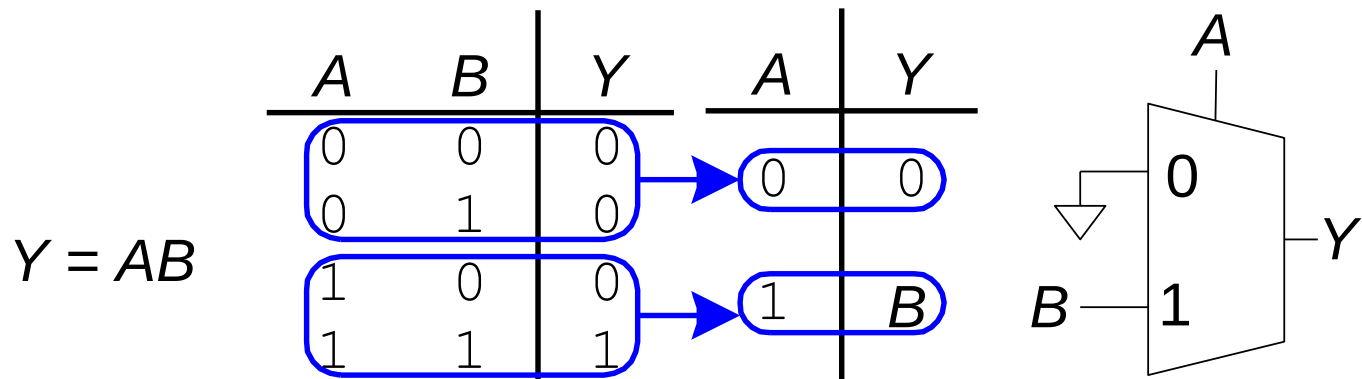

Decoders

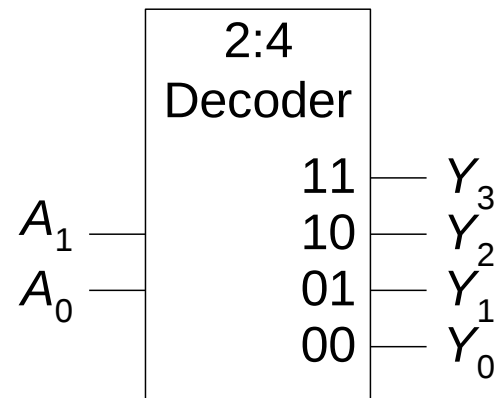- N inputs, 2^N outputs
- One-hot outputs: only one output HIGH at once




- Example

2:4 Decoder (2 inputs to 4 outputs)

- A_i decimal value selects the corresponding output


A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

Decoder Implementation

 


Logic Using Decoders

- OR minterms

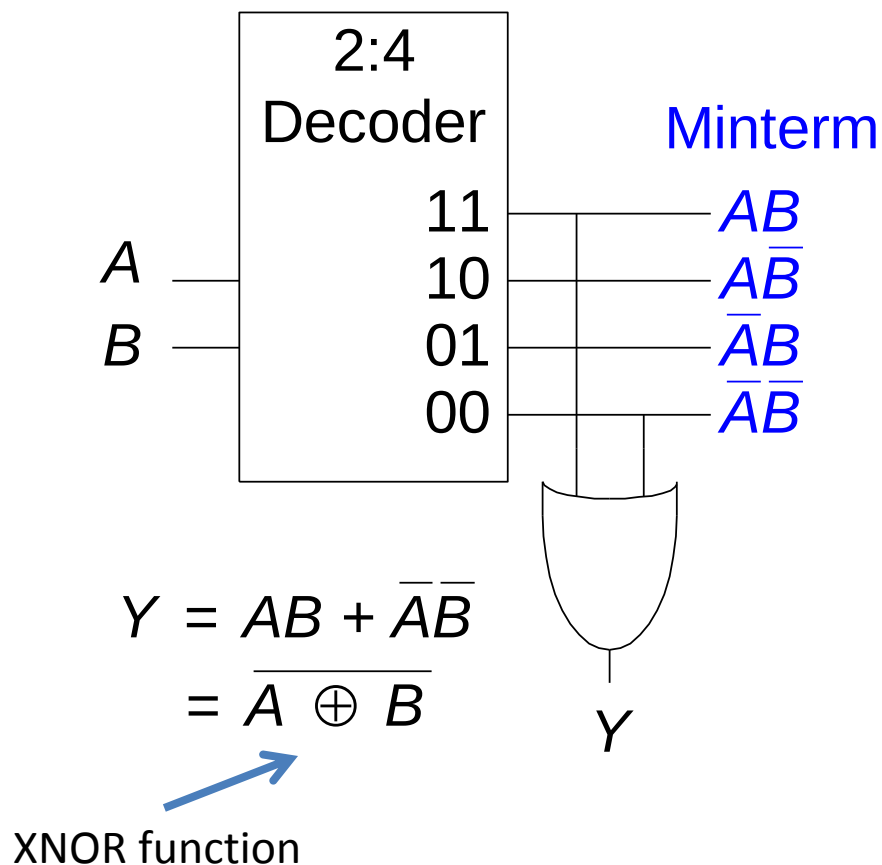

Timing

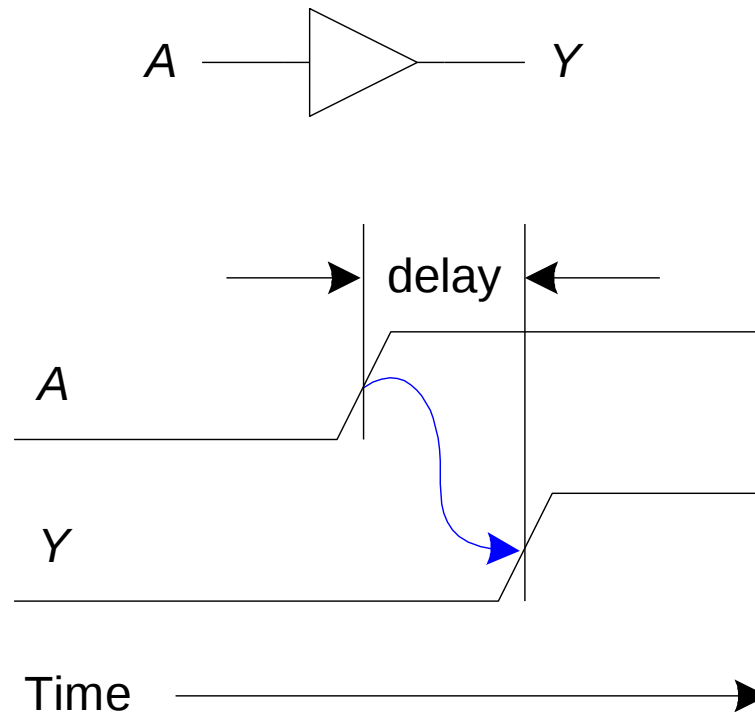
- Delay between input change and output changing



- How to build fast circuits?

Propagation & Contamination Delay

 - **Propagation delay:** t_{pd} = max delay from input to final output
- **Contamination delay:** t_{cd} = min delay from input to initial output change



Note: Timing diagram shows a signal with a high and low and transition time as an 'X'.


Cross hatch indicates unknown/changing values

Propagation & Contamination Delay

- Delay is caused by
 - Capacitance and resistance in a circuit
 - Speed of light limitation
- Reasons why t_{pd} and t_{cd} may be different:
 - Different rising and falling delays
 - Multiple inputs and outputs, some of which are faster than others
 - Circuits slow down when hot and speed up when cold



Critical (Long) & Short Paths

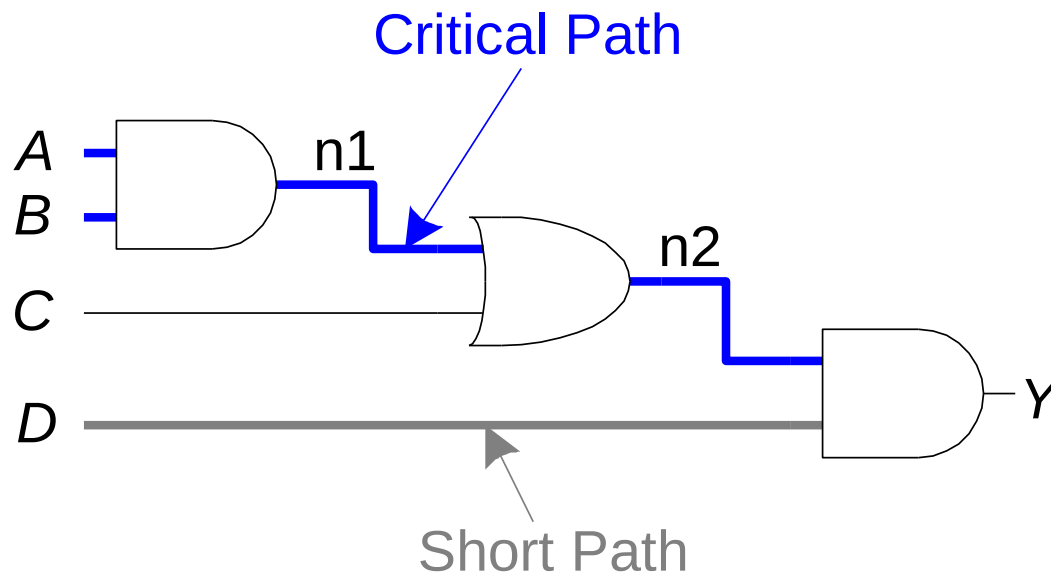

Critical (Long) Path: $t_{pd} = 2t_{pd_AND} + t_{pd_OR}$


Short Path: $t_{cd} = t_{cd_AND}$

Glitches

- When a single input change causes an output to change multiple times

Glitch Example


 
- What happens when $A = 0$, $C = 1$, B falls?



		AB			
		00	01	11	10
C	0	1	0	0	0
	1	1	1	1	0

$$Y = \bar{A}\bar{B} + BC$$

Glitch Example (cont.)

  


Note: $n1$ is slower than $n2$ because of the extra inverter for B to go through

Fixing the Glitch

Y C	AB			
	00	01	11	10
0	1	0	0	0
1	1	1	1	0

Consensus term $\bar{A}C$

$$Y = \bar{A}\bar{B} + BC + \bar{A}C$$

 

Why Understand Glitches?

- Glitches shouldn't cause problems because of **synchronous design** conventions (see Chapter 3)
- It's important to **recognize** a glitch: in simulations or on oscilloscope
- Can't get rid of all glitches – simultaneous transitions on multiple inputs can also cause glitches