 


Finite State Machine (FSM)

- Consists of:


- State register**

- Stores current state
 - Loads next state at clock edge



- Combinational logic**

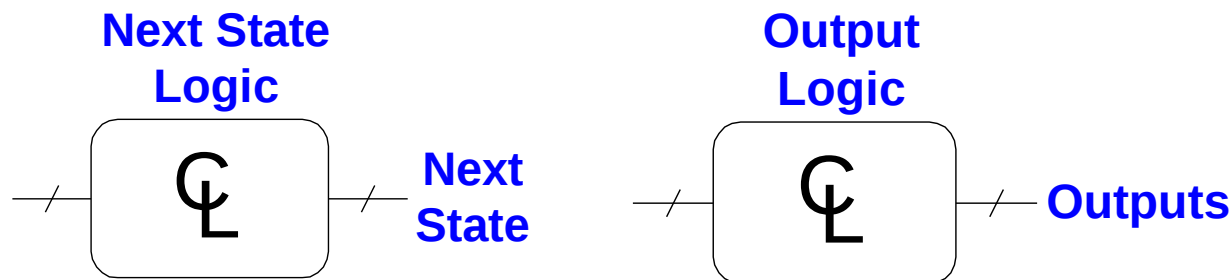
- Computes the next state
 - Computes the outputs




Finite State Machines (FSMs)

- Next state determined by current state and inputs
- Two types of finite state machines differ in output logic:
 - **Moore FSM:** outputs depend only on current state
 - **Mealy FSM:** outputs depend on current state *and* inputs

Moore FSM

 

Mealy FSM

 


FSM Design Procedure

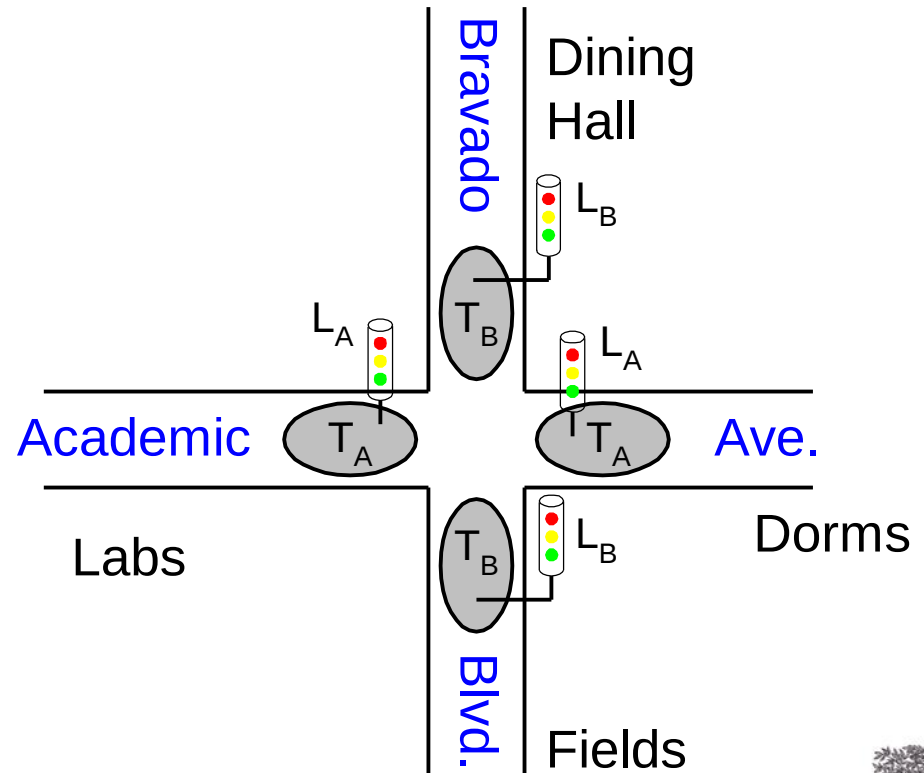1. Identify inputs and outputs
2. Sketch state transition diagram
3. Write state transition table
4. Select state encodings
5. Rewrite state transition table with state encodings
6. Write output table
7. Write Boolean equations for next state and output logic
8. Sketch the circuit schematic

FSM Example

- Traffic light controller
 - Traffic sensors: T_A , T_B (TRUE when there's traffic)
 - Lights: L_A , L_B




FSM Design Procedure

 1. **Identify inputs and outputs**
2. Sketch state transition diagram
3. Write state transition table
4. Select state encodings
5. Rewrite state transition table with state encodings
6. Write output table
7. Write Boolean equations for next state and output logic
8. Sketch the circuit schematic



FSM Black Box

- Inputs: CLK , $Reset$, T_A , T_B
- Outputs: L_A , L_B





FSM Design Procedure

  1. Identify inputs and outputs
2. **Sketch state transition diagram**
3. Write state transition table
4. Select state encodings
5. Rewrite state transition table with state encodings
6. Write output table
7. Write Boolean equations for next state and output logic
8. Sketch the circuit schematic





FSM State Transition Diagram

- **Moore FSM:** outputs labeled in each state
- **States:** Circles
- **Transitions:** Arcs



FSM State Transition Diagram

  - **Moore FSM:** outputs labeled in each state
- **States:** Circles
- **Transitions:** Arcs




FSM Design Procedure

1. Identify inputs and outputs
2. Sketch state transition diagram
3. **Write state transition table**
4. Select state encodings
5. Rewrite state transition table with state encodings
6. Write output table
7. Write Boolean equations for next state and output logic
8. Sketch the circuit schematic


FSM State Transition Table

Current State S	Inputs		Next State S'
	T_A	T_B	
S0	0	X	
S0	1	X	
S1	X	X	
S2	X	0	
S2	X	1	
S3	X	X	

 

FSM State Transition Table

Current State S	Inputs		Next State S'
	T_A	T_B	
S0	0	X	S1
S0	1	X	S0
S1	X	X	S2
S2	X	0	S3
S2	X	1	S2
S3	X	X	S0

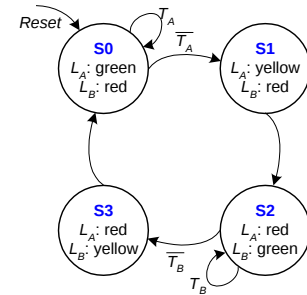

FSM Design Procedure

1. Identify inputs and outputs
2. Sketch state transition diagram
3. Write state transition table
4. **Select state encodings**
5. **Rewrite state transition table with state encodings**
6. Write output table
7. Write Boolean equations for next state and output logic
8. Sketch the circuit schematic




FSM Encoded State Transition Table

Current State		Inputs		Next State	
S_1	S_0	T_A	T_B	S'_1	S'_0
0	0	0	X		
0	0	1	X		
0	1	X	X		
1	0	X	0		
1	0	X	1		
1	1	X	X		

State	Encoding
S0	00
S1	01
S2	10
S3	11

Two bits required for 4 states

 

FSM Encoded State Transition Table


Current State		Inputs		Next State	
S_1	S_0	T_A	T_B	S'_1	S'_0
0	0	0	X	0	1
0	0	1	X	0	0
0	1	X	X	1	0
1	0	X	0	1	1
1	0	X	1	1	0
1	1	X	X	0	0

State	Encoding
S0	00
S1	01
S2	10
S3	11

Two bits required for 4 states

$$S'_1 = S_1 \oplus S_0$$
 
$$S'_0 = \overline{S_1} \overline{S_0} \overline{T_A} + S_1 \overline{S_0} \overline{T_B}$$



FSM Design Procedure


1. Identify inputs and outputs
2. Sketch state transition diagram
3. Write state transition table
4. Select state encodings
5. Rewrite state transition table with state encodings
6. **Write output table**
7. **Write Boolean equations for next state and output logic**
8. Sketch the circuit schematic

FSM Output Table

Current State		Outputs			
S_1	S_0	L_{A1}	L_{A0}	L_{B1}	L_{B0}
0	0				
0	1				
1	0				
1	1				

Output	Encoding
green	00
yellow	01
red	10

Two bits required for 3 outputs

 

FSM Output Table

Current State		Outputs			
S_1	S_0	L_{A1}	L_{A0}	L_{B1}	L_{B0}
0	0	0	0	1	0
0	1	0	1	1	0
1	0	1	0	0	0
1	1	1	0	0	1

Output	Encoding
green	00
yellow	01
red	10


Two bits required for 3 outputs

$$L_{A1} = S_1$$

$$L_{A0} = \overline{S_1}S_0$$

$$L_{B1} = S_1$$


$$L_{B0} = S_1S_0$$

 

FSM Design Procedure

1. Identify inputs and outputs
2. Sketch state transition diagram
3. Write state transition table
4. Select state encodings
5. Rewrite state transition table with state encodings
6. Write output table
7. Write Boolean equations for next state and output logic
8. **Sketch the circuit schematic**

FSM Schematic: State Register

 

$$S'_1 = S_1 \oplus S_0$$

$$S'_0 = S_1 S_0 T_A + S_1 S_0 T_B$$

$$L_{A1} = S_1$$


$$L_{A0} = S_1 S_0$$

$$L_{B1} = S_1$$

$$L_{B0} = S_1 S_0$$




FSM Schematic: Next State Logic

 

$$S'_1 = S_1 \oplus S_0$$

$$S'_0 = S_1 S_0 T_A + S_1 S_0 T_B$$

FSM Schematic: Output Logic

 



$$L_{A1} = S_1$$

$$L_{B1} = S_1$$

$$L_{A0} = S_1 S_0$$

$$L_{B0} = S_1 S_0$$

FSM Timing Diagram

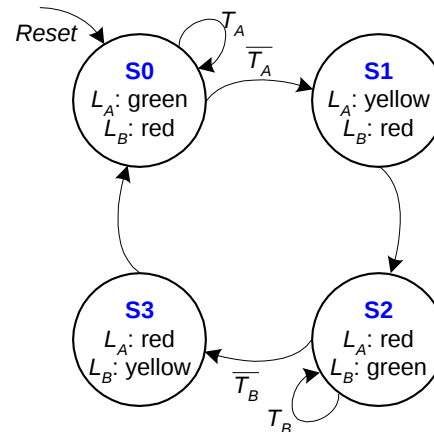 

FSM State Encoding

- **Binary** encoding:
 - i.e., for four states, 00, 01, 10, 11
- **One-hot** encoding
 - One state bit per state
 - Only one state bit HIGH at once
 - i.e., for 4 states, 0001, 0010, 0100, 1000
 - Requires more flip-flops
 - Often next state and output logic is simpler

FSM Design Procedure

1. Identify inputs and outputs
2. Sketch state transition diagram
3. Write state transition table
4. Select state encodings
5. Rewrite state transition table with state encodings
6. Write output table
7. Write Boolean equations for next state and output logic
8. Sketch the circuit schematic