

# CPE100: Digital Logic Design I



## Final Review

# Logistics

- Tuesday Dec 12<sup>th</sup>
  - 13:00-15:00 (1-3pm)
  - 2 hour exam
- Chapters 1-3, 5.4.1
  - Responsible for all material
- Closed book, closed notes
- No calculators
- Must show work and be legible for credit

# Preparation


- Read the book (2<sup>nd</sup> Edition)
  - Then, read it again
- Do example problems
  - Use both Harris and Roth books
- Be sure you understand homework solutions
- Come visit during office hours for questions
- Exam Advice: Be sure to attempt all problems.
  - Partial credit can only be given for something written on the page
  - Don't spend too much time thinking
  - Be sure to read questions completely

# Main New Material

- Synchronous timing
  - How can you ensure dynamic discipline is respected
- Parallelism
  - How can you increase operational speed
- Synchronous building blocks
  - Full-adder, counter

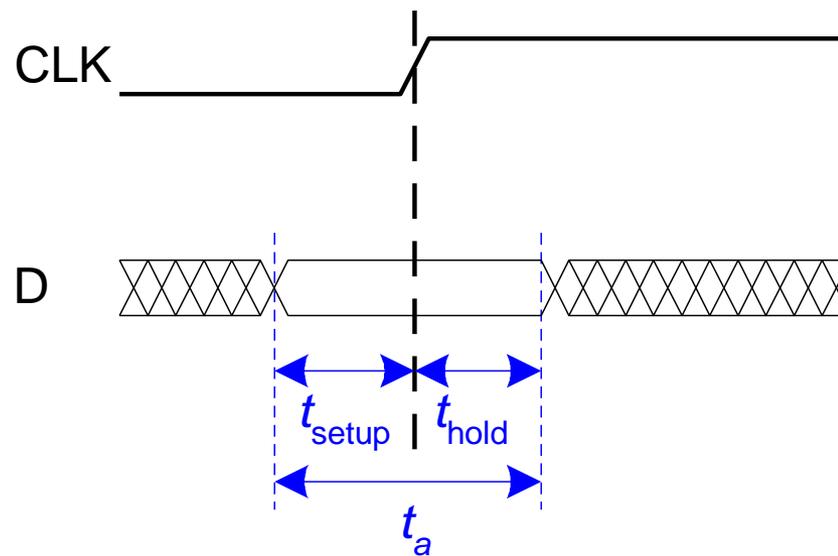
## Ch 3.5.2 Synchronous Timing

- Data input must be stable when sampled at rising clock edge
- Setup time:  $t_{setup}$  = time before clock edge data must be stable (i.e. not changing)
- Hold time:  $t_{hold}$  = time after clock edge data must be stable



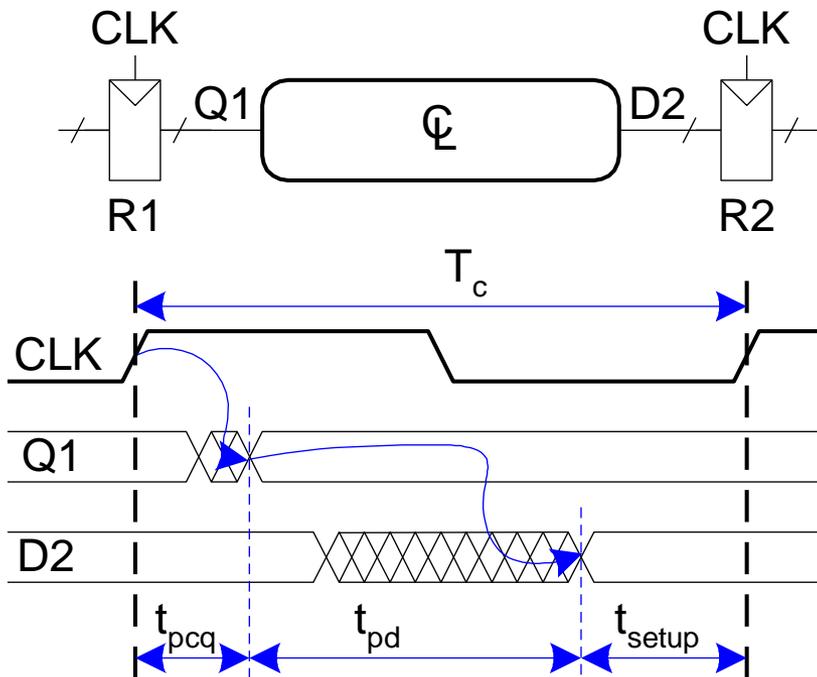
# Timing Constraints

- Setup Timing
- $D_2$  cannot change  $t_{setup}$  before next clock cycle
- $T_c \geq t_{pcq} + t_{pd} + t_{setup}$




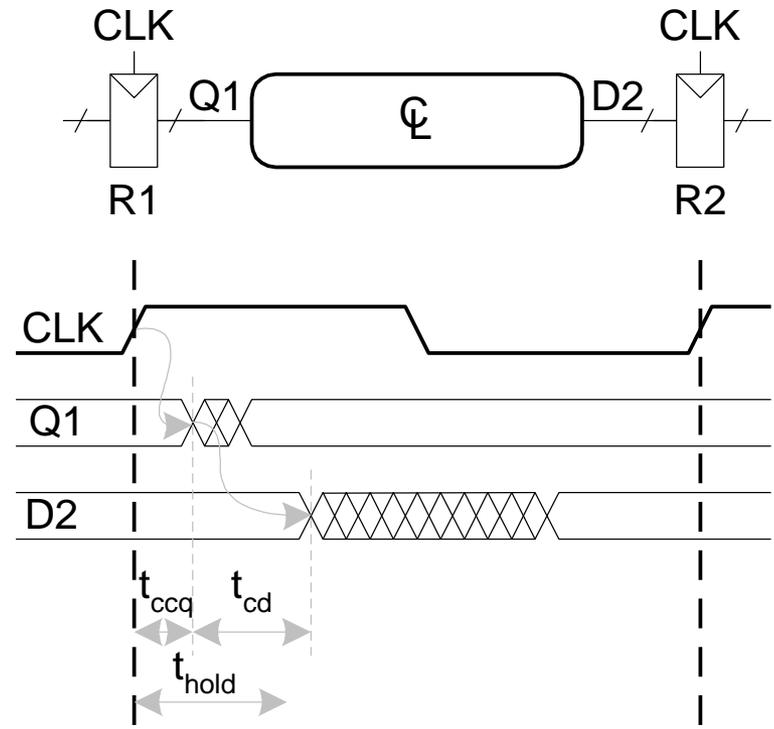
- Hold Timing
- $D_2$  cannot change until after  $t_{hold}$  of the current clock cycle
- $t_{hold} < t_{ccq} + t_{cd}$



## Ch 3.6 Parallelism


- Goal is to increase throughput of circuit
- Two types:
  - Spatial – duplicate hardware to do same task at once
  - Temporal – break task into smaller stages for pipelining (assembly line)
    - Note: this requires no dependencies between stages
- Token – group of inputs processed to produce group of outputs
- Latency – time for a single token to complete
- Throughput – # tokens produced per unit time

# Parallelism Timeline

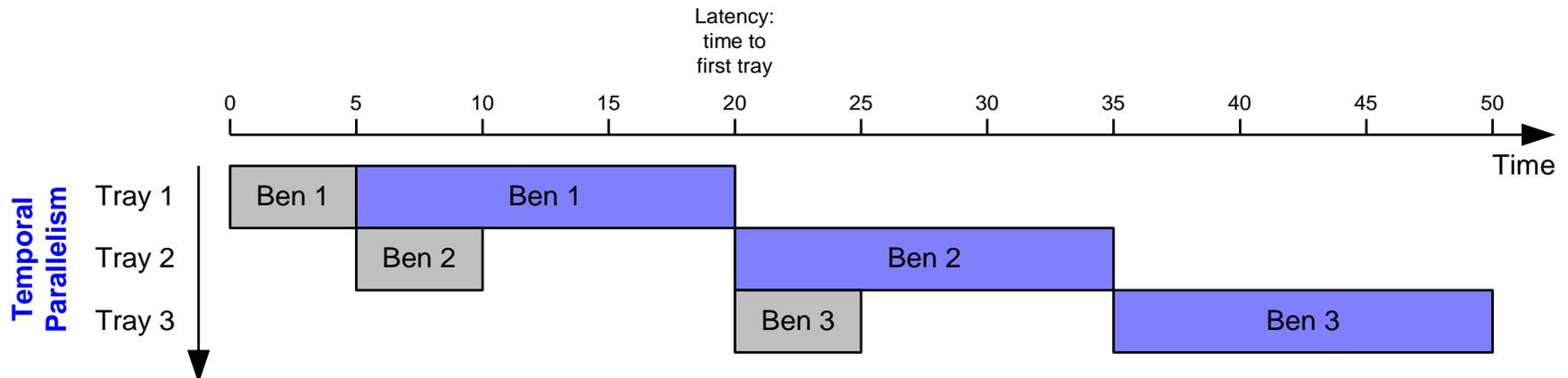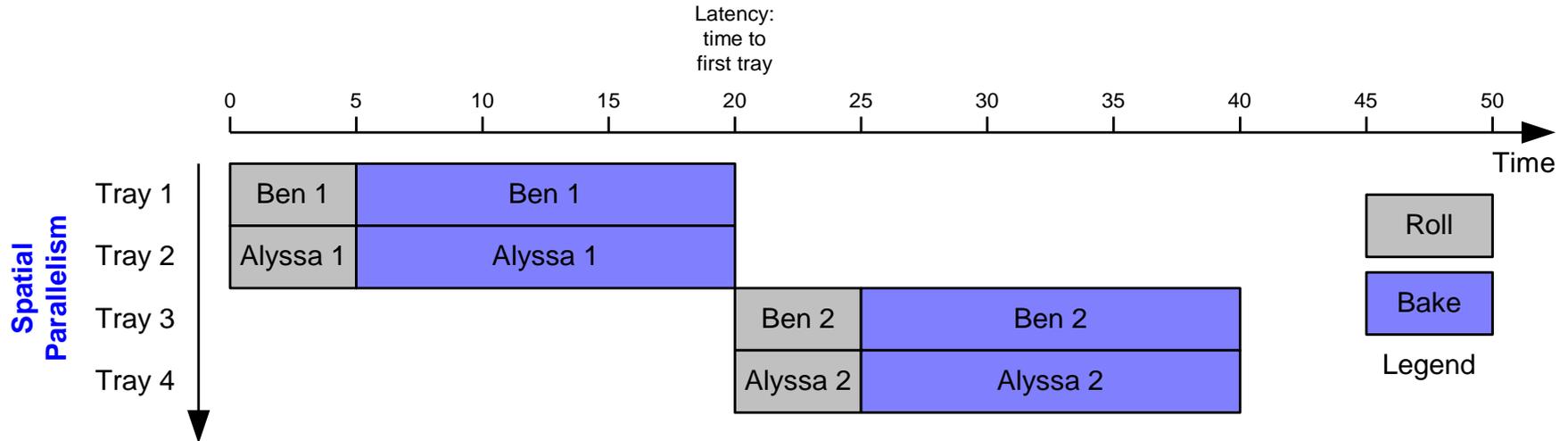

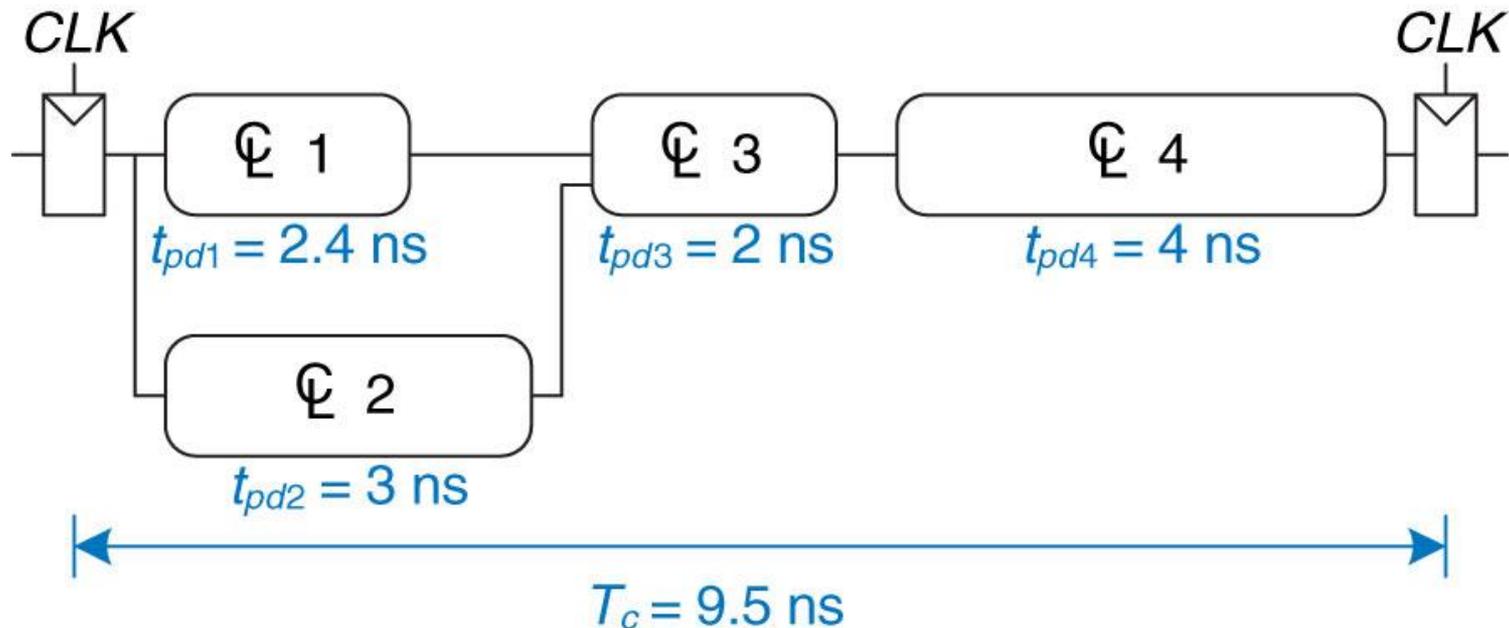
# Pipeline Example

- $t_{pcq} = 0.3, t_{setup} = 0.2$  ns
- Identify critical path




# Pipeline Example II

- Two-stage pipeline

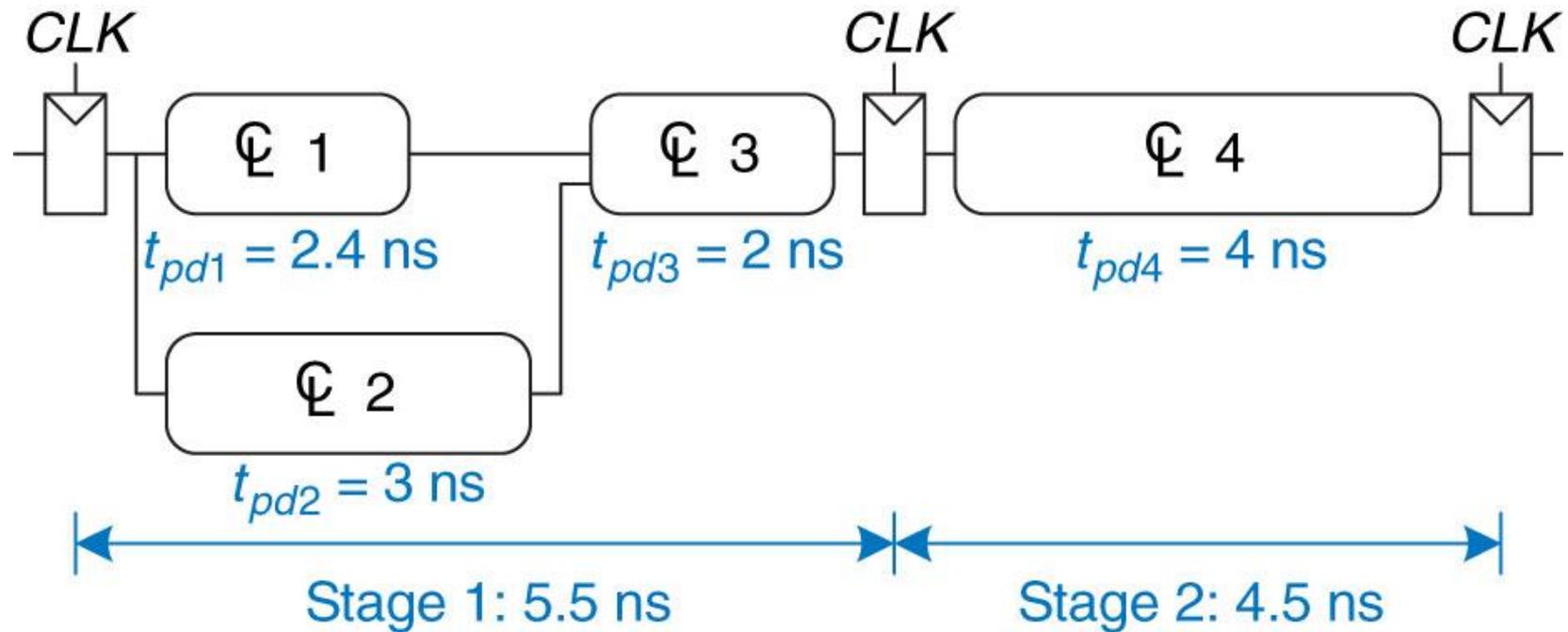

# Pipeline Example III

- Three-stage pipeline

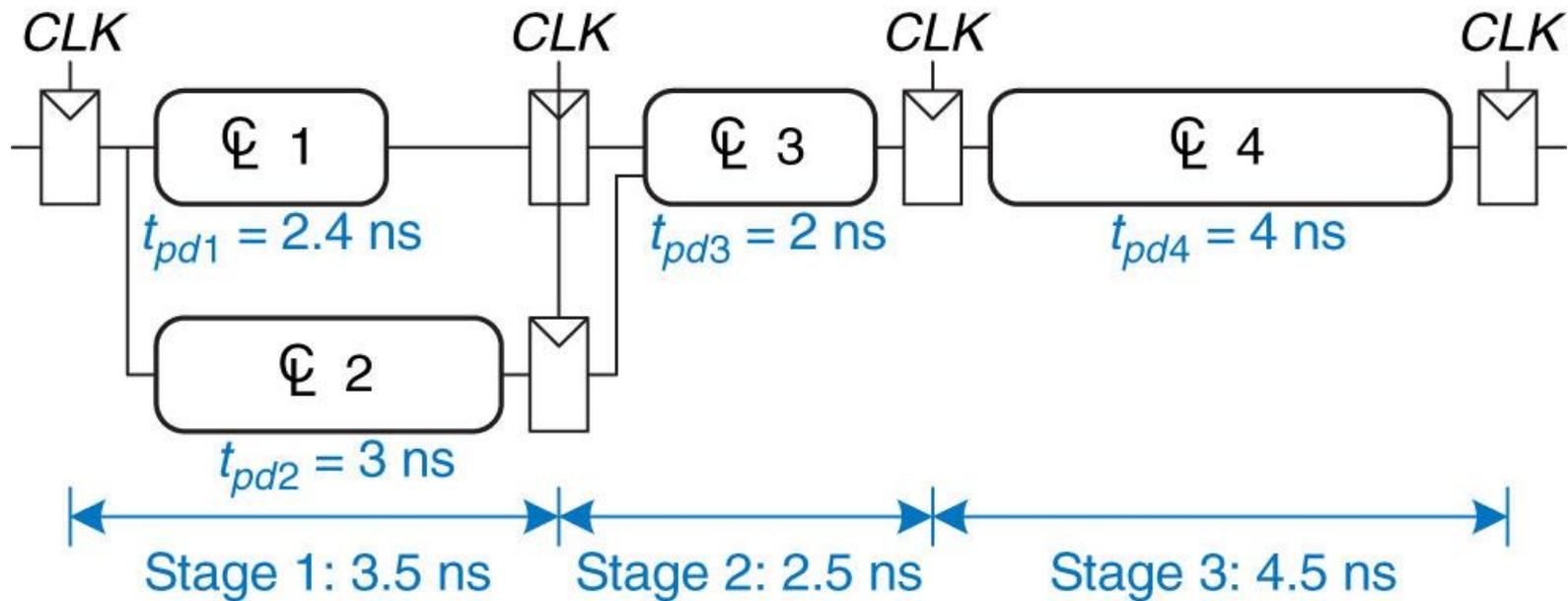


# Ch 5 Digital Building Blocks

- Emphasis on full adder (FA) and counter


- Understand ripple adder

- $t_{ripple} = Nt_{FA}$

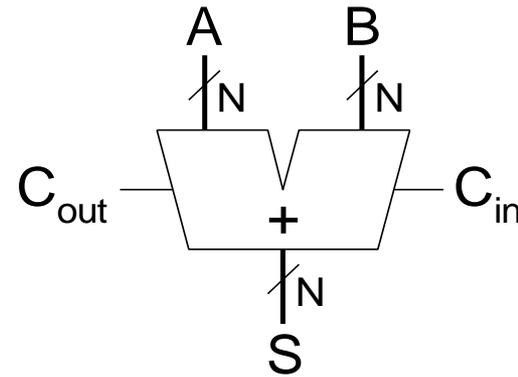


- Counter increments stored value each clock cycle

## Symbol

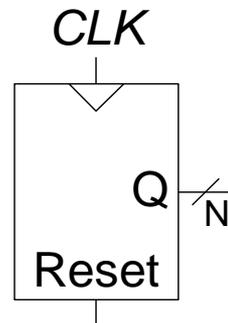


## Implementation

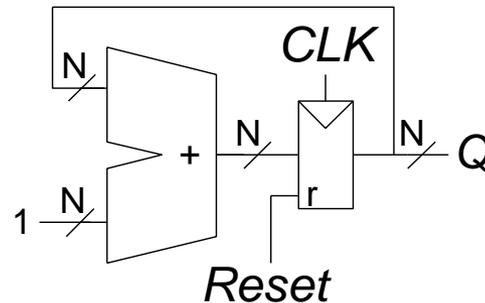
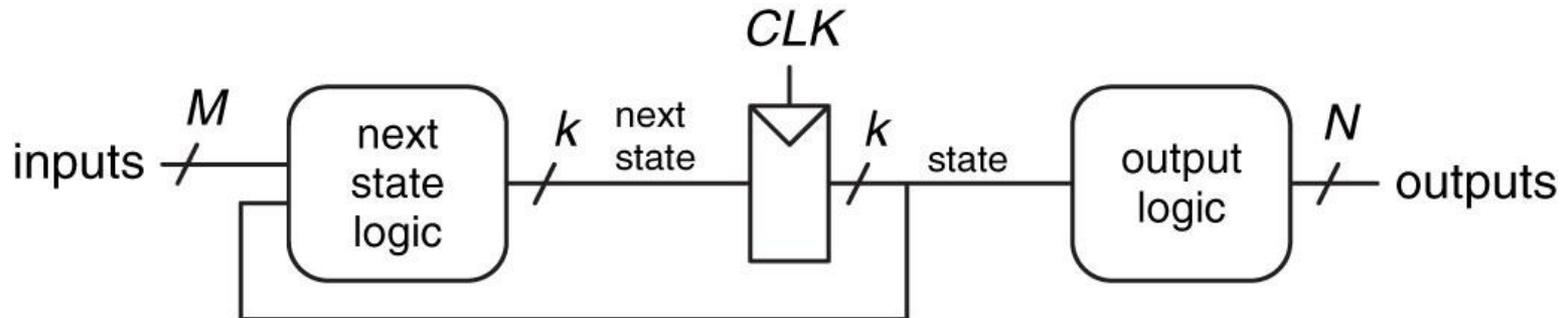
# Chapter 3.4 Finite State Machine

- Technique for representing synchronous sequential circuit
  - Consists of combinational logic and state register
  - Moore machine – output only dependent on state (not inputs)



# Chapter 3.4 FSM Design Steps

- 1. Identify inputs and outputs**
- 2. Sketch state transition diagram**
3. Write state transition table
4. Select state encodings
5. Rewrite state transition table with state encodings
6. Write output table
7. Write Boolean equations for next state and output logic
8. Sketch the circuit schematic

# Chapter 3.4 FSM Examples


- Given problem description, give state transition diagram
- Given state transition diagram, encode state and provide next state/output equations
- Given FSM circuit, describe what system does and give state transition/output tables

## Chapter 3.4 FSM Examples

- Design an edge detector circuit. The output should go HIGH for one cycle after the input makes a  $0 \rightarrow 1$  transition.
- Single input: A

# FSM Example

- State transition diagram

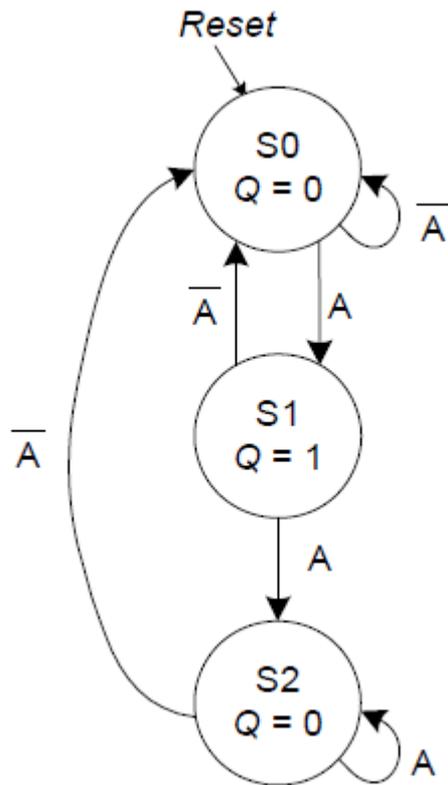


- State/Output Tables
  - Use binary state encoding

$S_1S_0$	$A$	$S'_1S'_0$	$Q$
00	0	00	0
00	1	01	0
01	0	00	1
01	1	10	1
10	0	00	0
10	1	10	0

# FSM Example

- Equations
- $S'_1 = AS_1 + AS_0$
- $S'_0 = A\bar{S}_1\bar{S}_0$
- $Q = S_1$

- Circuit diagram

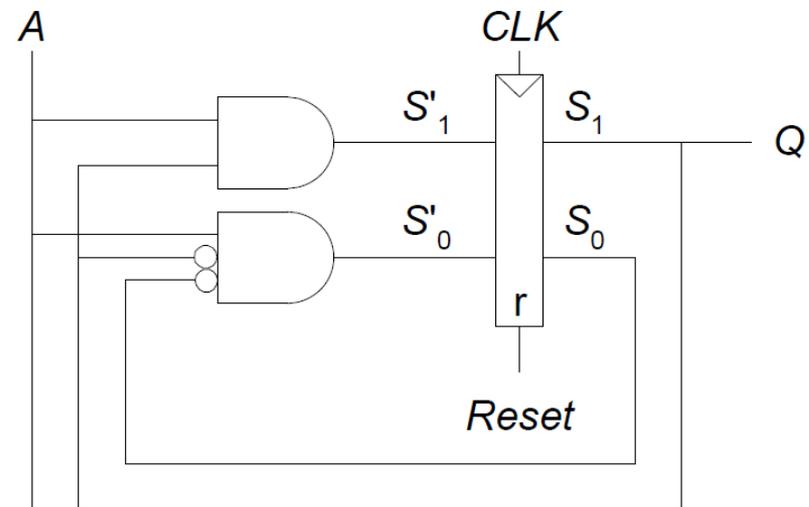

# Ch 1.4 Number Systems

- General number representation
  - N-digit number  $\{a_{N-1} a_{N-2} \dots a_1 a_0\}$  of base  $R$  in decimal
    - $a_{N-1}R^{N-1} + a_{N-2}R^{N-2} + \dots + a_1R^1 + a_0R^0$
    - $= \sum_{i=0}^{N-1} a_i R^i$
  - What is range of values?
- Should be very familiar with common bases such as 2, 10, 16
  - Be able to convert between bases

# Number Example

- What is  $10110_2$  in (unsigned) decimal?
  
  
  
  
  
  
  
  
  
  
- Convert  $10110_2$  to base 6

# Binary Addition

- Understand signed number representation (unsigned, two's complement, sign-mag)
- Addition
  - Potential for overflow – know how and when occurs
- Subtraction
  - Find negative of number and do addition
- Zero/sign extension – when should you use which?

# Binary Addition Example

- Assume 4-bit 2's complement and indicate if overflow occurs
- Add  $-8 + 4$

# Ch 1.5 Logic Gates

- Know circuit symbols and associated truth tables
  - NOT/BUF, AND/OR, NAND/NOR, XOR, XNOR
- Be able to determine output from gate level circuit schematic
  - Both give truth table and provide Boolean equation

# Ch 2.3-2.4 Boolean Equations

- Sum-of-product (SOP) minterm form
- Product-of-sum (POS) maxterm form
- Simplify using axioms/theorems
- Example

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

# Ch 2.7 Kmap

- Convert truth table to Kmap and draw bubbles to maximally cover ones
  - Be sure to know how to include don't cares
  - Know up to 5-input function
- Example

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1


# Ch 2.8 Mux/Decoder

- Know how to do logic with mux or decoder
- Mux

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

$$Y = A\bar{B} + \bar{B}\bar{C} + \bar{A}BC$$

(a)

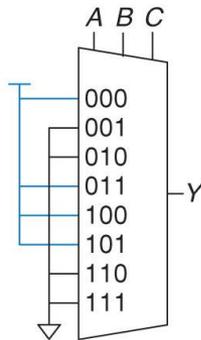


(b)

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0


(a)

(b)

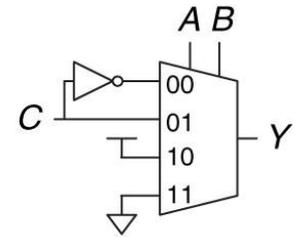

(c)

- Decoder

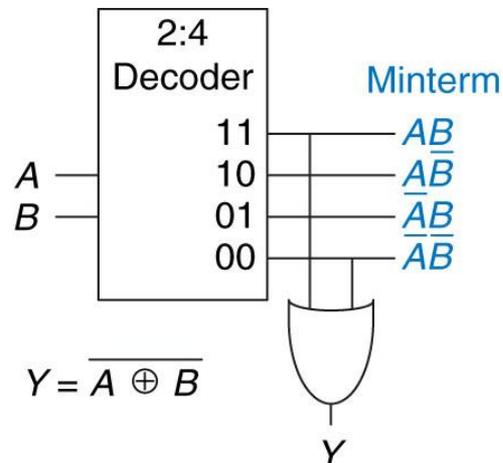

## Ch 2.9 Combinational Timing

- Delay for input to cause a change in output
- Propagation delay  $t_{pd}$  is longest time to see output change
- Contamination delay  $t_{cd}$  is shortest time to see output change

## Ch 3.2 Sequential Elements

- Sequential elements store “state” – have memory
- Need to know the operation of different devices
  - SR latch, D latch, D flip-flop
- Should also understand the internal circuitry for these elements
  - Given a sequential circuit design you can explain operation
  - Given a description of operation, build a circuit using sequential building blocks.

# Sequential Element Example

- How does the following work?

