

# Chapter 5




## ***Digital Design and Computer Architecture, 2<sup>nd</sup> Edition***

---

David Money Harris and Sarah L. Harris

# Chapter 5 :: Topics

- Introduction
- Arithmetic Circuits
- Number Systems
- Sequential Building Blocks
- Memory Arrays
- Logic Arrays

   
Application Software	<code>&gt;"hello world!"</code>
Operating Systems	
Architecture	
Micro-architecture	
Logic	
Digital Circuits	
Analog Circuits	
Devices	
Physics	

# Introduction

- **Digital building blocks:**
  - Gates, multiplexers, decoders, registers, arithmetic circuits, counters, memory arrays, logic arrays
- **Building blocks demonstrate hierarchy, modularity, and regularity:**
  - Hierarchy of simpler components
  - Well-defined interfaces and functions
  - Regular structure easily extends to different sizes
- **You can use these building blocks to build a processor (see Chapter 7, CpE 300)**

# Review: 1-Bit Adders

## Half Adder

 


A	B	$C_{out}$	S
0	0		
0	1		
1	0		
1	1		

$$S = A \oplus B$$

$$C_{out} = A \cdot B$$

## Full Adder

 


$C_{in}$	A	B	$C_{out}$	S
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

$$S = A \oplus B \oplus C_{in}$$

$$C_{out} = A \cdot B + (A \oplus B) \cdot C_{in}$$

# Review: 1-Bit Adders

## Half Adder

 


A	B	$C_{out}$	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$S = A \oplus B$$

$$C_{out} = A \cdot B$$

## Full Adder

 

$C_{in}$	A	B	$C_{out}$	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


$$S = A \oplus B \oplus C_{in}$$

$$C_{out} = (A \cdot B) \oplus (A \oplus B) \cdot C_{in}$$



# Review: 1-Bit Adders

## Half Adder

 


A	B	C <sub>out</sub>	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$S = A \oplus B$$

$$C_{out} = AB$$

## Full Adder

 


C <sub>in</sub>	A	B	C <sub>out</sub>	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S = A \oplus B \oplus C_{in}$$

$$C_{out} = AB + AC_{in} + BC_{in}$$

 
# Multibit Adders (CPAs)

- Types of carry propagate adders (CPAs):
  - Ripple-carry (slow)
  - Carry-lookahead (fast)
  - Prefix (faster) – see book
- Carry-lookahead and prefix adders faster for large adders but require more hardware


 
# Ripple-Carry Adder

- Chain 1-bit adders together
- Carry ripples through entire chain
- Disadvantage: **slow**



# Ripple-Carry Adder Delay

$$t_{\text{ripple}} = Nt_{FA}$$

where  $t_{FA}$  is the delay of a 1-bit full adder

# Carry-Lookahead Adder

- **Some definitions:**
  - Column  $i$  produces a carry out by either **generating** a carry out or **propagating** a carry in to the carry out

# Carry-Lookahead Adder

- **Some definitions:**
  - Column  $i$  produces a carry out by either **generating** a carry out or **propagating** a carry in to the carry out
  - Generate ( $G_i$ ) and propagate ( $P_i$ ) signals for each column:
    - **Generate:** Column  $i$  will generate a carry out if  $A_i$  AND  $B_i$  are both 1.

$$G_i = A_i B_i$$

# Carry-Lookahead Adder

- **Some definitions:**

- Column  $i$  produces a carry out by either **generating** a carry out or **propagating** a carry in to the carry out
- Generate ( $G_i$ ) and propagate ( $P_i$ ) signals for each column:
  - **Generate:** Column  $i$  will generate a carry out if  $A_i$  AND  $B_i$  are both 1.

$$G_i = A_i B_i$$

- **Propagate:** Column  $i$  will propagate a carry in to the carry out if  $A_i$  OR  $B_i$  is 1.

$$P_i = A_i + B_i$$

# Carry-Lookahead Adder

- **Some definitions:**

- Column  $i$  produces a carry out by either **generating** a carry out or **propagating** a carry in to the carry out
- Generate ( $G_i$ ) and propagate ( $P_i$ ) signals for each column:
  - **Generate:** Column  $i$  will generate a carry out if  $A_i$  AND  $B_i$  are both 1.

$$G_i = A_i B_i$$

- **Propagate:** Column  $i$  will propagate a carry in to the carry out if  $A_i$  OR  $B_i$  is 1.

$$P_i = A_i + B_i$$

- **Carry out:** The carry out of column  $i$  ( $C_i$ ) is:

$$C_i = G_i + P_i C_{i-1}$$

# Carry-Lookahead Adder

- **Some definitions:**

- Column  $i$  produces a carry out by either **generating** a carry out or **propagating** a carry in to the carry out
- Generate ( $G_i$ ) and propagate ( $P_i$ ) signals for each column:
  - **Generate:** Column  $i$  will generate a carry out if  $A_i$  AND  $B_i$  are both 1.

$$G_i = A_i B_i$$

- **Propagate:** Column  $i$  will propagate a carry in to the carry out if  $A_i$  OR  $B_i$  is 1.

$$P_i = A_i + B_i$$

- **Carry out:** The carry out of column  $i$  ( $C_i$ ) is:

$$C_i = G_i + P_i C_{i-1} = A_i B_i + (A_i + B_i) C_{i-1}$$

# Carry-Lookahead Adder

Compute carry out ( $C_{out}$ ) for ***k*-bit blocks** using *generate* and *propagate* signals

# Carry-Lookahead Adder

- **Example:** 4-bit blocks:

# Carry-Lookahead Adder

- **Example:** 4-bit blocks:

**Propagate:**  $P_{3:0} = P_3 P_2 P_1 P_0$

- All columns must propagate

**Generate:**  $G_{3:0} = G_3 + P_3 (G_2 + P_2 (G_1 + P_1 G_0))$

- Most significant bit generates or lower bit propagates a generated carry

# Carry-Lookahead Adder

- **Example:** 4-bit blocks:

**Propagate:**  $P_{3:0} = P_3 P_2 P_1 P_0$

- All columns must propagate

**Generate:**  $G_{3:0} = G_3 + P_3 (G_2 + P_2 (G_1 + P_1 G_0))$

- Most significant bit generates or lower bit propagates a generated carry
- **Generally,**

$$P_{i:j} = P_i P_{i-1} P_{i-2} \dots P_j$$

$$G_{i:j} = G_i + P_i (G_{i-1} + P_{i-1} (G_{i-2} + P_{i-2} G_j))$$


$$C_i = G_{i:j} + P_{i:j} C_{j-1}$$

# Carry-Lookahead Addition

- **Step 1:** Compute  $G_i$  and  $P_i$  for all columns
- **Step 2:** Compute  $G$  and  $P$  for  $k$ -bit blocks
- **Step 3:**  $C_{in}$  propagates through each  $k$ -bit propagate/generate block


 
# Ripple-Carry Adder

- Chain 1-bit adders together
- Carry ripples through entire chain
- Disadvantage: **slow**



$$t_{\text{ripple}} = Nt_{FA}$$

# 32-bit CLA with 4-bit Blocks

  

$$t_{CLA} = t_{pg} + t_{pg\_block} + (N/k - 1)t_{AND\_OR} + kt_{FA}$$



# Carry-Lookahead Adder Delay

For  $N$ -bit CLA with  $k$ -bit blocks:

$$t_{CLA} = t_{pg} + t_{pg\_block} + (N/k - 1)t_{AND\_OR} + kt_{FA}$$

- $t_{pg}$  : delay to generate all  $P_i, G_i$
- $t_{pg\_block}$  : delay to generate all  $P_{i:j}, G_{i:j}$
- $t_{AND\_OR}$  : delay from  $C_{in}$  to  $C_{out}$  of final AND/OR gate in  $k$ -bit CLA block

An  $N$ -bit carry-lookahead adder is generally much faster than a ripple-carry adder for  $N > 16$

# Adder Delay Comparisons


Compare delay of 32-bit ripple-carry and carry-lookahead adders

- CLA has 4-bit blocks
- 2-input gate delay = 100 ps; full adder delay = 300 ps
- Ripple
  - $t_{ripple} = Nt_{FA} = 32(300) = 9.6 \text{ ns}$
- Carry-lookahead
  - $t_{CLA} = t_{pg} + t_{pg\_block} + (N/k - 1)t_{AND\_OR} + k t_{FA}$
  - $t_{CLA} = 100 + 600 + 7(200) + 4(300) = 3.3 \text{ ns}$


AND/OR      6 Gates      3 Gates for  
for  $G_{3:0}$        $C_{in} \rightarrow C_{out}$

# Subtractor

## Symbol

 


## Implementation

 


# Comparator: Equality

## Symbol

 


## Implementation

 

# Counters

- Increments on each clock edge
- Used to cycle through numbers. For example,
  - 000, 001, 010, 011, 100, 101, 110, 111, 000, 001...
- Example uses:
  - Digital clock displays
  - Program counter: keeps track of current instruction executing


## Symbol

 


# Counters

- Increments on each clock edge
- Used to cycle through numbers. For example,
  - 000, 001, 010, 011, 100, 101, 110, 111, 000, 001...
- Example uses:
  - Digital clock displays
  - Program counter: keeps track of current instruction executing

## Symbol

 


## Implementation

 

# Shift Registers

- Shift a new bit in on each clock edge
- Shift a bit out on each clock edge
- *Serial-to-parallel converter*: converts serial input ( $S_{in}$ ) to parallel output ( $Q_{0:N-1}$ )


**Symbol:**

 

# Shift Registers

- Shift a new bit in on each clock edge
- Shift a bit out on each clock edge
- *Serial-to-parallel converter*: converts serial input ( $S_{in}$ ) to parallel output ( $Q_{0:N-1}$ )

## Symbol:

 

## Implementation:

