

#### Chapter 1

Professor Brendan Morris, SEB 3216, <a href="mailto:brendan.morris@unlv.edu">brendan.morris@unlv.edu</a> <a href="http://www.ee.unlv.edu/~b1morris/cpe100/">http://www.ee.unlv.edu/~b1morris/cpe100/</a>

#### **CPE100: Digital Logic Design I**

From Zero to One





#### Background: Digital Logic Design


- How have digital devices changed the world?
- How have digital devices changed your life?




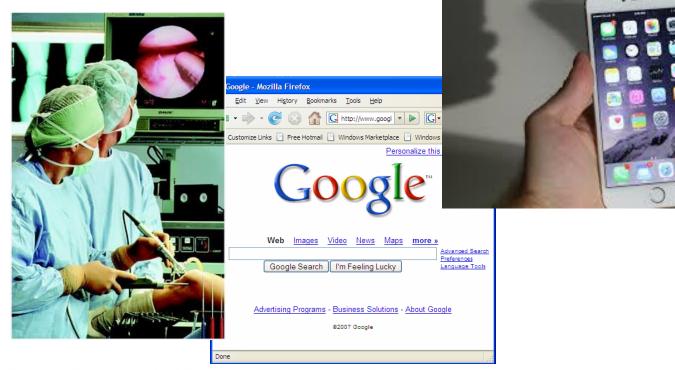
#### Background

- Digital Devices have revolutionized our world
  - Internet, cell phones, rapid advances in medicine, etc.
- The semiconductor industry has grown from \$21 billion in 1985 to over \$300 billion in 2015





#### The Game Plan

- Purpose of course:
  - Learn the principles of digital design
  - Learn to systematically debug increasingly complex designs



# ONE S

#### Chapter 1: Topics

- The Art of Managing Complexity
- The Digital Abstraction
- Number Systems
- Addition
- Binary Codes
- Signed Numbers
- Logic Gates
- Logic Levels
- CMOS Transistors
- Power Consumption





### The Art of Managing Complexity

- Abstraction
- Discipline
- The Three –y's
  - Hierarchy
  - Modularity
  - Regularity





#### Abstraction

- What is abstraction?
  - Hiding details when they are not important

- Electronic computer abstraction
  - Different levels with different building blocks

Application >"hello programs Software world!" Operating device drivers Systems instructions Architecture registers datapaths Microcontrollers architecture adders Logic memories **AND** gates Digital Circuits **NOT** gates Analog amplifiers Circuits filters transistors **Devices** diodes **Physics** electrons

course

focus of this



#### Discipline

- Intentionally restrict design choices
- Example: Digital discipline
  - Discrete voltages (0 V, 5 V) instead of continuous (0V – 5V)
  - Simpler to design than analog circuits can build more sophisticated systems
  - Digital systems replacing analog predecessors:
    - i.e., digital cameras, digital television, cell phones, CDs





#### The Three -y's

- Hierarchy
  - A system divided into modules and submodules

- Modularity
  - Having well-defined functions and interfaces


- Regularity
  - Encouraging uniformity, so modules can be easily reused




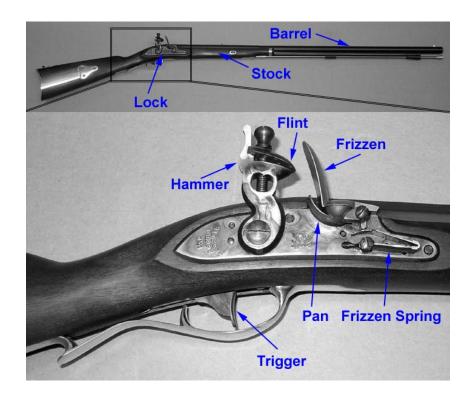
#### Example: Flintlock Rifle

- Hierarchy
  - Three main modules: Lock, stock, and barrel
  - Submodules of lock: Hammer, flint, frizzen, etc.






## ONE RON

#### Example Flintlock Rifle

- Modularity
  - Function of stock: mount barrel and lock
  - Interface of stock: length and location of mounting pins

- Regularity
  - Interchangeable parts

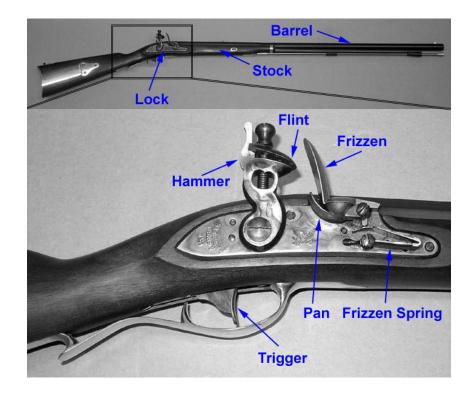





### The Art of Managing Complexity

- Abstraction
- Discipline
- The Three –y's
  - Hierarchy
  - Modularity
  - Regularity





#### The Digital Abstraction

- Most physical variables are continuous
  - Voltage on a wire (1.33 V, 9 V, 12.2 V)
  - Frequency of an oscillation (60 Hz, 33.3 Hz, 44.1 kHz)
  - Position of mass (0.25 m, 3.2 m)
- Digital abstraction considers discrete subset of values
  - 0 V, 5 V
  - "0", "1"





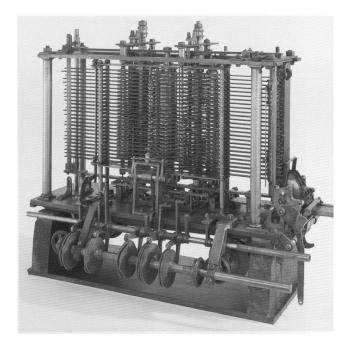
#### The Analytical Engine

- Designed by Charles
   Babbage from 1834 –

   1871
- Considered to be the first digital computer
- Built from mechanical gears, where each gear represented a discrete value (0-9)
- Babbage died before it was finished







Chapter 1 <14>



#### Digital Discipline: Binary Values

- Two discrete values
  - 1 and 0
    - 1 = TRUE = HIGH = ON
    - 0 = FALSE = LOW = OFF
- How to represent 1 and 0
  - Voltage levels, rotating gears, fluid levels, etc.
- Digital circuits use voltage levels to represent
   1 and 0
  - Bit = binary digit
    - Represents the status of a digital signal (2 values)





#### Why Digital Systems?


- Easier to design
- Fast
- Can overcome noise
- Error detection/correction




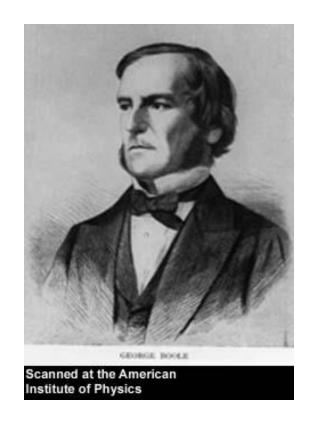
#### George Boole, 1815-1864

- Born to working class parents
- Taught himself mathematics and joined the faculty of Queen's College in Ireland
- Wrote An Investigation of the Laws of Thought (1854)
- Introduced binary variables
- Introduced the three fundamental logic operations: AND, OR, and NOT





# ONE

#### Number Systems

- Decimal
  - Base 10
- Binary
  - Base 2
- Hexadecimal
  - Base 16






#### **Decimal Numbers**

Five

Base 10 (our everyday number system)

1's Column 10's Column 100's Column 1000's Column
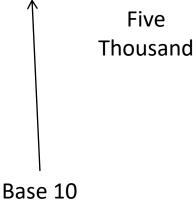
$$5374_{10} = 5 \times 10^3 + 3 \times 10^2 + 7 \times 10^1 + 4 \times 10^0$$



Three Hundred Seven Tens

Four Ones





#### **Binary Numbers**

Base 2 (computer number system)

$$1101_2 = 1 \times 2^3 + 1 \times 2^2 + 0 \times 2^1 + 1 \times 2^0$$

$$\uparrow \qquad \text{One} \qquad \text{One} \qquad \text{Two} \qquad \text{One}$$
Eight Four Two One



#### Powers of Two

• 
$$2^0 =$$

• 
$$2^1 =$$

• 
$$2^2 =$$

• 
$$2^3 =$$

• 
$$2^4 =$$

• 
$$2^5 =$$

• 
$$2^6 =$$

• 
$$2^7 =$$

• 
$$2^8 =$$

• 
$$2^9 =$$

• 
$$2^{10} =$$

• 
$$2^{11} =$$

• 
$$2^{12} =$$

• 
$$2^{13} =$$

• 
$$2^{14} =$$

• 
$$2^{15} =$$



#### Powers of Two

• 
$$2^0 = 1$$

• 
$$2^1 = 2$$

• 
$$2^2 = 4$$

• 
$$2^3 = 8$$

• 
$$2^4 = 16$$

• 
$$2^5 = 32$$

• 
$$2^6 = 64$$

• 
$$2^7 = 128$$

• 
$$2^8 = 256$$

• 
$$2^9 = 512$$

• 
$$2^{10} = 1024$$

• 
$$2^{11} = 2048$$

• 
$$2^{12} = 4096$$

• 
$$2^{13} = 8192$$

• 
$$2^{14} = 16384$$

• 
$$2^{15} = 32768$$

Handy to memorize up to 2<sup>10</sup>



### ONE 20

### Bits, Bytes, Nibbles ...

Bits

- Bytes = 8 bits
- Nibble = 4 bits

10010110
most least significant bit bit

10010110

- Words = 32 bits
  - Hex digit to represent nibble

CEBF9AD7

most significant byte

least significant byte





#### Decimal to Binary Conversion

Two Methods:

 Method 1: Find largest power of 2 that fits, subtract and repeat

 Method 2: Repeatedly divide by 2, remainder goes in next most significant bit





 Find largest power of 2 that fits, subtract, repeat

53<sub>10</sub>





 Find largest power of 2 that fits, subtract, repeat

$$53_{10}$$
  $32 \times 1$   
 $53-32 = 21$   $16 \times 1$   
 $21-16 = 5$   $4 \times 1$   
 $5-4 = 1$   $1 \times 1$ 

$$= 110101_2$$





 Repeatedly divide by 2, remainder goes in next most significant bit

$$53_{10} =$$





 Repeatedly divide by 2, remainder goes in next most significant bit

$$53_{10} = 53/2 = 26 \text{ R1}$$
 $26/2 = 13 \text{ R0}$ 
 $13/2 = 6 \text{ R1}$ 
 $6/2 = 3 \text{ R0}$ 
 $3/2 = 1 \text{ R1}$ 
 $1/2 = 0 \text{ R1}$ 
MSB



 $= 110101_2$ 



#### Number Conversion

- Binary to decimal conversion
  - Convert 10011<sub>2</sub> to decimal

$$16 \times 1 + 8 \times 0 + 4 \times 0 + 2 \times 1 + 1 \times 1 = 19_{10}$$

- Decimal to binary conversion
  - Convert 47<sub>10</sub> to binary

$$32 \times 1 + 16 \times 0 + 8 \times 1 + 4 \times 1 + 2 \times 1 + 1 \times 1 = 1011111_2$$





#### D2B Example

• Convert 75<sub>10</sub> to binary





Sign

#### D2B Example

Convert 75<sub>10</sub> to binary

$$75_{10} = 64 + 8 + 2 + 1 = 1001011_2$$

• Or 75/2 = 37 R1

37/2 = 18 R1

18/2 = 9 R0

9/2 = 4 R1

4/2 = 2 R0

2/2 = 1 R0

1/2 = 0 R1





- N-digit decimal number
  - How many values?
  - Range?

- Example:3-digit decimal number
  - Possible values
  - Range





- N-digit decimal number
  - How many values?
    - 10<sup>N</sup>
  - Range?
    - $[0, 10^N 1]$
- Example: 3-digit decimal number
  - Possible values
    - $10^3 = 1000$
  - Range
    - [0,999]





- N-bit binary number
  - How many values?
  - Range?

- Example: 3-bit binary number
  - Possible values
  - Range





- N-bit binary number
  - How many values?
    - 2<sup>N</sup>
  - Range?
    - $[0, 2^N 1]$
- Example:3-bit binary number
  - Possible values

• 
$$2^3 = 8$$

- Range
  - $[0,7] = [000_2, 111_2]$





- N-digit decimal number
  - How many values?
    - 10<sup>N</sup>
  - Range?
    - $[0, 10^N 1]$
- Example:3-digit decimal number
  - Possible values
    - $10^3 = 1000$
  - Range
    - [0,999]

- N-bit binary number
  - How many values?
    - 2<sup>N</sup>
  - Range?
    - $[0, 2^N 1]$
- Example: 3-bit binary number
  - Possible values

• 
$$2^3 = 8$$

- Range
  - $[0,7] = [000_2, 111_2]$





# Hexadecimal Numbers

Base 16 number system

- Shorthand for binary
  - Four binary digits (4-bit binary number) is a single hex digit



# ONE

### **Hexadecimal Numbers**

Hex Digit	Decimal Equivalent	Binary Equivalent
0	0	
1	1	
2	2	
3	3	
4	4	
5	5	
6	6	
7	7	
8	8	
9	9	
A	10	
В	11	
С	12	
D	13	
Е	14	
F	15	



# Hexadecimal Numbers

Hex Digit	Decimal Equivalent	Binary Equivalent
0	0	0000
1	1	0001
2	2	0010
3	3	0011
4	4	0100
5	5	0101
6	6	0110
7	7	0111
8	8	1000
9	9	1001
A	10	1010
В	11	1011
С	12	1100
D	13	1101
Е	14	1110
F	15	1111





# Hexadecimal to Binary Conversion

- Hexadecimal to binary conversion:
  - Convert 4AF<sub>16</sub> (also written 0x4AF) to binary

- Hexadecimal to decimal conversion:
  - Convert 0x4AF to decimal





# Hexadecimal to Binary Conversion

- Hexadecimal to binary conversion:
  - Convert 4AF<sub>16</sub> (also written 0x4AF) to binary
    - $0x4AF = 0100\ 1010\ 11111_2$

- Hexadecimal to decimal conversion:
  - Convert 0x4AF to decimal
    - $4 \times 16^2 + 10 \times 16^1 + 15 \times 16^0 = 1199_{10}$





# Number Systems

- Popular
  - Decimal Base 10
  - Binary Base 2
  - Hexadecimal Base 16

- Others
  - Octal Base 8
  - Any other base





### **Octal Numbers**

Same as hex with one less binary digit

Octal Digit	Decimal Equivalent	Binary Equivalent
0	0	000
1	1	001
2	2	010
3	3	011
4	4	100
5	5	101
6	6	110
7	7	111





# Number Systems

• In general, an N-digit number  $\{a_{N-1}a_{N-2}\dots a_1a_0\}$  of base R in decimal equals

• 
$$a_{N-1}R^{N-1} + a_{N-2}R^{N-2} + \dots + a_1R^1 + a_0R^0$$

• Example: 4-digit  $\{5173\}$  of base 8 (octal)





# Number Systems

• In general, an N-digit number  $\{a_{N-1}a_{N-2}\dots a_1a_0\}$  of base R in decimal equals

• 
$$a_{N-1}R^{N-1} + a_{N-2}R^{N-2} + \dots + a_1R^1 + a_0R^0$$

- Example: 4-digit {5173} of base 8 (octal)
  - $5 \times 8^3 + 1 \times 8^2 + 7 \times 8^1 + 3 \times 8^0 = 2683_{10}$





# Decimal to Octal Conversion

- Remember two methods for D2B conversion
  - 1: remove largest multiple; 2: repeated divide
- Convert 29<sub>10</sub> to octal





### Decimal to Octal Conversion

- Remember two methods for D2B conversion
  - 1: remove largest multiple; 2: repeated divide
- Convert 29<sub>10</sub> to octal
- Method 2

$$29_{10} = 35_8$$





# Decimal to Octal Conversion

- Remember two methods for D2B conversion
  - 1: remove largest multiple; 2: repeated divide
- Convert 29<sub>10</sub> to octal
- Method 1

$$29_{10} = 24 + 5 = 3 \times 8^1 + 5 \times 8^0 = 35_8$$

Or (better scalability)

$$29_{10} = 16 + 8 + 4 + 1 = 11101_2 = 35_8$$





# Octal to Decimal Conversion

Convert 163<sub>8</sub> to decimal





# Octal to Decimal Conversion

Convert 163<sub>8</sub> to decimal

• 
$$163_8 = 1 \times 8^2 + 6 \times 8^1 + 3$$

• 
$$163_8 = 64 + 48 + 3$$

• 
$$163_8 = 115_{10}$$





# Recap: Binary and Hex Numbers

• Example 1: Convert 83<sub>10</sub> to hex

Example 2: Convert 01101011<sub>2</sub> to hex and decimal

Example 3: Convert 0xCA3 to binary and decimal



# Recap: Binary and Hex Numbers

- Example 1: Convert 83<sub>10</sub> to hex
  - $83_{10} = 64 + 16 + 2 + 1 = 1010011_2$
  - $1010011_2 = 1010011_2 = 53_{16}$
- Example 2: Convert 01101011<sub>2</sub> to hex and decimal
  - $01101011_2 = 0110 \ 1011_2 = 6B_{16}$
  - $0x6B = 6 \times 16^1 + 11 \times 16^0 = 96 + 11 = 107$
- Example 3: Convert 0xCA3 to binary and decimal
  - $0xCA3 = 1100\ 1010\ 0011_2$
  - $0xCA3 = 12 \times 16^2 + 10 \times 16^1 + 3 \times 16^0 = 3235_{10}$



# Large Powers of Two

- $2^{10} = 1 \text{ kilo}$   $\approx 1000 (1024)$
- $2^{20} = 1 \text{ mega} \approx 1 \text{ million } (1,048,576)$
- $2^{30} = 1$  giga  $\approx 1$  billion (1,073,741,824)
- $2^{40} = 1 \text{ tera}$   $\approx 1 \text{ trillion } (1,099,511,627,776)$



# NE NO

# Large Powers of Two: Abbreviations

•  $2^{10} = 1 \text{ kilo}$   $\approx 1000 (1024)$ 

**for example:** 1 kB = 1024 Bytes

1 kb = 1024 bits

•  $2^{20} = 1 \text{ mega} \approx 1 \text{ million } (1,048,576)$ 

for example: 1 MiB, 1 Mib (1 megabit)

•  $2^{30} = 1$  giga  $\approx 1$  billion (1,073,741,824)

for example: 1 GiB, 1 Gib



# **Estimating Powers of Two**

What is the value of 2<sup>24</sup>?

 How many values can a 32-bit variable represent?





# **Estimating Powers of Two**

- What is the value of 2<sup>24</sup>?
  - $2^4 \times 2^{20} \approx 16$  million

- How many values can a 32-bit variable represent?
  - $2^2 \times 2^{30} \approx 4$  billion





# **Binary Codes**

Another way of representing decimal numbers in binary

### **Example binary codes:**

- Weighted codes
  - Binary Coded Decimal (BCD) (8-4-2-1 code)
  - 6-3-1-1 code
  - 8-4-2-1 code (simple binary)
- Gray codes
- Excess-3 code
- 2-out-of-5 code



# **ASCII-Code**

TABLE 1-3 ASCII Code
----------------------

TABLE 1-3	AS	CII	Coc	le																				
			ASC	III C	ode	9					ASC	III C	ode					-	ASC	II Co	ode			
Character	$A_6$	A <sub>5</sub>	$A_4$	$A_3$	$A_2$	A <sub>1</sub>	$A_0$	Character	$A_6$	$A_5$	$A_4$	$A_3$	$A_2$	$A_1$	$A_0$	Character	$A_6$	$A_5$	$A_4$	A <sub>3</sub>	$A_2$	$A_1$	A <sub>0</sub>	
space	0	1	0	0	0	0	0	@	1	0	0	0	0	0	0	,	1	1	0	0	0	0	0	
1	0	1	0	0	0	0	1	Α	1	0	0	0	0	0	1	a	1	1	0	0	0	0	1	
"	0	1	0	0	0	1	0	В	1	0	0	0	0	1	0	b	1	1	0	0	0	1	0	
#	0	1	0	0	0	1	1	C	1	0	0	0	0	1	1	c	1	1	0	0	0	1	1	
\$	0	1	0	0	1	0	0	D	1	0	0	0	1	0	0	d	1	1	0	0	1	0	0	
%	0	1	0	0	1	0	1	E	1	0	0	0	1	0	1	e	1	1	0	0	1	0	1	
&	0	1	0	0	1	1	0	F	1	0	0	0	1	1	0	f	1	1	0	0	1	1	0	
,	0	1	0	0	1	1	1	G	1	0	0	0	1	1	1	g	1	1	0	0	1	1	1	
(	0	1	0	1	0	0	0	н	1	0	0	1	0	0	0	h	1	1	0	1	0	0	0	
)	0	1	0	1	0	0	1	1	1	0	0	1	0	0	1	i	1	1	0	1	0	0	1	
*	0	1	0	1	0	1	0	J	1	0	0	1	0	1	0	j	1	1	0	1	0	1	0	
+	0	1	0	1	0	1	1	K	1	0	0	1	0	1	1	k	1	1	0	1	0	1	1	
	0	1	0	1	1	0	0	L	1	0	0	1	1	0	0		1	1	0	1	1	0	0	
-	0	1	0	1	1	0	1	M	1	0	0	1	1	0	1	m	1	1	0	1	1	0	1	
	0	1	0	1	1	1	0	N	1	0	0	1	1	1	0	n	1	1	0	1	1	1	0	
/	0	1	0	1	1	1	1	0	1	0	0	1	1	1	1	0	1	1	0	1	1	1	1	
0	0	1	1	0	0	0	0	P	1	0	1	0	0	0	0	р	1	1	1	0	0	0	0	
1	0	1	1	0	0	0	1	Q	1	0	1	0	0	0	1	q	1	1	1	0	0	0	1	
2	0	1	1	0	0	1	0	R	1	0	1	0	0	1	0	r	1	1	1	0	0	1	0	
3	0	1	1	0	0	1	1	S	1	0	1	0	0	1	1	S	1	1	1	0	0	1	1	
4	0	1	1	0	1	0	0	Т	1	0	1	0	1	0	0	t	1	1	1	0	1	0	0	
5	0	1	1	0	1	0	1	U	1	0	1	0	1	0	1	u	1	1	1	0	1	0	1	
6	0	1	1	0	1	1	0	V	1	0	1	0	1	1	0	v	1	1	1	0	1	1	0	
7	0	1	1	0	1	1	1	W	1	0	1	0	1	1	1	w	1	1	1	0	1	1	1	
8	0	1	1	1	0	0	0	X	1	0	1	1	0	0	0	X	1	1	1	1	0	0	0	4
9	0	1	1	1	0	0	1	Y	1	0	1	1	0	0	1	у	1	1	1	1	0	0	1	2
:	0	1	1	1	0	1	0	Z	1	0	1	1	0	1	0	z	1	1	1	1	0	1	0	ing
;	0	1	1	1	0	1	1	Į.	1	0	1	1	0	1	1	{	1	1	1	1	0	1	1	earr
<	0	1	1	1	1	0	0	<u>`</u>	1	0	1	1	1	0	0	Į	1	1	1	1	1	0	0	Cengage Learning 2014
=	0	1	1	1	1	0	1	J	1	0	1	1	1	0	1	}	1	1	1	1	1	0	1	nga
>	0	1	1	1	1	1	0	۸	1	0	1	1	1	1	0	~	1	1	1	1	1	1	0	ق
?	0	1	1	1	1	1	1	_	1	0	1	1	1	1	1	delete	1	1	1	1	1	1	1	0





# Binary Codes

Decimal #	8-4-2-1 (BCD)	6-3-1-1	Excess-3	2-out-of-5	Gray		
0	0000	0000	0011	00011	0000		
1	0001	0001	0100	00101	0001		
2	0010	0011	0101	00110	0011		
3	0011	0100	0110	01001	0010		
4	0100	0101	0111	01010	0110		
5	0101	0111	1000	01100	1110		
6	0110	1000	1001	10001	1010		
7	0111	1001	1010	10010	1011		
8	1000	1011	1011	10100	1001		
9	1001	1100	1100	11000	1000		

Each code combination represents a single decimal digit.





# **Gray Codes**

Decimal #	Gray
0	0000
1	0001
2	0011
3	0010
4	0110
5	1110
6	1010
7	1011
8	1001
9	1000

- Next number differs in only one bit position
  - Example: 000, 001, 011, 010, 110, 111, 101, 100
- Example use: Analog-to-Digital (A/D) converters. Changing 2 bits at a time (i.e., 011 →100) could cause large inaccuracies.
- Will use in K-maps





# Addition

Decimal

Binary



# ONE Sio

# Addition

Decimal

Binary



# ONE Sio

# Addition

Decimal

Binary





# Binary Addition Examples

 Add the following 4-bit binary numbers

 Add the following 4-bit binary numbers





# Binary Addition Examples

Add the following 4-bit binary numbers

 Add the following 4-bit binary numbers



# ONE RON

# Binary Addition Examples

 Add the following 4-bit binary numbers

 Add the following 4-bit binary numbers

Overflow!





### Overflow

- Digital systems operate on a fixed number of bits
- Overflow: when result is too big to fit in the available number of bits
- See previous example of 11 + 6





# Signed Binary Numbers

- Sign/Magnitude Numbers
- Two's Complement Numbers



# ONE Sign

# Sign/Magnitude

- 1 sign bit, *N*-1 magnitude bits
- Sign bit is the most significant (left-most) bit
  - **Positive number:** sign bit = 0
  - Negative number: sign bit = 1

$$A:\{a_{N-1},a_{N-2},\cdots a_2,a_1,a_0\}$$

$$A = (-1)^{a_{n-1}} \sum_{i=0}^{n-2} a_i 2^i$$

- Example, 4-bit sign/magnitude representations of  $\pm$  6:
  - +6=
  - **-**6 =
- Range of an *N*-bit sign/magnitude number:



# ONE Sio

# Sign/Magnitude

- 1 sign bit, *N*-1 magnitude bits
- Sign bit is the most significant (left-most) bit
  - **Positive number:** sign bit = 0
  - Negative number: sign bit = 1

$$A:\{a_{N-1},a_{N-2},\cdots a_2,a_1,a_0\}$$

$$A = (-1)^{a_{n-1}} \sum_{i=0}^{n-2} a_i 2^i$$

- Example, 4-bit sign/magnitude representations of  $\pm$  6:
  - +6 = 0110
  - -6 = **1110**
- Range of an *N*-bit sign/magnitude number:
  - $[-(2^{N-1}-1), 2^{N-1}-1]$





# Sign/Magnitude Numbers

- Problems:
  - Addition doesn't work, for example -6 + 6:

$$+0110$$

• Two representations of  $0 (\pm 0)$ :

• 
$$(+0) =$$

• 
$$(-0) =$$





# Sign/Magnitude Numbers

- Problems:
  - Addition doesn't work, for example -6 + 6:

$$+0110$$

- Two representations of  $0 (\pm 0)$ :
  - (+0) = 0000
  - (-0) = 1000





# Two's Complement Numbers

- Don't have same problems as sign/magnitude numbers:
  - Addition works
  - Single representation for 0

- Range of representable numbers not symmetric
  - One extra negative number





# Two's Complement Numbers

• msb has value of  $-2^{N-1}$ 

$$A = a_{n-1} \left( -2^{n-1} \right) + \sum_{i=0}^{n-2} a_i 2^i$$

- The most significant bit still indicates the sign (1 = negative, 0 = positive)
- Range of an *N*-bit two's comp number?

- Most positive 4-bit number?
- Most negative 4-bit number?





# Two's Complement Numbers

• msb has value of  $-2^{N-1}$ 

$$A = a_{n-1} \left( -2^{n-1} \right) + \sum_{i=0}^{n-2} a_i 2^i$$

- The most significant bit still indicates the sign (1 = negative, 0 = positive)
- Range of an *N*-bit two's comp number?

• 
$$[-(2^{N-1}), 2^{N-1} - 1]$$

- Most positive 4-bit number? 0111
- Most negative 4-bit number? 1000





# "Taking the Two's Complement"

- Flips the sign of a two's complement number
- Method:
  - 1. Invert the bits
  - 2. Add 1
- Example: Flip the sign of  $3_{10} = 0011_2$





# "Taking the Two's Complement"

- Flips the sign of a two's complement number
- Method:
  - 1. Invert the bits
  - 2. Add 1
- Example: Flip the sign of  $3_{10} = 0011_2$ 
  - 1. 1100

$$2. \ \ \frac{+ \ 1}{1101 = -3_{10}}$$





# Two's Complement Examples

• Take the two's complement of  $6_{10} = 0110_2$ 

• What is the decimal value of the two's complement number 1001<sub>2</sub>?





# Two's Complement Examples

- Take the two's complement of  $6_{10} = 0110_2$ 
  - 1. 1001

$$2. \ \ \frac{+ \ \ 1}{1010_2} = -6_{10}$$

- What is the decimal value of the two's complement number 1001<sub>2</sub>?
  - 1. 0110

2. 
$$\frac{+}{0111_2} = 7_{10}$$
, so  $1001_2 = -7_{10}$ 





# Two's Complement Addition

• Add 6 + (-6) using two's complement numbers

• Add -2 + 3 using two's complement numbers





# Two's Complement Addition

• Add 6 + (-6) using two's complement numbers

• Add -2 + 3 using two's complement numbers





# Two's Complement Addition

• Add 6 + (-6) using two's complement numbers

• Add -2 + 3 using two's complement numbers





# Increasing Bit Width

- Extend number from N to M bits (M > N):
  - Sign-extension
  - Zero-extension





# Sign-Extension

- Sign bit copied to msb's
- Number value is same

- Example 1
  - 4-bit representation of 3 = 0011
  - 8-bit sign-extended value:
- Example 2
  - 4-bit representation of -7 = 1001
  - 8-bit sign-extended value:





# Sign-Extension

- Sign bit copied to msb's
- Number value is same

- Example 1
  - 4-bit representation of 3 = 0011
  - 8-bit sign-extended value: 00000011
- Example 2
  - 4-bit representation of -7 = 1001
  - 8-bit sign-extended value: 11111001





#### Zero-Extension

- Zeros copied to msb's
- Value changes for negative numbers

- Example 1
  - 4-bit value =

0011<sub>2</sub>

- 8-bit zero-extended value:
- Example 2
  - 4-bit value =

1001

8-bit zero-extended value:





#### Zero-Extension

- Zeros copied to msb's
- Value changes for negative numbers

Example 1

4-bit value =

00112

- 8-bit zero-extended value: 00000011
- Example 2
  - 4-bit value =

1001

• 8-bit zero-extended value: 00001001



# NE

#### Zero-Extension

- Zeros copied to msb's
- Value changes for negative numbers

Example 1

$$0011_2 = 3_{10}$$

- 8-bit zero-extended value:  $00000011 = 3_{10}$
- Example 2

$$1001 = -7_{10}$$


• 8-bit zero-extended value:  $00001001 = 9_{10}$ 



### Number System Comparison

Number System	Range
Unsigned	$[0, 2^{N}-1]$
Sign/Magnitude	$[-(2^{N-1}-1), 2^{N-1}-1]$
Two's Complement	$[-2^{N-1}, 2^{N-1}-1]$

#### For example, 4-bit representation:

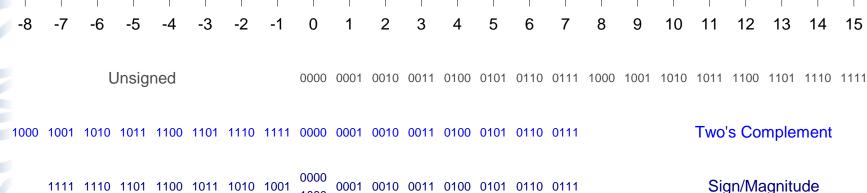






### Logic Gates

- Perform logic functions:
  - inversion (NOT), AND, OR, NAND, NOR, etc.
- Single-input:
  - NOT gate, buffer
- Two-input:
  - AND, OR, XOR, NAND, NOR, XNOR
- Multiple-input




# Single-Input Logic Gates

#### **NOT**

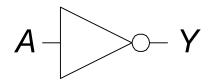

$$Y = \overline{A}$$

#### **BUF**

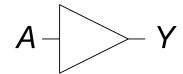


$$Y = A$$

Α	Y
0	
1	




# Single-Input Logic Gates

Bubble on wire indicates inversion

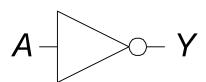

$$Y = \overline{A}$$

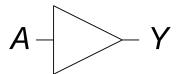

$$Y = A$$

A	Y
0	0
1	1

 Note: bar over variable indicates complement (invert value)

### Two-Input Logic Gates


#### **AND**



$$Y = AB$$

Α	В	Y
0	0	
0	1	
1	0	
1	1	

#### OR

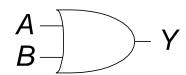

$$Y = A + B$$

A	В	Y
0	0	
0	1	
1	0	
1	1	



### Two-Input Logic Gates


#### **AND**



$$Y = AB$$

Α	В	Y
0	0	0
0	1	0
1	0	0
1	1	1

#### OR

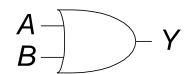


$$Y = A + B$$

_A	В	Y
0	0	0
0	1	1
1	0	1
1	1	1



### More Two-Input Logic Gates


#### **XOR**

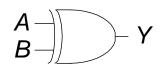

$$Y = A \oplus B$$

A	В	Y
0	0	
0	1	
1	0	
1	1	


#### **NAND**

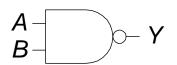

$$Y = \overline{AB}$$

Α	В	Υ
0	0	
0	1	
1	0	
1	1	


#### **NOR**

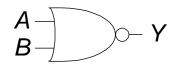

$$Y = \overline{A + B}$$

A	В	Y
0	0	
0	1	
1	0	
1	1	

#### **XNOR**

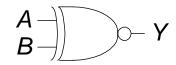


$$Y = \overline{A + B}$$

Α	В	Y
0	0	
0	1	
1	0	
1	1	



### More Two-Input Logic Gates


#### **XOR**

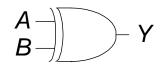

$$Y = A \oplus B$$

A	В	Υ
0	0	0
0	1	1
1	0	1
1	1	0


#### **NAND**

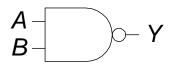

$$Y = \overline{AB}$$

Α	В	Υ
0	0	1
0	1	1
1	0	1
1	1	0


#### **NOR**

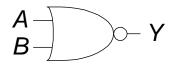

$$Y = \overline{A + B}$$

A	В	Y
0	0	1
0	1	0
1	0	0
1	1	0

#### **XNOR**

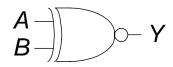

$$Y = \overline{A + B}$$


A	В	Y
0	0	1
0	1	0
1	0	0
1	1	1



# SE

# Multiple-Input Logic Gates


#### NOR<sub>3</sub>

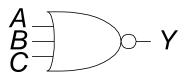

$$Y = \overline{A + B + C}$$

_A	В	С	Y
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

#### AND3

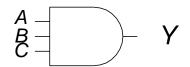


$$Y = ABC$$

A	В	С	Y
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	



### Multiple-Input Logic Gates


#### NOR3

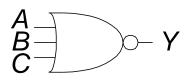

$$Y = \overline{A + B + C}$$

Α	В	С	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

#### AND3

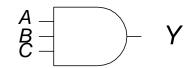

$$Y = ABC$$

Α	В	С	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

• Multi-input XOR = Odd parity (#on inputs odd → 1)





# Logic Levels

- Discrete voltages represent 1 and 0
- For example:
  - 0 = ground (GND) or 0 volts
  - 1 =  $V_{DD}$  or 5 volts
- What about 4.99 volts? Is that a 0 or a 1?
- What about 3.2 volts?





# Logic Levels

Must have range of voltages for 1 and 0

Different ranges for inputs and outputs to allow for noise






#### What is Noise?

- Anything that degrades the signal
  - E.g., resistance, power supply noise, coupling to neighboring wires, etc.

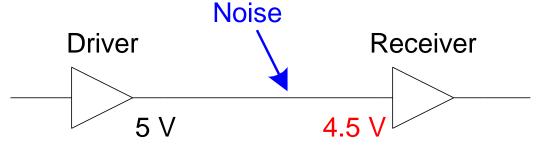 Example: a gate (driver) outputs 5 V but, because of resistance in a long wire, receiver gets 4.5 V







# The Static Discipline

 With logically valid inputs, every circuit element must produce logically valid outputs

Use limited ranges of voltages to represent discrete values






# Real Logic Levels



 Want driver to output "clean" high/low and receiver to handle noisy high/low


# ONE

# Real Logic Levels

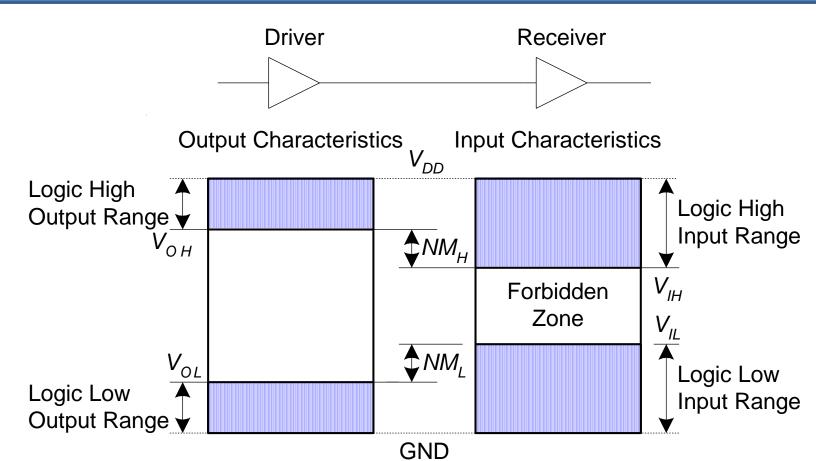

 Want driver to output "clean" high/low and receiver to handle noisy high/low

# Real Logic Levels

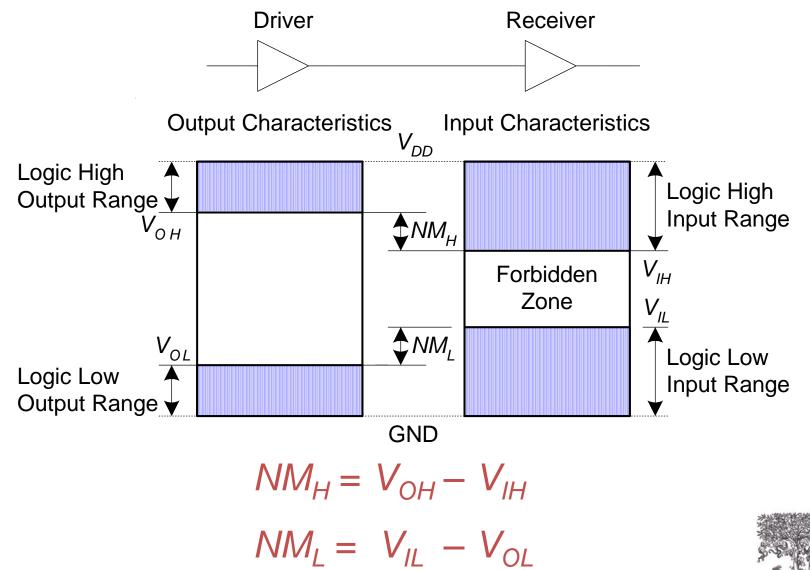





# V<sub>DD</sub> Scaling

- In 1970's and 1980's,  $V_{DD} = 5 \text{ V}$
- V<sub>DD</sub> has dropped
  - 3.3 V, 2.5 V, 1.8 V, 1.5 V, 1.2 V, 1.0 V, ...
  - Avoid frying tiny transistors
  - Save power

- Be careful connecting chips with different supply voltages
  - Easy to fry if not careful



# ONE

# Logic Family Examples


<b>Logic Family</b>	$V_{DD}$	$V_{IL}$	$V_{IH}$	$V_{OL}$	$V_{OH}$
TTL	5 (4.75 - 5.25)	0.8	2.0	0.4	2.4
CMOS	5 (4.5 - 6)	1.35	3.15	0.33	3.84
LVTTL	3.3 (3 - 3.6)	0.8	2.0	0.4	2.4
LVCMOS	3.3 (3 - 3.6)	0.9	1.8	0.36	2.7




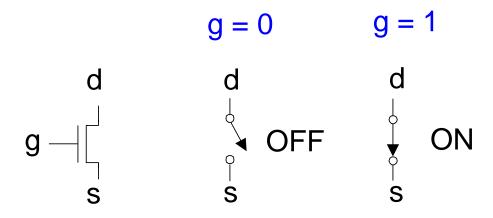
#### **Transistors**

- Logic gates built from transistors
- Simple model: 3-ported voltage-controlled switch
  - 2 ports connected depending on voltage of 3rd
  - d and s are connected (ON) when g is 1







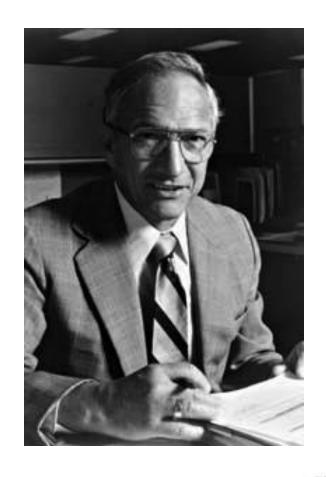
## Robert Noyce, 1927-1990


- Nicknamed "Mayor of Silicon Valley"
- Cofounded Fairchild Semiconductor in 1957
- Cofounded Intel in 1968
- Co-invented the integrated circuit




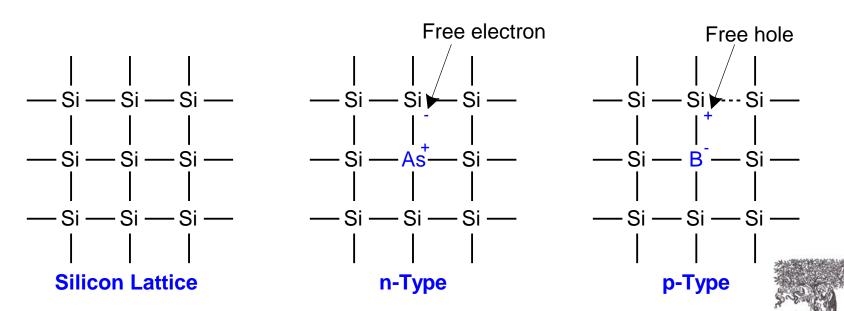
## Silicon


- Transistors built from silicon, a semiconductor
- Pure silicon is a poor conductor (no free charges)
- Doped silicon is a good conductor (free charges)
  - n-type (free negative charges, electrons)
  - p-type (free positive charges, holes)




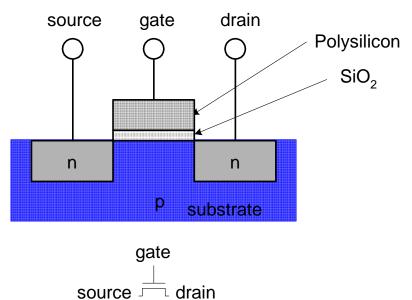
## **MOS Transistors**

- Metal oxide silicon (MOS) transistors:
  - Polysilicon (used to be metal) gate
  - Oxide (silicon dioxide) insulator
  - Doped silicon



nMOS



# ZE

## nMOS Transistors

- Gate = 0
- OFF (no connection between source and drain)
- source drain


  gate
  GND

  gate
  GND

Diode connection from p to n doped area

→ current cannot travel from n→p

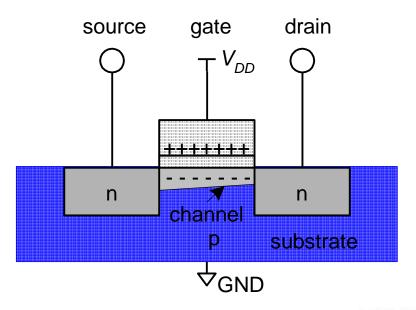- Gate = 1
- ON (channel between source and drain)







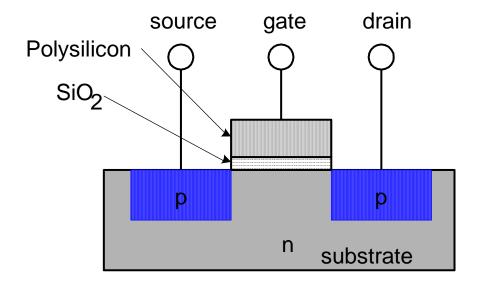
## pMOS Transistors

- pMOS transistor is opposite of nMOS
  - ON when Gate = 0
  - OFF when Gate = 1



Note bubble on gate to indicate on when low source drain



## **Transistor Function**

Voltage controlled switch



pMOS

$$g \longrightarrow \int_{d}$$


$$g = 0$$


$$0$$

$$0$$

$$0$$

$$0$$

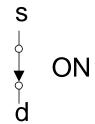

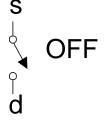






## **Transistor Composition**

- nMOS: pass good 0's
  - Connect source to GND
  - "Pull down" transistor

- pMOS: pass good 1's
  - Connect source to VDD
  - "Pull up" transistor

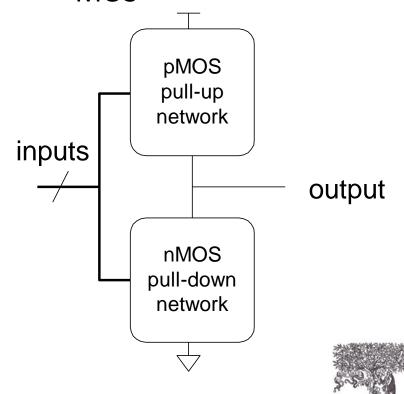- Build logic gates from composition
  - CMOS = complementary MOS




# ONE
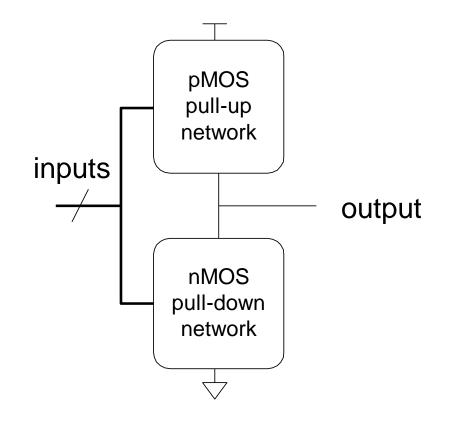
## **CMOS Gate Structure**

- Pull-up pMOS network connects to  $V_{DD}$
- Pull-down nMOS network connects to GND


 Use series and parallel connections to implement gate logic






## CMOS Gates: NOT Gate

## **NOT**

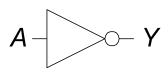

$$Y = \overline{A}$$

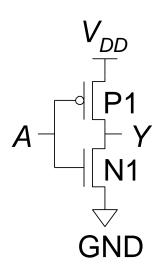


A	P1	N1	Y
0			
1			




## CMOS Gates: NOT Gate

## **NOT**

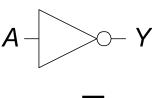

$$Y = \overline{A}$$

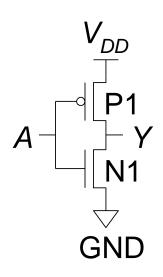


A	P1	N1	Y			
0	ON	OFF	1			
1	OFF	ON	0			



# ONE


## **CMOS Gates: NAND Gate**

## **NAND**

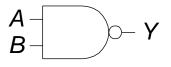

$$Y = \overline{AB}$$

A	В	Y
0	0	1
0	1	1
1	0	1
1	1	0

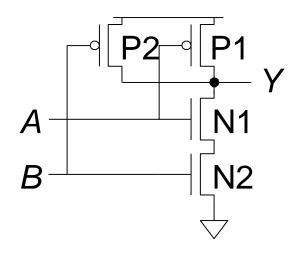


A	B	P1	P2	N1	N2	Y
0	0					
0	1					
1	0					
1	1					



# ONE


## **CMOS Gates: NAND Gate**

## **NAND**

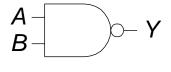

$$Y = \overline{AB}$$

_A	В	Y
0	0	1
0	1	1
1	0	1
1	1	0

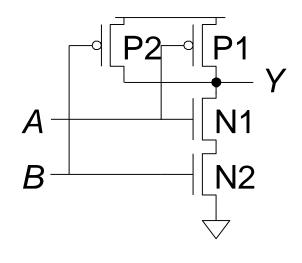

A	B	P1	P2	N1	N2	Y
0	0	ON	ON	OFF	OFF	1
0	1	ON	OFF	OFF	ON	1
1	0	OFF	ON	ON	OFF	1
1	1	OFF	OFF	ON	ON	0





## CMOS Gates: NOR Gate


How can you build three input (A, B, C) NOR gate?




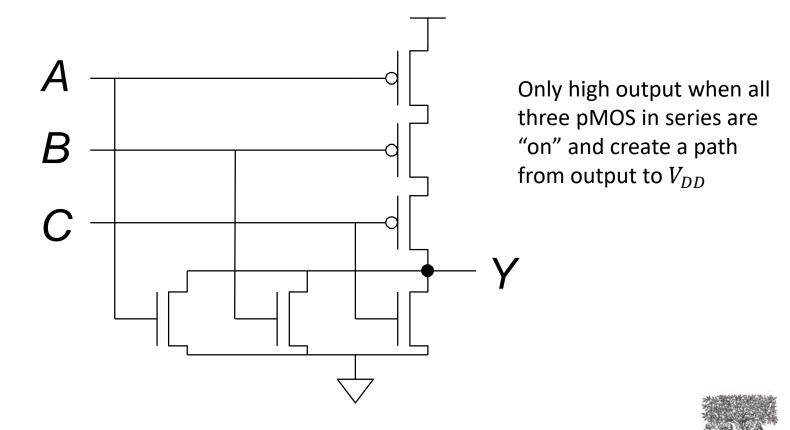
## CMOS Gates: NOR Gate

How can you build three input (A, B, C) NOR gate?





## CMOS Gates: AND Gate


How can you build 2 input AND gate?





## CMOS Gates: AND Gate

How can you build 2 input AND gate?

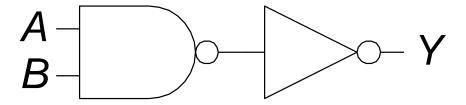






## CMOS Gates: AND Gate

How can you build 2 input AND gate?

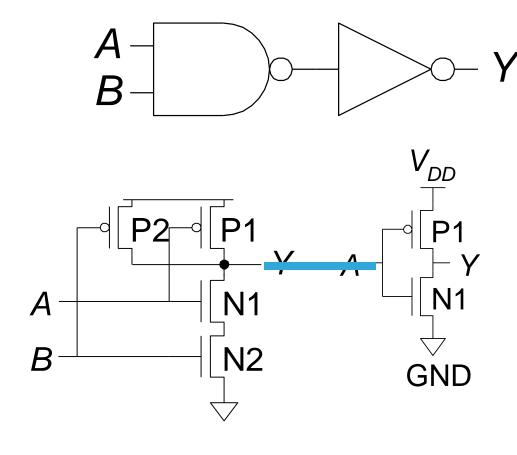


Note: AND requires 2 more gates than NAND. Inverted logic is more efficient implementation.




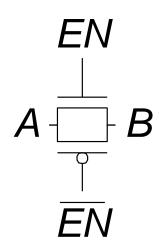
## **Transmission Gates**


- nMOS pass 1's poorly, pMOS pass 0's poorly
- Transmission gate is for passing signal
  - Pass both 0 and 1 well
- When EN = 1, the switch is ON:
  - $\overline{EN} = 0$  and A is connected to B
- When EN = 0, the switch is OFF:
  - A is not connected to B




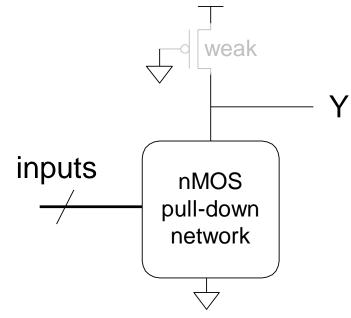
## Psuedo-nMOS

- Replace pull-up network with weak pMOS transistor that is always on
  - pMOS gate tied to ground
- pMOS transistor: pulls output HIGH only when nMOS network not pulling it LOW







## Psuedo-nMOS Example: NOR4


How many transistors needed?




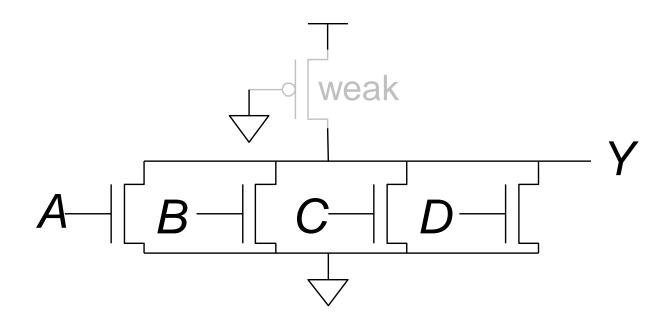
## Psuedo-nMOS Example: NOR4

- How many transistors needed?
  - Only 5 since a single pMOS is used






# ONE 20
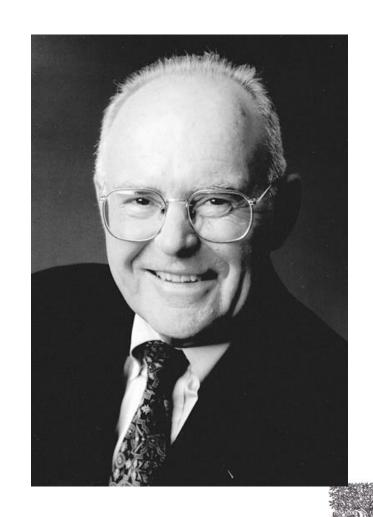
## Gordon Moore, 1929-

- Cofounded Intel in 1968 with Robert Noyce.
- Moore's Law: number of transistors on a computer chip doubles every year (observed in 1965)
  - Since 1975, transistor counts have doubled every two years.





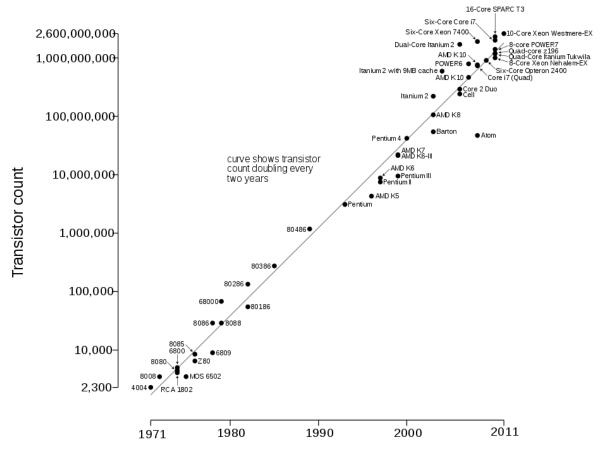
## Moore's Law

Transistor count doubles every 2 years


Microprocessor Transistor Counts 1971-2011 & Moore's Law





# ONE

## Moore's Law Trends

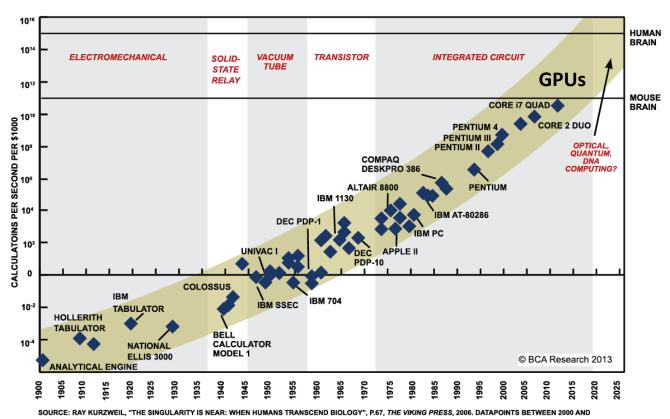

2012 REPRESENT BCA ESTIMATES.

 "If the automobile had followed the same development cycle as the computer, a Rolls-Royce would today cost \$100, get one million miles to the gallon, and explode once a year . . ."

Robert Cringley



## Power Consumption

Power = Energy consumed per unit time

- Two types of power
  - Dynamic power consumption
  - Static power consumption





## **Dynamic Power Consumption**

- Power to charge transistor gate capacitances
  - Energy required to charge a capacitance, C, to  $V_{DD}$  is  $CV_{DD}^2$
  - Circuit running at frequency f: transistors switch (from 1 to 0 or vice versa) at that frequency
  - Capacitor is charged f/2 times per second (discharging from 1 to 0 is free)
- Dynamic power consumption

$$P_{dynamic} = \frac{1}{2}CV_{DD}^2 f$$





## Static Power Consumption

- Power consumed when no gates are switching
- Caused by the quiescent supply current,  $I_{DD}$  (also called the leakage current)

Static power consumption

$$P_{static} = I_{DD}V_{DD}$$





## Power Consumption Example

- Estimate the power consumption of a wireless handheld computer
  - $V_DD = 1.2 \text{ V}$
  - $C = 20 \, \text{nF}$
  - f = 1 GHz
  - $I_{DD} = 20 \text{ mA}$

 Total power is sum of dynamic and static





## Power Consumption Example

- Estimate the power consumption of a wireless handheld computer
  - $V_DD = 1.2 \text{ V}$
  - $C = 20 \, \text{nF}$
  - f = 1 GHz
  - $I_{DD} = 20 \text{ mA}$

 Total power is sum of dynamic and static

$$P = \frac{1}{2}CV_{DD}^{2}f + I_{DD}V_{DD}$$

$$= \frac{1}{2}(20 \text{ n})(1.2)^{2}(1 \text{ G})$$

$$+ (20 \text{ m})(1.2)$$

$$= (14.4 + 0.024)W$$

$$= 14.4 \text{ W}$$



## Extras





## Binary Codes

Another way of representing decimal numbers

## **Example binary codes:**

- Weighted codes
  - Binary Coded Decimal (BCD) (8-4-2-1 code)
  - 6-3-1-1 code
  - 8-4-2-1 code (simple binary)
- Gray codes
- Excess-3 code
- 2-out-of-5 code





## Binary Codes

Decimal #	8-4-2-1 (BCD)	6-3-1-1	Excess-3	2-out-of-5	Gray
0	0000	0000	0011	00011	0000
1	0001	0001	0100	00101	0001
2	0010	0011	0101	00110	0011
3	0011	0100	0110	01001	0010
4	0100	0101	0111	01010	0110
5	0101	0111	1000	01100	1110
6	0110	1000	1001	10001	1010
7	0111	1001	1010	10010	1011
8	1000	1011	1011	10100	1001
9	1001	1100	1100	11000	1000

Each code combination represents a single decimal digit.



## ASCII-Code

TABLE 1-3 ASCII Code

IABLE 1-3	AS	CII	Coc	e																			
			ASC	II C	ode	e					ASC	II C	ode					-	ASC	II C	ode		
Character	$A_6$	A <sub>5</sub>	A <sub>4</sub>	A <sub>3</sub>	A <sub>2</sub>	A <sub>1</sub>	$A_0$	Character	$A_6$	A <sub>5</sub>	$A_4$	A <sub>3</sub>	A <sub>2</sub>	$A_1$	A <sub>0</sub>	Character	$A_6$	A۶	$A_4$	A <sub>3</sub>	A <sub>2</sub>	A <sub>1</sub>	A <sub>0</sub>
space	0	1	0	0	0	0	0	@	1	0	0	0	0	0	0	,	1	1	0	0	0	0	0
	0	1	0	0	0	0	1	Α	1	0	0	0	0	0	1	a	1	1	0	0	0	0	1
"	0	1	0	0	0	1	0	В	1	0	0	0	0	1	0	b	1	1	0	0	0	1	0
#	0	1	0	0	0	1	1	C	1	0	0	0	0	1	1	c	1	1	0	0	0	1	1
\$	0	1	0	0	1	0	0	D	1	0	0	0	1	0	0	d	1	1	0	0	1	0	0
%	0	1	0	0	1	0	1	E	1	0	0	0	1	0	1	e	1	1	0	0	1	0	1
&	0	1	0	0	1	1	0	F	1	0	0	0	1	1	0	f	1	1	0	0	1	1	0
,	0	1	0	0	1	1	1	G	1	0	0	0	1	1	1	g	1	1	0	0	1	1	1
(	0	1	0	1	0	0	0	н	1	0	0	1	0	0	0	h	1	1	0	1	0	0	0
)	0	1	0	1	0	0	1	1	1	0	0	1	0	0	1	i	1	1	0	1	0	0	1
*	0	1	0	1	0	1	0	J	1	0	0	1	0	1	0	j	1	1	0	1	0	1	0
+	0	1	0	1	0	1	1	K	1	0	0	1	0	1	1	k	1	1	0	1	0	1	1
,	0	1	0	1	1	0	0	L	1	0	0	1	1	0	0	- 1	1	1	0	1	1	0	0
_	0	1	0	1	1	0	1	M	1	0	0	1	1	0	1	m	1	1	0	1	1	0	1
	0	1	0	1	1	1	0	N	1	0	0	1	1	1	0	n	1	1	0	1	1	1	0
/	0	1	0	1	1	1	1	0	1	0	0	1	1	1	1	0	1	1	0	1	1	1	1
0	0	1	1	0	0	0	0	Р	1	0	1	0	0	0	0	р	1	1	1	0	0	0	0
1	0	1	1	0	0	0	1	Q	1	0	1	0	0	0	1	q	1	1	1	0	0	0	1
2	0	1	1	0	0	1	0	R	1	0	1	0	0	1	0	r	1	1	1	0	0	1	0
3	0	1	1	0	0	1	1	S	1	0	1	0	0	1	1	S	1	1	1	0	0	1	1
4	0	1	1	0	1	0	0	T	1	0	1	0	1	0	0	t	1	1	1	0	1	0	0
5	0	1	1	0	1	0	1	U	1	0	1	0	1	0	1	u	1	1	1	0	1	0	1
6	0	1	1	0	1	1	0	V	1	0	1	0	1	1	0	v	1	1	1	0	1	1	0
7	0	1	1	0	1	1	1	W	1	0	1	0	1	1	1	w	1	1	1	0	1	1	1
8	0	1	1	1	0	0	0	X	1	0	1	1	0	0	0	x	1	1	1	1	0	0	0
9	0	1	1	1	0	0	1	Y	1	0	1	1	0	0	1	У	1	1	1	1	0	0	1
:	0	1	1	1	0	1	0	Z	1	0	1	1	0	1	0	z	1	1	1	1	0	1	0
;	0	1	1	1	0	1	1	Į.	1	0	1	1	0	1	1	{	1	1	1	1	0	1	1
<	0	1	1	1	1	0	0	,	1	0	1	1	1	0	0	Į	1	1	1	1	1	0	0
=	0	1	1	1	1	0	1	j	1	0	1	1	1	0	1	}	1	1	1	1	1	0	1
>	0	1	1	1	1	1	0	^	1	0	1	1	1	1	0	~	1	1	1	1	1	1	0
?	0	1	1	1	1	1	1	_	1	0	1	1	1	1	1	delete	1	1	1	1	1	1	1



## Weighted Codes

- Weighted codes: each bit position has a given weight
  - Binary Coded Decimal (BCD) (8-4-2-1 code)
    - Example:  $726_{10} = 0111 \ 0010 \ 0110_{BCD}$
  - 6-3-1-1 code
    - **Example:**  $1001 (6-3-1-1 \text{ code}) = 1\times6 + 0\times3 + 0\times1 + 1\times1$
    - Example:  $726_{10} = 1001 \ 0011 \ 1000_{6311}$
- BCD numbers are used to represent fractional numbers exactly (vs. floating point numbers – which can't - see Chapter 5)



## Weighted Codes

Decimal #	8-4-2-1 (BCD)	6-3-1-1
0	0000	0000
1	0001	0001
2	0010	0011
3	0011	0100
4	0100	0101
5	0101	0111
6	0110	1000
7	0111	1001
8	1000	1011
9	1001	1100

## BCD Example:

$$726_{10} = 0111\ 0010\ 0110_{BCD}$$

## 6-3-1-1 code Example:

$$726_{10} = 1001\ 0011\ 1000_{6311}$$



# ONE ROM

## Excess-3 Code

Decimal #	Excess-3
0	0011
1	0100
2	0101
3	0110
4	0111
5	1000
6	1001
7	1010
8	1011
9	1100

- Add 3 to number, then represent in binary
  - Example:  $5_{10} = 5 + 3 = 8 = 1000_2$
- Also called a biased number
- Excess-3 codes (also called XS-3) were used in the 1970's to ease arithmetic

## Excess-3 Example:

$$726_{10} = 1010\ 0101\ 1001_{xs3}$$



## 2-out-of-5 Code

Decimal #	2-out-of-5
0	00011
1	00101
2	00110
3	01001
4	01010
5	01100
6	10001
7	10010
8	10100
9	11000

2 out of the 5 bits
 are 1

- Used for error detection:
  - If more or less than 2 of 5 bits are 1, error



# N N 2

## **Gray Codes**

Decimal #	Gray
0	0000
1	0001
2	0011
3	0010
4	0110
5	1110
6	1010
7	1011
8	1001
9	1000

- Next number differs in only one bit position
  - Example: 000, 001, 011, 010, 110, 111, 101, 100
- Example use: Analog-to-Digital (A/D) converters. Changing 2 bits at a time (i.e., 011 →100) could cause large inaccuracies.

