

CPE100: Digital Logic Design I

Professor Brendan Morris, SEB 3216, brendan.morris@unlv.edu

K-Map Examples


Chapter 2.7

Example 1: 3 Input

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

Example 1: 3 Input

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

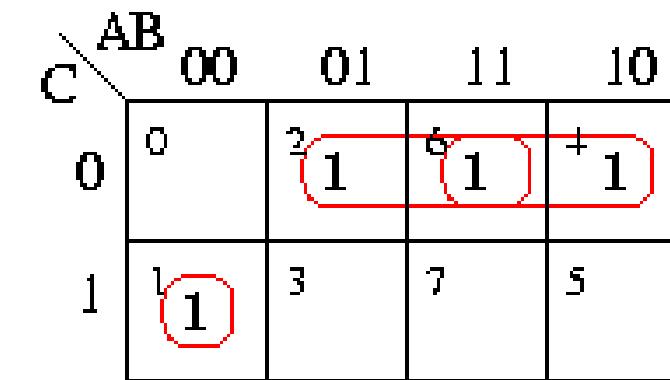


$$Y = \bar{A} \bar{B} C + B \bar{C} + A \bar{C}$$

Example 2: 3 Input

A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

Example 2: 3 Input

A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

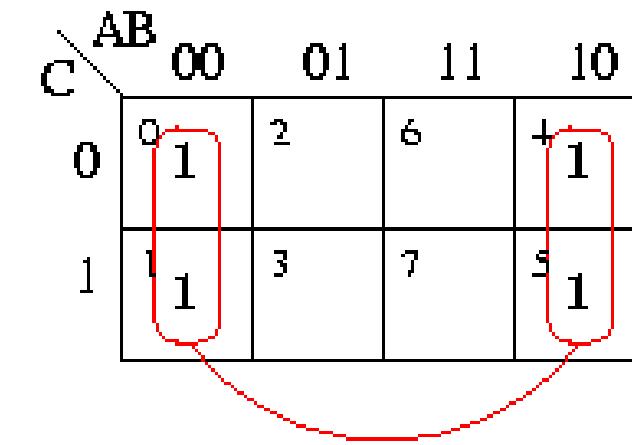


$$Y = \bar{B}$$

Example 3: 4 Input

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	1

Example 3: 4 Input

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	1

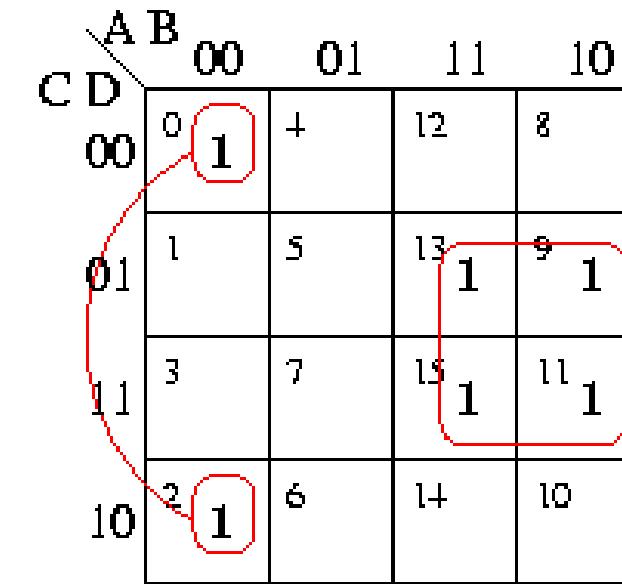


$$Y = AD + \bar{A}\bar{B}\bar{D}$$

Example 4: Minterm Specification

- 4 variable (A,B,C,D) input
- $Y = \sum m(0,2,8,9,10,11)$
- E.g.
- $m8 = A\bar{B}\bar{C}\bar{D} = 1000$
- $A = 1, B = 0, C = 0, D = 0$

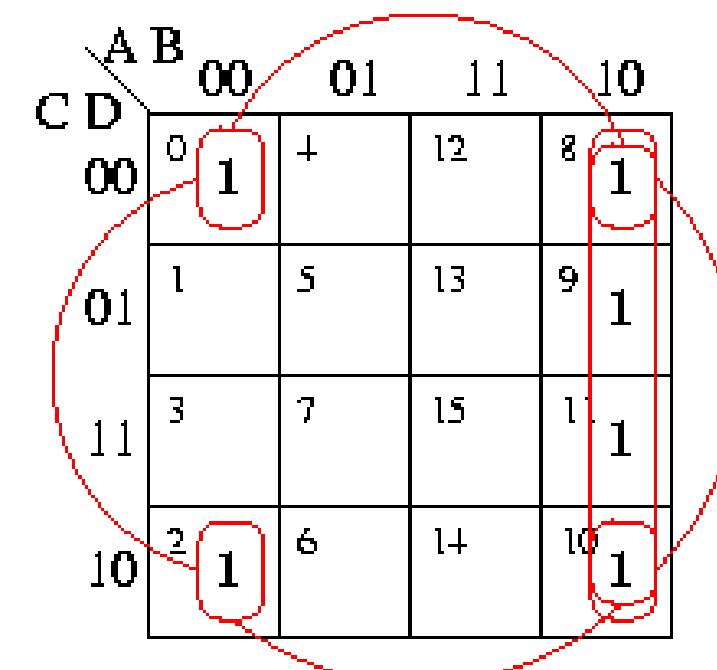Example 4: Minterm Specification

- 4 variable (A,B,C,D) input
- $Y = \sum m(0,2,8,9,10,11)$
- E.g.
- $m8 = A\bar{B}\bar{C}\bar{D} = 1000$
- $A = 1, B = 0, C = 0, D = 0$



$$Y = \bar{B}\bar{D} + A\bar{B}$$

Example 5: Minterm Specification

- 4 variable (A,B,C,D) input
- $Y = \sum m(1,3,6,9,11,12,13)$

Example 5: Minterm Specification

- 4 variable (A,B,C,D) input
- $Y = \sum m(1,3,6,9,11,12,13)$

		A	B	00	01	11	10
		C	D	00	+	12	8
00	01	1					
		1		5		13	1
11	10	3		7		15	1
		1				11	1
2	6	1		14		10	

$$Y = AB\bar{C} + \bar{B}D + \bar{A}BC\bar{D}$$


Example 6: Don't Cares

- 4 variable (A,B,C,D) input
- $Y = \sum m(4,5,7,8,10,11,13,14) + \sum d(0,1,2)$
 - d term indicates do not care

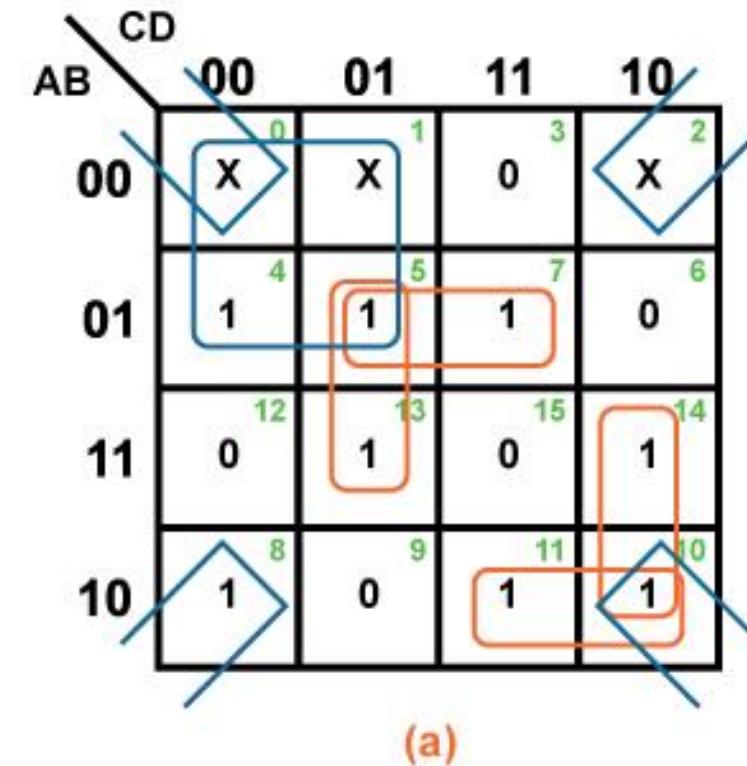Example 6: Don't Cares

- 4 variable (A,B,C,D) input

- $Y = \sum m(4,5,7,8,10,11,13,14) + \sum d(0,1,2)$
 - d term indicates do not care



$$Y = \bar{B}\bar{D} + \bar{A}\bar{C} + B\bar{C}D + \bar{A}BD + ACD + A\bar{B}C$$


Note: AB and CD are switched in this K-map

Example 7: Maxterm Specification

- 4 variable (A,B,C,D) input
- Maxterm expression for POS form
- $$Y = \prod M(3,6,9,12,15) + \sum d(0,1,2)$$

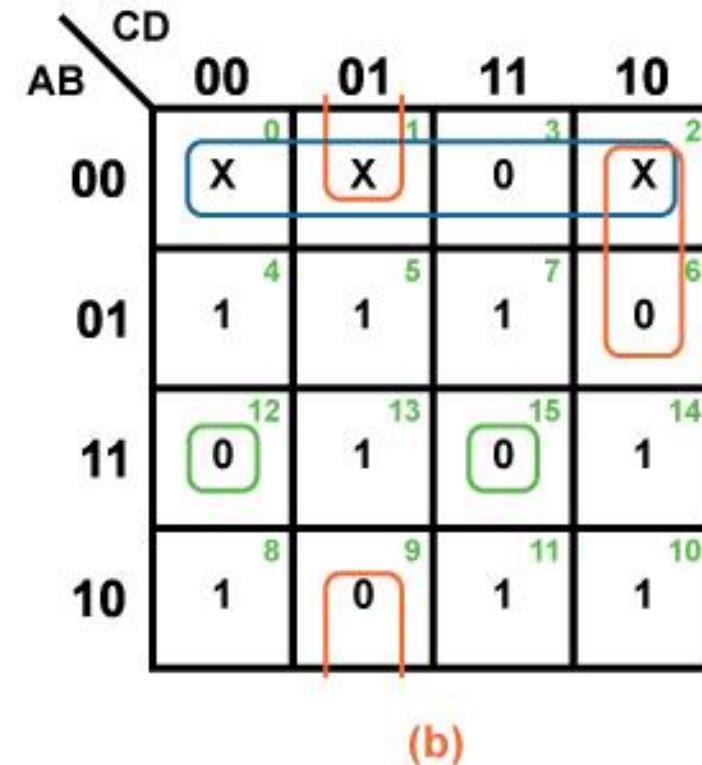Example 7: Maxterm Specification

- 4 variable (A,B,C,D) input
- Maxterm expression for POS form
- $Y = \prod M(3,6,9,12,15) + \sum d(0,1,2)$



$$Y = (A + B)(B + C + \bar{D})(A + \bar{C} + D)(\bar{A} + \bar{B} + C + D)(\bar{A} + \bar{B} + \bar{C} + \bar{D})$$

Note: AB and CD are switched in this K-map

Example 8: Equation Specification

- Use a K-map to simplify the following equation
- $Y = ABC + BCD + AC + BC$
- Note this is a 4-input problem
- Use expansion to find canonical minterms or
- Create full truth table
- Ex:
 - $ABC \rightarrow 1110$ and 1111 (D can be either 0 or 1)
 - $AC \rightarrow 1010, 1011, 1110$, and 1111
 - 1st and 3rd bits turned on

Example 8: Equation Specification

- Use a K-map to simplify the following equation
- $Y = ABC + BCD + AC + BC$

A	B	C	D	Y
0	0	0	0	
0	0	0	1	
0	0	1	0	
0	0	1	1	
0	1	0	0	
0	1	0	1	
0	1	1	0	
0	1	1	1	
1	0	0	0	
1	0	0	1	
1	0	1	0	
1	0	1	1	
1	1	0	0	
1	1	0	1	
1	1	1	0	
1	1	1	1	

Example 8: Equation Specification

- Use a K-map to simplify the following equation
- $Y = \textcolor{red}{ABC} + BCD + AC + BC$

A	B	C	D	Y
0	0	0	0	
0	0	0	1	
0	0	1	0	
0	0	1	1	
0	1	0	0	
0	1	0	1	
0	1	1	0	
0	1	1	1	
1	0	0	0	
1	0	0	1	
1	0	1	0	
1	0	1	1	
1	1	0	0	
1	1	0	1	
1	1	1	0	1
1	1	1	1	1

Example 8: Equation Specification

- Use a K-map to simplify the following equation
- $Y = ABC + \textcolor{red}{BCD} + AC + BC$

A	B	C	D	Y
0	0	0	0	
0	0	0	1	
0	0	1	0	
0	0	1	1	
0	1	0	0	
0	1	0	1	
0	1	1	0	
0	1	1	1	1
1	0	0	0	
1	0	0	1	
1	0	1	0	
1	0	1	1	
1	1	0	0	
1	1	0	1	
1	1	1	0	1
1	1	1	1	1

Example 8: Equation Specification

- Use a K-map to simplify the following equation
- $Y = ABC + BCD + AC + BC$

A	B	C	D	Y
0	0	0	0	
0	0	0	1	
0	0	1	0	
0	0	1	1	
0	1	0	0	
0	1	0	1	
0	1	1	0	
0	1	1	1	1
1	0	0	0	
1	0	0	1	
1	0	1	0	1
1	0	1	1	1
1	1	0	0	
1	1	0	1	
1	1	1	0	1
1	1	1	1	1

Example 8: Equation Specification

- Use a K-map to simplify the following equation
- $Y = ABC + BCD + AC + BC$
- Normal simplification
 - $Y = AC + BC$


A	B	C	D	Y
0	0	0	0	
0	0	0	1	
0	0	1	0	
0	0	1	1	
0	1	0	0	
0	1	0	1	
0	1	1	0	1
0	1	1	1	1
1	0	0	0	
1	0	0	1	
1	0	1	0	1
1	0	1	1	1
1	1	0	0	
1	1	0	1	
1	1	1	0	1
1	1	1	1	1

Example 9: 5 Input

- 5-input function (A,B,C,D,E)
 - Create two 4-input K-maps and “stack”

A = 0		BC				
		DE	00	01	11	10
DE	00	0	4	12	8	
	01	1	5	13	9	
	11	3	7	15	11	
	10	2	6	14	10	

A = 1		BC				
		DE	00	01	11	10
DE	00	16	20	28	24	
	01	17	21	29	25	
	11	19	23	31	27	
	10	18	22	30	26	

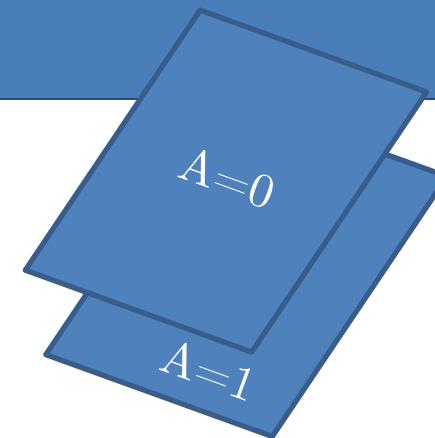

- Draw bubbles within 4x4 and in between stack (above or below)
 - E.g. cell 5 and 21 → B'CD'E

Example 9: 5 Input

- $Y = \sum m(0,1,2,3,8,9,16,17,20,21,24,25,28,29,30,31)$

Example 9: 5 Input

- $Y = \sum m(0,1,2,3,8,9,16,17,20,21,24,25,28,29,30,31)$

		BC			
		00	01	11	10
DE	00	1	4	12	1
	01	1	5	13	1
11	1	7	15	11	
10	1	6	14	10	

		BC			
		00	01	11	10
DE	00	1	1	1	1
	01	1	1	1	1
11	19	23	1	27	
10	18	22	1	26	

- Be sure to check “above/below”
- $Y = AD' + A'B'C' + ABC + C'D'$