

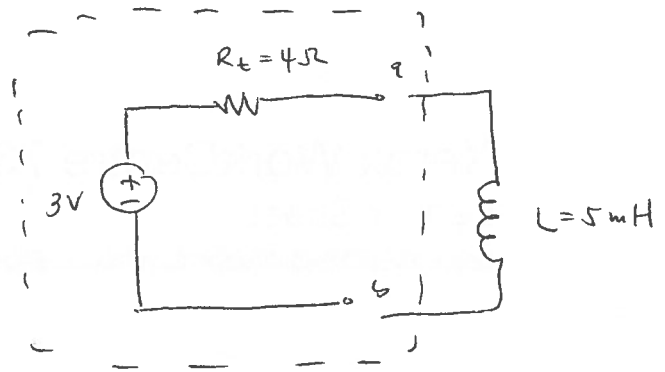


Find i , v , and i_1

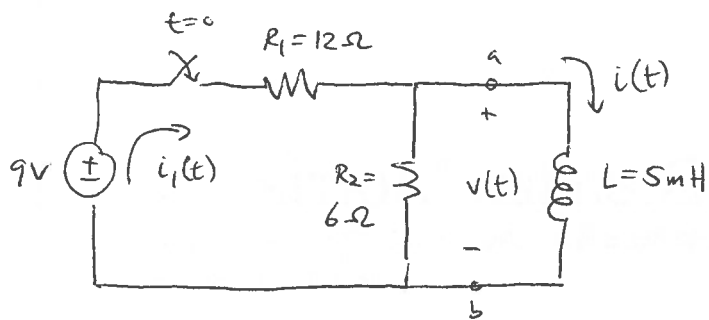

1. equivalent circuit

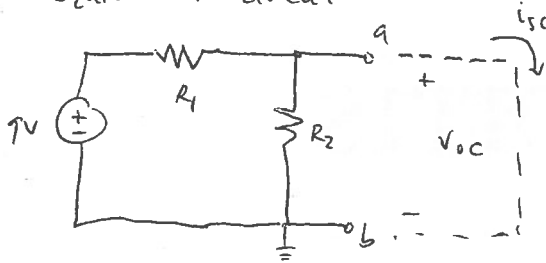

by voltage divider

$$\begin{aligned} V_{oc} &= 9 \left(\frac{R_2}{R_1 + R_2} \right) \\ &= 9 \left(\frac{6}{6 + 12} \right) \\ &= 3V \end{aligned}$$

KCL @ a

$$\frac{V_a - 9}{R_1} + \frac{V_a}{R_2} + i_{sc} = 0$$

$$i_{sc} = \frac{9 - V_a}{R_1} - \frac{V_a}{R_2}$$


because of short circuit

$$V_a = V_b = 0$$

$$i_{sc} = \frac{9}{R_1} = \frac{9}{12} = \frac{3}{4} A$$

$$R_t = \frac{V_{oc}}{i_{sc}} = \frac{3}{3/4} = 4\Omega$$

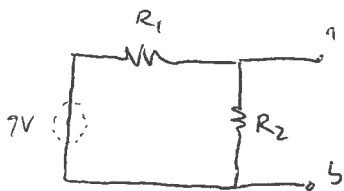using shortcut of zeroing dependent sources



$$\begin{aligned} R_t &= R_1 \parallel R_2 \\ &= \frac{6 \cdot 12}{6 + 12} = \frac{72}{18} \\ &= 4\Omega \end{aligned}$$

Using the Thevenin equivalent circuit

$$\tau = \frac{L}{R} = \frac{5m}{4} = \frac{5}{4} m = 1.25 mSec$$

solving for $i(t)$

$t \ll 0$

no current

$$v(t) = 0$$

$$i_1(t) = 0$$

$$i(t) = 0$$


$t = 0^+$ right after switch

current cannot change in inductor immediately

$$i(0^-) = i(0^+) = 0$$

$t \gg 0$

replace inductor by short circuit

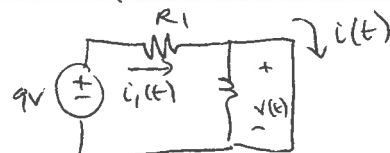

$$i_1(t) = i(t) = \frac{9}{R_1} = \frac{9}{12} = \frac{3}{4} A = i_F$$

$$v(t) = 0 = v_F$$

solving for $i(t)$

$$i(t) = i_f + [i(0^+) - i_f] e^{-t/\tau}$$


$$= \frac{3}{4} + \left[0 - \frac{3}{4}\right] e^{-t/1.25m} = \frac{3}{4} - \frac{3}{4} e^{-800t} \quad t > 0$$

solving for voltage $v(t)$

we can use current/voltage relationship of inductor

$$v(t) = L \frac{di(t)}{dt} = L \left(-\frac{3}{4}(-800) e^{-800t}\right) = 5m (3 \cdot 200 e^{-800t}) = 3 e^{-800t} \quad t > 0$$

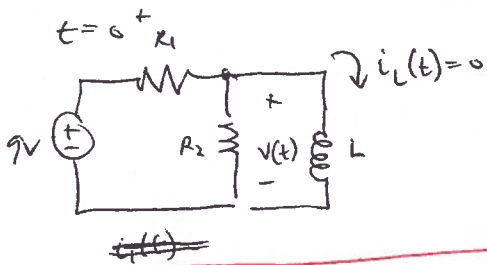or we can use the general first-order formula



since all current goes through R_2
use a voltage divider

$$v(t) = 9 \left(\frac{R_2}{R_1 + R_2}\right) = 3V$$


and we saw earlier

$$v_f = 0V.$$

$$v(t) = 0 + [3 - 0] e^{-800t} = 3 e^{-800t}$$

solving for $i_1(t)$

for $t \gg 0$

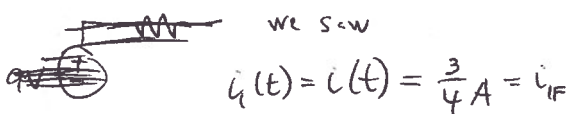

for $t = 0^+$

$$i_1(0^+) = \frac{v(0^+)}{R_2}$$

$$= \frac{3}{6} = \frac{1}{2} A$$

$$i_1(t) = i_{1f} + [i_1(0^+) - i_{1f}] e^{-t/\tau}$$

$$= \frac{3}{4} + \left[\frac{1}{2} - \frac{3}{4}\right] e^{-t/\tau}$$

$$i_1(t) = \frac{3}{4} - \frac{1}{4} e^{-800t}$$

using circuit analysis

$$i_1(t) = \frac{9 - v(t)}{R_1} = \frac{9 - v(t)}{12}$$

$$= \frac{9 - 3 e^{-800t}}{12}$$

$$= \frac{3}{4} - \frac{1}{4} e^{-800t}$$