

Homework #5
Due Th. 10/18

You may use Matlab to generate plots.

1. (Hambley P4.7)

Given an initially charged capacitance that begins to discharge through a resistance at $t = 0$,

- (a) What percentage of the initial voltage remains at two time constants?
- (b) What percentage of initial stored energy remains?

2. (Hambley P4.9)

In physics, the half-life is often used to characterize exponential decay of physical quantities such as radioactive substances. The half-life is the time required for the quantity to decay to half of its initial value. The time constant for the voltage on a capacitance discharging through a resistance is $\tau = RC$. Find an expression for the half-life of the voltage in terms of RC .

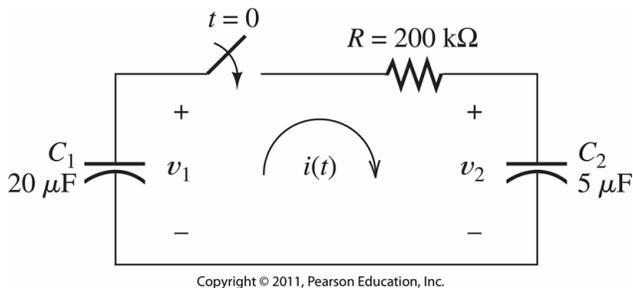


Figure P4.18

3. (Hambley P4.18)

Consider the circuit shown in Fig. P4.18. Prior to $t = 0$, $v_1 = 100$ V, and $v_2 = 0$.

- (a) Immediately after the switch is closed, what is the value of the current [i.e., what is the value of $i(0^+)$]?
- (b) Write the circuit equations needed to obtain the differential equation relating current?
- (c) What is the value of the time constant in this circuit?

- (d) Find an expression for the current as a function of time.
- (e) Find the value that v_2 approaches as t becomes very large.

4. (Hambley P4.20)

Explain why we replace capacitances with open circuits and inductances with short circuits in dc steady-state analysis.

5. (Hambley P4.24)

The circuit shown in Fig. P4.24 has been setup for a long time prior to $t = 0$ with the switch closed. Find the value of v_C prior to $t = 0$. Find the steady-state value of v_C after the switch has been opened for a long time.

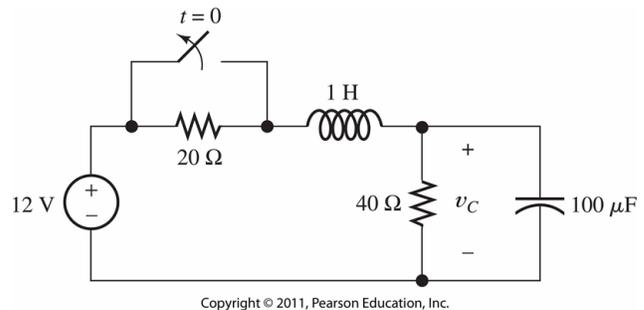


Figure P4.24

6. (Hambley P4.27)

The circuit of Fig. P4.27 has been connected for a very long time. Determine the values of v_C and i_R .

7. (Hambly P4.28)

Consider the circuit of Fig. P4.28 in which the switch has been closed for a long time prior to $t = 0$.

- (a) Determine the values of $v_C(t)$ before $t = 0$ and a long time after $t = 0$.
- (b) Also determine the time constant after the switch opens and an expression for $v_C(t)$.
- (c) Sketch $v_C(t)$ to scale versus time for $-0.2 \leq t \leq 0.5$ s

8. (Hambly P4.42)

The switch shown in Fig. P4.42 has been closed for a long time prior to $t = 0$, then it opens at $t = 0$ and closes again at $t = 1$ s. Find $i_L(t)$ for all t .

9. (Hambly P4.43)

Determine expressions for and sketch $v_R(t)$ to scale versus time for the circuit of Fig. P4.43. The circuit is operating in steady state with the switch closed prior to $t = 0$. Consider the time interval $-1 \leq t \leq 5$ ms.

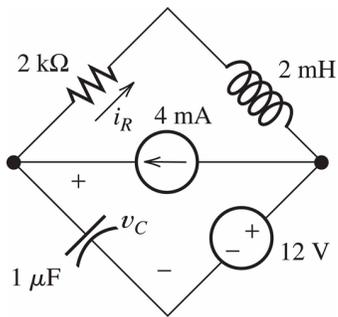


Figure P4.27

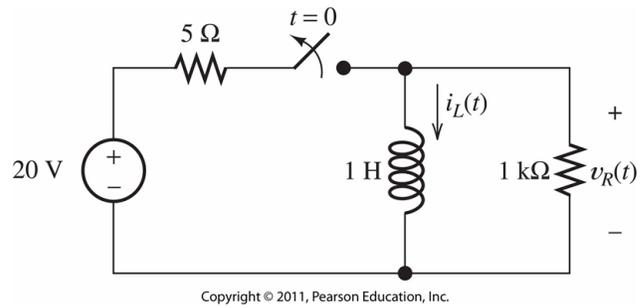


Figure P4.43

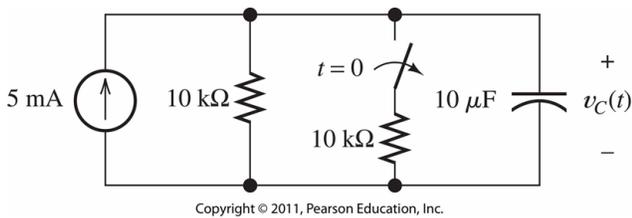


Figure P4.28

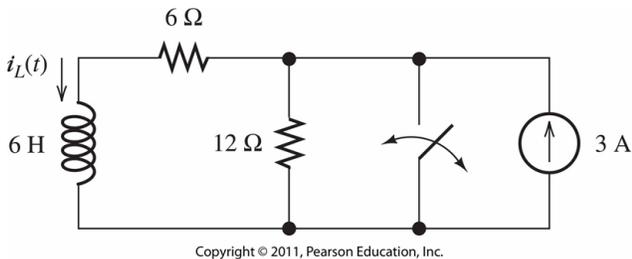


Figure P4.42