

ee 292 midterm 01 review

9/22 chapter 1 p1.13, p1.18, p1.25, p1.26, p1.66, p1.68, p1.72, p1.74, t1.3, t1.5

current - time rate of flow of electrical charge through a circuit element

$$i(t) = \frac{dq(t)}{dt} \quad q(t) = \int_{t_0}^t i(t) dt + q(t_0)$$

power - rate of energy transfer

$$p(t) = v(t) i(t) \quad \text{passive reference}$$

$$p(t) = -v(t) i(t) \quad \text{not passive reference}$$

energy

$$w = \int_{t_1}^{t_2} p(t) dt$$

$p, w > 0$ energy absorbed by element

$p, w < 0$ energy supplied by element

KCL - conservation of charge

① net current into a node is zero

② sum of currents into a node equals sum of currents leaving a node

KVL - conservation of energy

the sum of voltages around a loop is zero

Ohm's Law - relationship for an ideal resistor

$$v = iR \Rightarrow v(t) = i(t)R$$

$$p(t) = i^2(t)R = \frac{v^2(t)}{R} \quad \text{always } > 0 \text{ absorbs energy}$$

chapter 3 p3.4, p3.13, p3.26, p3.47, p3.51, p3.62

capacitance - ~~time~~ energy stored in electric fields.

capacitor

$$q = Cv \Rightarrow q(t) = Cv(t) \Rightarrow i(t) = \frac{dq(t)}{dt} = C \frac{dv(t)}{dt}$$

$$\text{constant voltage} \Rightarrow \frac{dv}{dt} = 0 \Rightarrow i(t) = 0 \Rightarrow \text{open circuit}$$

no current flow

$$\text{power} - p(t) = v(t) C \frac{dv(t)}{dt}$$

$$\text{energy} - w = \frac{1}{2} C v^2(t)$$

inductor - circuit element to store energy in a magnetic field

$$v(t) = L \frac{di(t)}{dt}$$

constant current $\Rightarrow \frac{di(t)}{dt} = 0 \Rightarrow v(t) = 0 \Rightarrow$ short circuit.

power - $p(t) = L \frac{di}{dt} i(t)$

energy - $w(t) = \frac{1}{2} L i^2(t)$

series connections

capacitors - $C_{eq} = \left[\sum \frac{1}{C_i} \right]^{-1}$

inductors - $L_{eq} = \sum L_i$

parallel connections

capacitors - $C_{eq} = \sum C_i$

inductors - $L_{eq} = \left[\sum \frac{1}{L_i} \right]^{-1}$


chapter 2

series resistance - $R_{eq} = \sum R_i$

parallel resistance - $R_{eq} = \left[\sum \frac{1}{R_i} \right]^{-1}$

voltage divider - series combination of resistors.
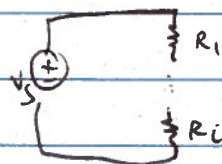
$$V_{R_i} = V_S \left(\frac{R_i}{\sum R_i} \right)$$



current divider - two parallel resistors.



$$i_1 = I_S \left(\frac{R_2}{R_1 + R_2} \right) \quad i_2 = I_S \left(\frac{R_1}{R_1 + R_2} \right)$$

node-voltage analysis - voltages are unknown in the circuit

define ground and use KCL at nodes

- by convention, define currents leaving node (unless it is a source)

super nodes - required for a voltage source not connected to ground

acts as a node for KCL, gives a relationship for node voltages.

mesh current analysis - mesh currents are unknown in circuit

requires a planar circuit,

define clockwise mesh currents and apply KVL around the loops.


current through a circuit element is sum of ^{mesh} loop currents.

supermeshes - required for a shared current source.

do KVL around supermesh, gives relationship between shared mesh current

superposition - linear sources can be treated independently and the total response is the sum of individual responses.

Thevenin/Norton equivalents:

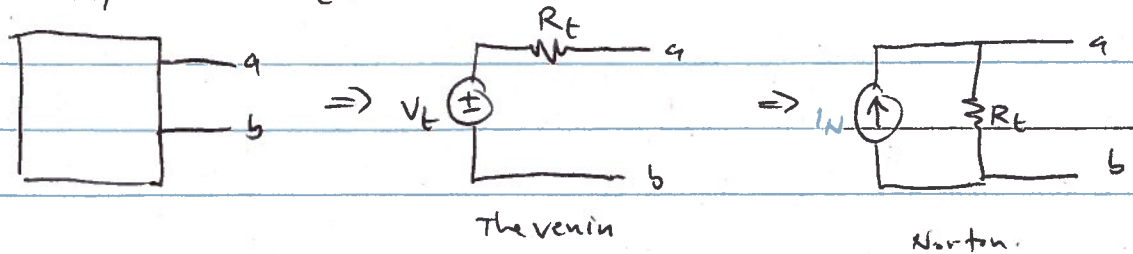

- ① open circuit voltage $V_{oc} = V_t$
- ② short circuit current $I_{sc} = I_N$
- ③ equivalent resistance $R_{eq} = R_t = \frac{V_{oc}}{I_{sc}}$