

EE292: Fundamentals of ECE

Fall 2012

TTh 10:00-11:15 SEB 1242

Lecture 2

120830

<http://www.ee.unlv.edu/~b1morris/ee292/>

Outline

- Review
- Power/Energy
- KCL
- KVL
- Circuit Elements

Fluid Flow Analogy

- Fluid = electric charge
 - What is moving around
- Pipes = wires
 - The medium of transport
- Valve = switch
 - Start/stop flow
- Pump = battery
 - Provides the force to move charge
- Pipe blockage = resistor
 - Prevents smooth flow

Electric Charge


- A conductor is a material where charge is free to flow
- Even at rest, charge carriers are in rapid motion due to thermal energy
 - Think back to physics
- Typical charge carriers are electrons (negative) and ions or holes (positive) charge
- Electron charge (Coulombs)
 - $q = -1.602 \times 10^{-19} \text{ C}$

Current

- Current is charge in motion
- It is defined as the amount of charge passing through a surface in a small time interval
- $i(t) = \frac{dq(t)}{dt}$
 - $q(t)$ is the charge crossing a surface over time
 - Units are [C/s], also known as an amp

Current Reference Directions

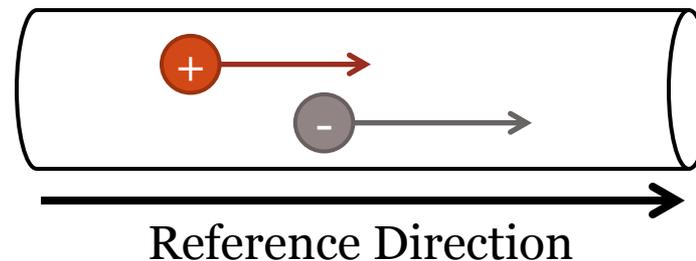- In order to define a current, a reference direction must be defined
- The reference direction indicates which direction positive charge is moving




- Positive charge carriers in reference direction → positive current
- Negative charge carriers in reference direction → negative current

Determining Current Direction

- When analyzing a circuit the direction of current flow is unknown
- Arbitrarily define a current reference direction
 - This may not match actual current flow
 - If the current value turns out to be negative, it means current flows opposite your reference direction

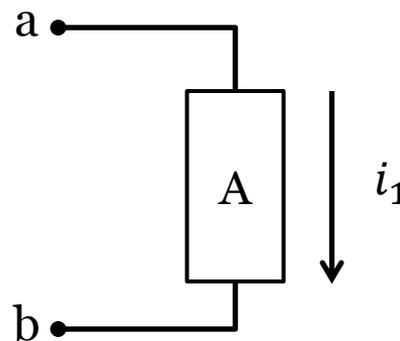
- $i_1 = -2 \text{ mA}$
 - Current flows from b to a



Double Subscript Notation

- Alternative to arrows for denoting reference direction
- Current is defined from a start node to an end node

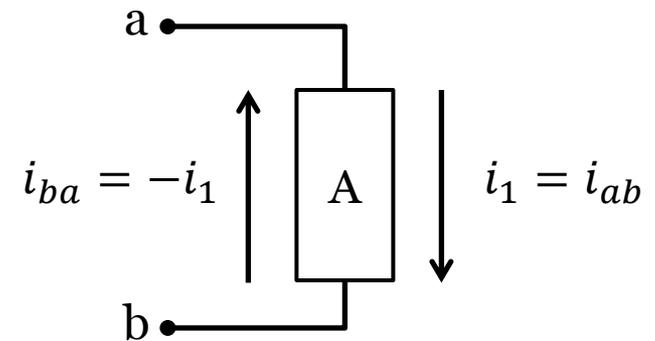- $i_1 = i_{ab}$
 - Current flow from a to b
- $i_1 = i_{ab} = -i_{ba}$




Voltage

- A measure of the energy transferred per unit charge from one point to another in a circuit
- The potential difference between two nodes
- Units are Volts [$V = J/C$]

Voltage Reference Polarities

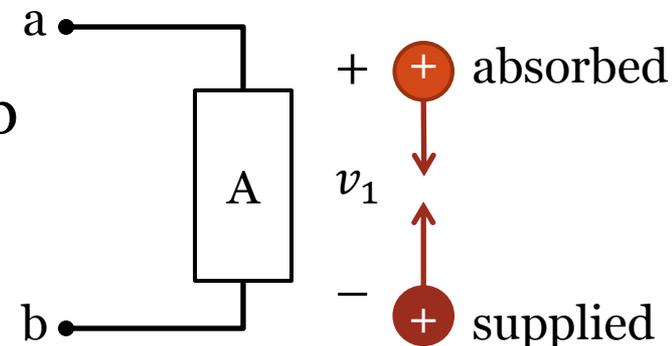
- Like with currents, must assign arbitrary reference
- Set the polarity on either side of circuit element
 - a is positive polarity
 - b is negative polarity
 - Assume a has higher voltage than b



- Positive charge flowing into the positive terminal \rightarrow energy is absorbed by element A
- Positive charge flowing into the negative terminal \rightarrow energy supplied by element A


Double Subscript Notation

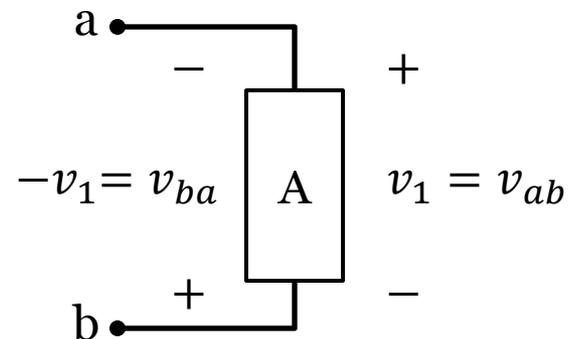- Voltage is defined based on polarities
 - Voltage from the positive to the negative polarity
- $v_1 = v_{ab}$
 - Voltage from node a to node b
 - Implicitly assume that a is at higher voltage than b
- $v_1 = v_{ab} = -v_{ba}$



Battery Example


- Imagine a battery and a light bulb

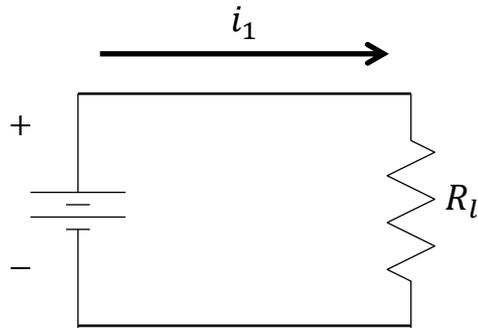

- $i_1 > 0$ current leaves the battery \rightarrow energy is supplied to the light
- $i_1 < 0$ current enters the battery \rightarrow energy is absorbed (charging)

DC and AC

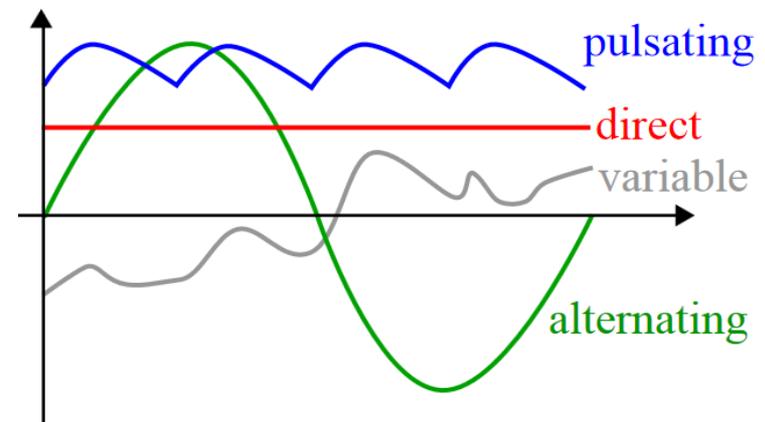- Terms apply to both current and voltage
 - Originally come from current
- Direct current (DC) – constant in time
 - E.g. 9V battery – always outputs 9V
- Alternating current (AC) – time-varying and sign/direction changes
 - E.g. 120V 60 Hz wall outlet




Source: Wikipedia

Power

- Rate of energy transfer
- $p = vi$
 - Voltage v is J/C (energy/charge)
 - Current i is C/s (charge/second)
- Units are watts [$W = (J/C)(C/s) = J/s$]


Passive Reference Configuration

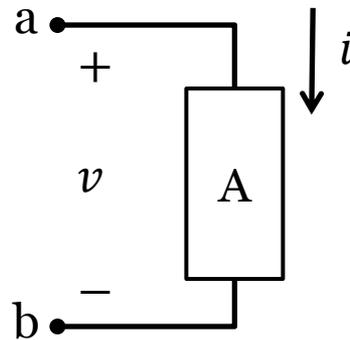- Current flows into the positive polarity terminal




- $p > 0 \rightarrow$ energy absorbed by element
 - $p < 0 \rightarrow$ energy supplied by element
- If current is defined into the negative terminal
 - $p = -vi$

Example

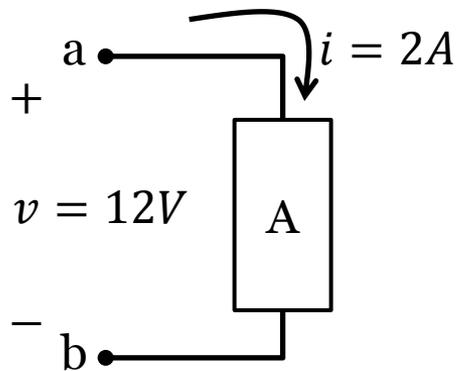


$$p = vi = 24 \text{ W}$$

A absorbs energy

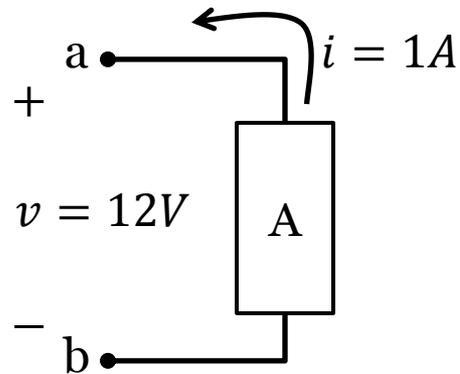

$$p = -vi = -12 \text{ W}$$

A supplies energy

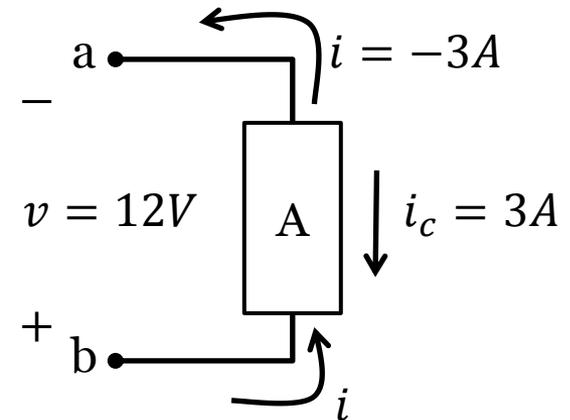

$$\begin{aligned} p &= vi = (12)(-3) \\ &= -vi_c = -(12)(3) \\ &= -36 \text{ W} \end{aligned}$$

A supplies energy


Energy

- The amount of power delivered in a time interval


$$w = \int_{t_1}^{t_2} p(t) dt$$

- Power p is a function of time

Example

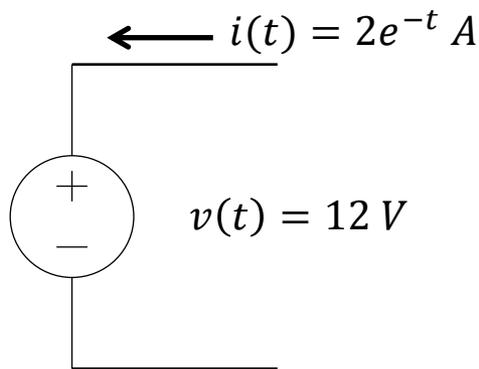
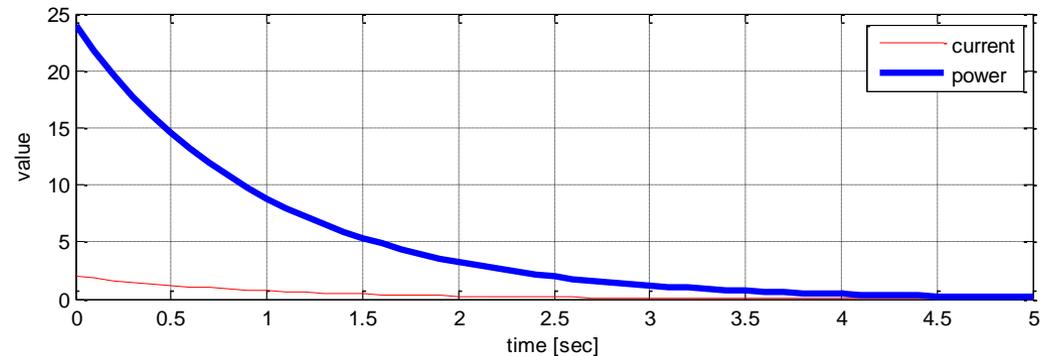
$$p(t) = v(t)i(t) = 12 \cdot 2e^{-t} = 24e^{-t}$$




$$\begin{aligned} w &= \int_0^{\infty} p(t) dt = \int_0^{\infty} 24e^{-t} dt \\ &= 24 [-e^{-t}]_0^{\infty} = 24[1 - 0] = 24 \text{ J} \end{aligned}$$

- Positive power/energy \rightarrow absorbed by voltage source

Kirchhoff's Current Law (KCL)


- KCL states the net current entering a node is zero
 - Sum of currents into a node is equal to sum of currents leaving the node
- This is a consequence of conservation of charge
 - Cannot have accumulation of charge
 - Think of:
 - pipes and fluid flow → water in must go out

KCL Examples

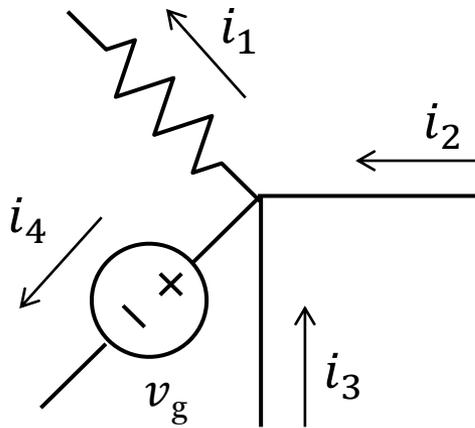


$$i_2 + i_3 = i_1 + i_4$$

$$i_2 + i_3 - i_1 - i_4 = 0$$

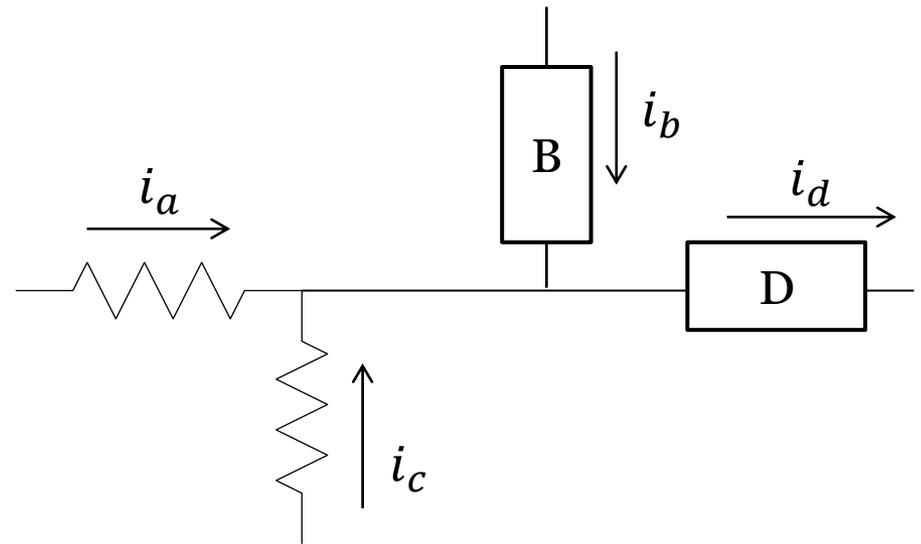

$$i_a + i_c + i_b = i_d$$

Series Example

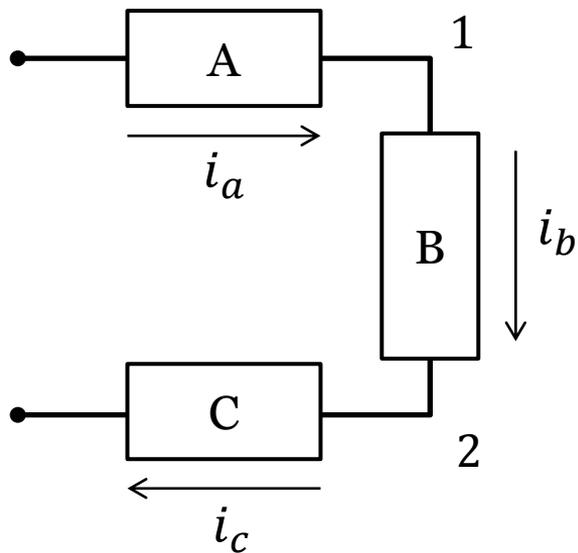

by KCL


$$\left. \begin{array}{l} 1. i_a = i_b \\ 2. i_b = i_c \end{array} \right\} i_a = i_b = i_c$$

- These elements are connected in series \rightarrow same current flows through all of them

Kirchhoff's Voltage Law (KVL)


- KVL states the algebraic sum of voltages for any closed path (loop) is zero
- This is a consequence of conservation of energy
 - Cannot have more energy absorbed than supplied
 - Think of:
 - potential energy in going up a hill → energy gained going up is lost going back down

Example Loop

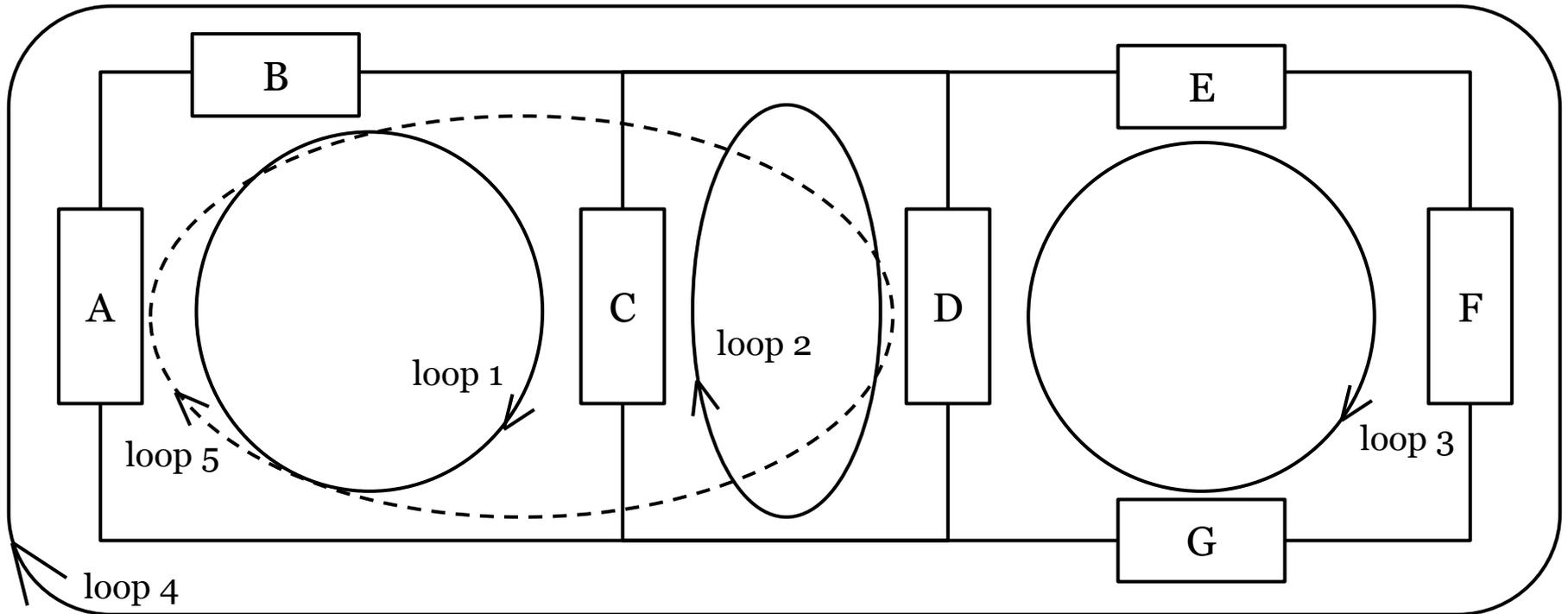


A loop is a closed path along circuit from a start node back to itself

Example

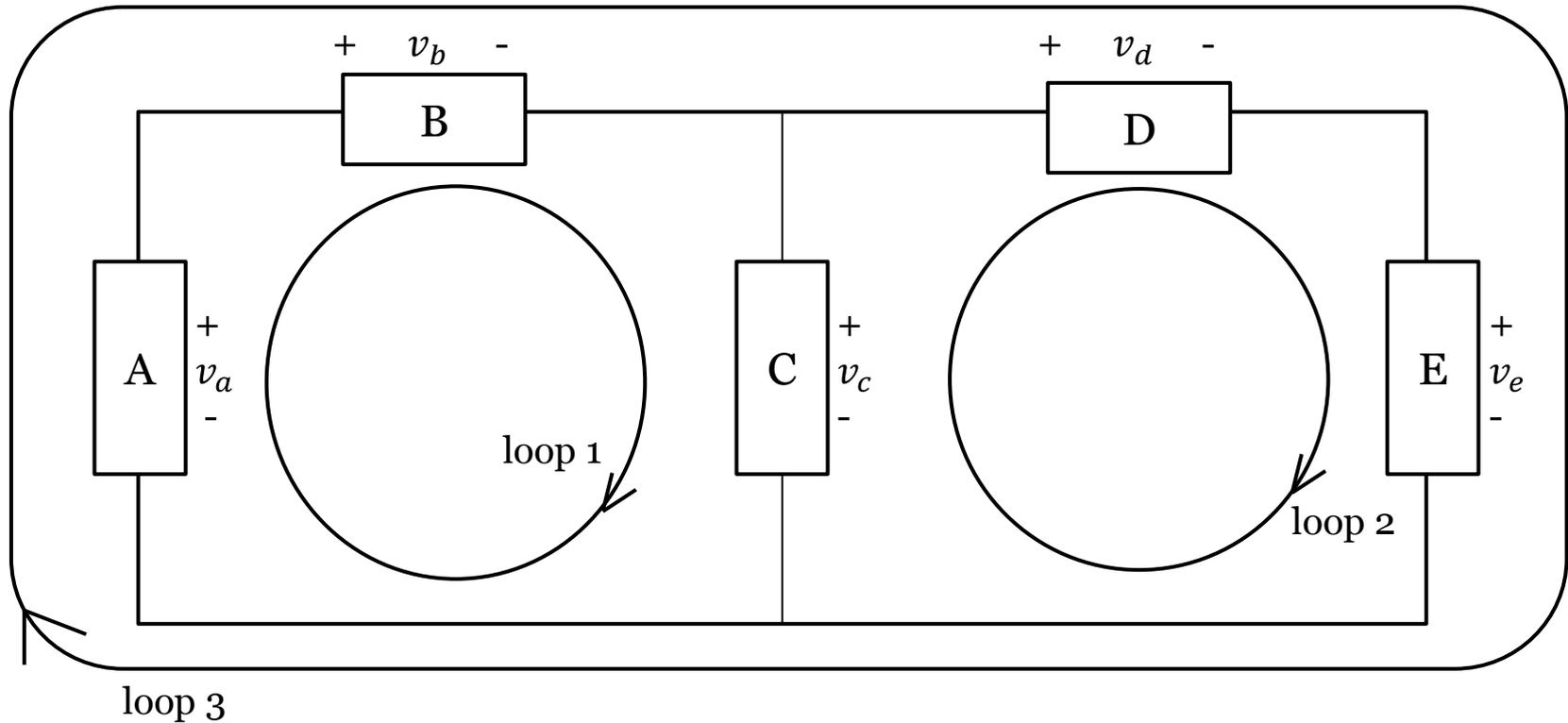

- Loop 1 $v_a - v_b - v_c = 0$
- Loop 2 $v_c - v_d - v_e = 0$
- Loop 3 $v_a - v_b - v_d - v_e = 0$

Parallel Example

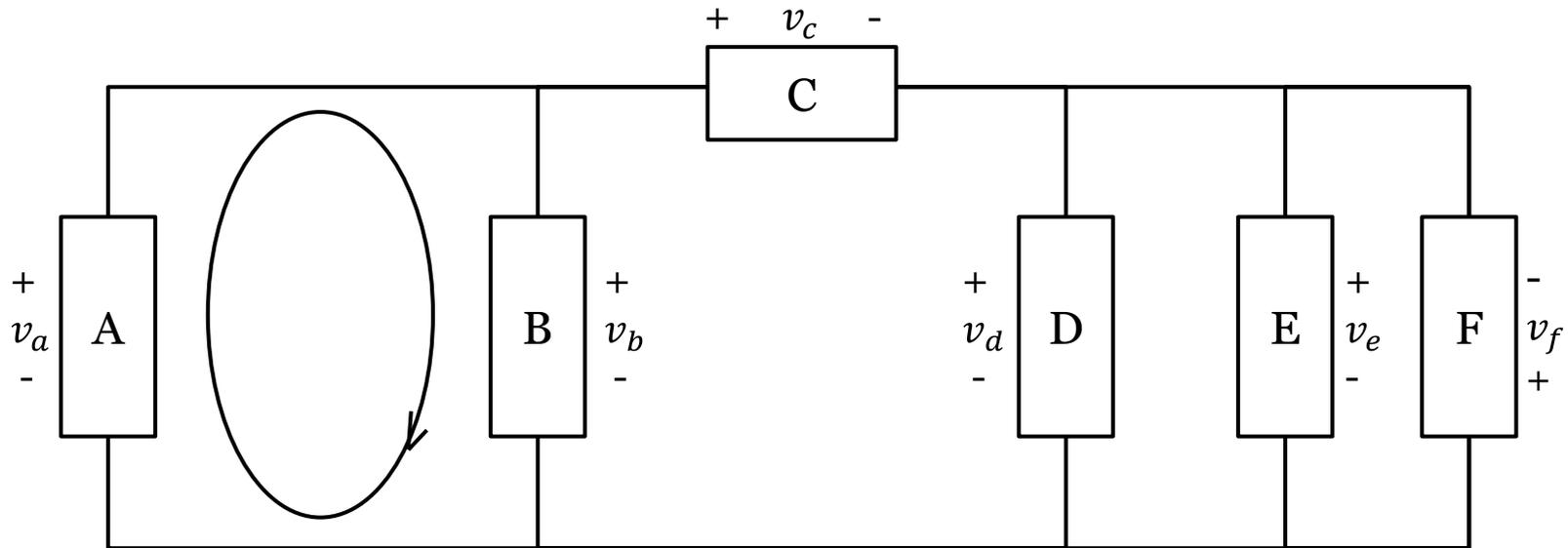

- Using KVL
 - $v_a - v_b = 0 \rightarrow v_a = v_b$
 - $v_a = v_b$ the ends are the same wire
 - $v_d = v_e = -v_f$


Conductors

- Charge carrying material
- Ideal conductors – voltage drop between ends is zero regardless of current flow
 - Think a direct connection
 - Represented by solid lines in a circuit
- “Short Circuit” – two circuit points connected by an ideal conductor
 - The points are “shorted” together
- “Open circuit” – no conducting path between two elements
 - No current flow between points

Independent Voltage Sources

- Maintains a specified voltage across its terminals independent of any other circuit elements


- Ideal sources

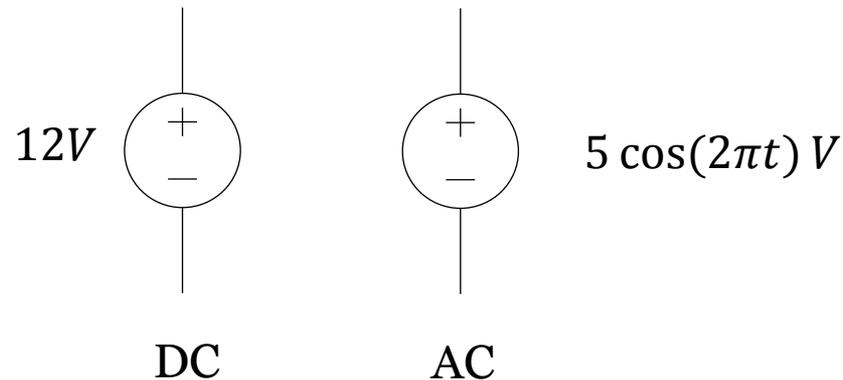

- Non-ideal source
 - Voltage not constant with current
 - Modeled as a series resistance (more later)
 - What happens if you were to put a screwdriver across the terminals of a car battery?


Dependent (Controlled) Voltage Sources

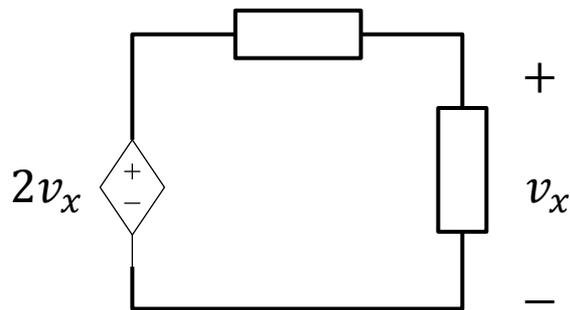- Source voltage is a function of other voltages or currents



Voltage-controlled
voltage source

$$\text{gain} = 2 \frac{V}{V}$$

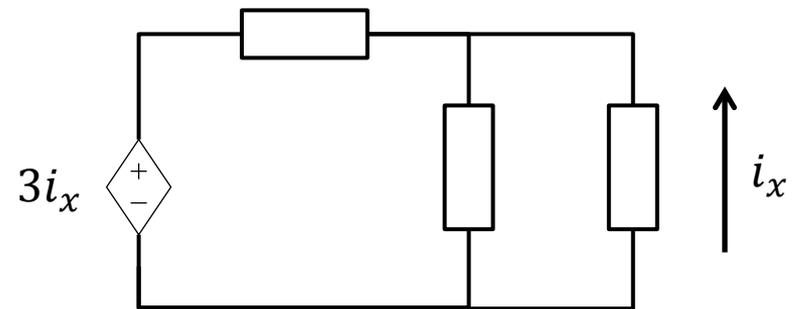


Current-controlled
voltage source

$$\text{gain} = 3 \frac{V}{A}$$

Independent Current Sources

- Maintains a fixed current through it


- Ideal sources

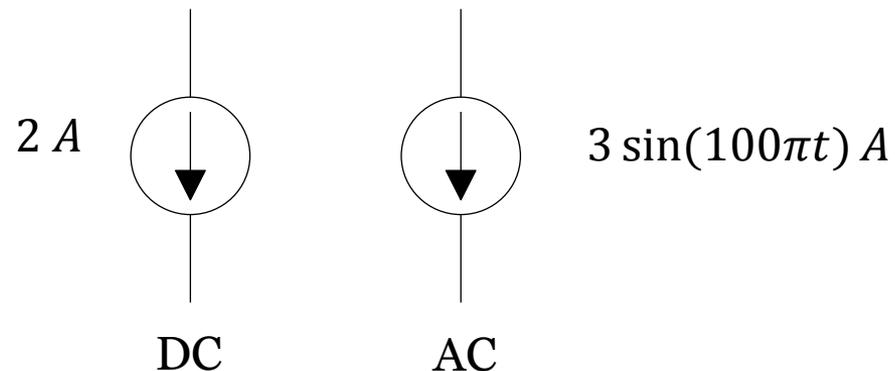

- Non-ideal source
 - Current not constant
 - Modeled as a parallel resistance (more later)


Dependent (Controlled) Current Sources

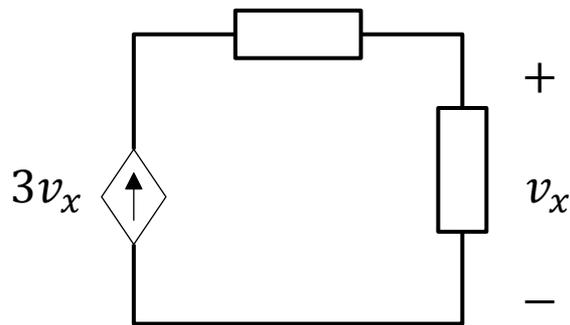- Source current is a function of other voltages or currents



Voltage-controlled
current source

$$\text{gain} = 2 \frac{A}{V}$$

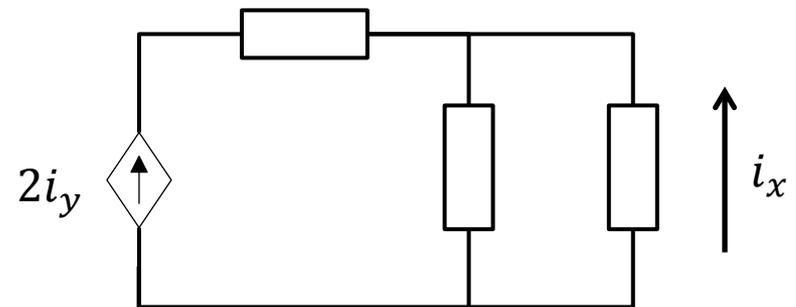


Current-controlled
current source

$$\text{gain} = 2 \frac{A}{A}$$

Resistor

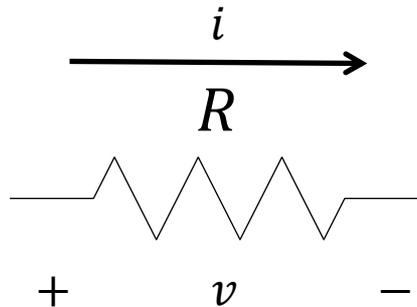- Circuit element that impedes current flow



- Ohm's Law
 - $v = iR$
- Resistance – prevents current flow
 - $R = \frac{v}{i}$ Units Ohms [$\Omega = \text{V/A}$]
- Conductance – allows current flow
 - $G = \frac{1}{R}$ Units [Ω^{-1}]

Power with Resistors

$$\begin{aligned} p &= vi & v &= iR \\ &= i^2 R \\ &= \frac{V^2}{R} = GV^2 \end{aligned}$$

- Power in a resistor is always positive \rightarrow energy is absorbed
 - A result of squared term