

EE292: Fundamentals of ECE

Fall 2012

TTh 10:00-11:15 SEB 1242

Lecture 6

120913

ENGINEERING TUTORING

Courses tutored include:

CEE – CPE – CS –EE –ME
courses + much more

MATH: 181, 182, 283, 431

PHYS: 151, 152, 180, 181

Staff

UNLV graduate & undergraduate engineering majors

*Accepting applications for new tutors this semester *

General information:

- Free drop-in lab * no appt needed
- TBE – A 207L * Next door to the advising center
- Mon-Fri 12 - 5:00pm
- Sept. 4 – Dec 7, 2012
- (702) 774-4623
- UNLV student ID required

Outline


- Review Mesh-Current Analysis
- Thevenin Equivalent Circuits
- Norton Equivalent Circuits
- Capacitance
- Inductance

Mesh-Current Analysis

- Currents around a “mesh” are unknown
 - Requires planar (non-overlapping) circuits
- Use KVL equations around a mesh

- Steps:
 1. Define mesh currents clockwise around “minimum” loops
 2. Write network KVL equations for each mesh current
 - Define current sources in terms of mesh currents
 - Shared current sources require a supermesh
 - Dependent source equations should be re-written in terms of mesh currents
 3. Put the equations into standard form and solve for the node voltages


Write KVL Equations

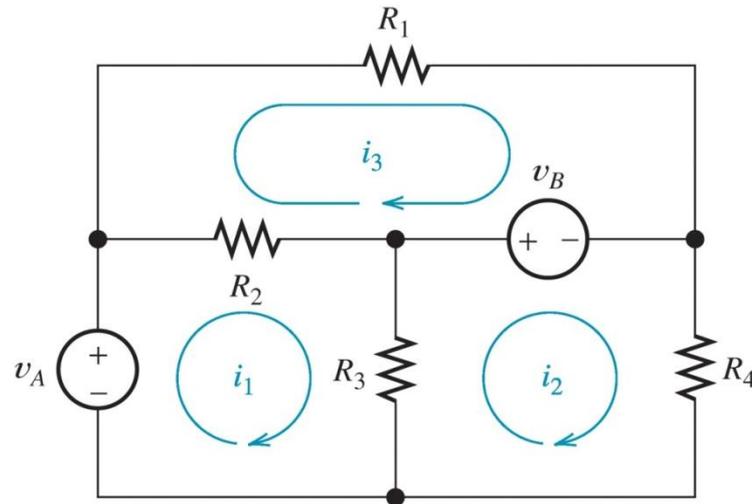


- KVL clockwise around mesh i_1
 - $v_A - (i_1 - i_3)R_2 - (i_1 - i_2)R_3 = 0$
- KVL clockwise around mesh i_2
 - $-(i_2 - i_1)R_3 - v_B - i_2R_4 = 0$
- KVL clockwise mesh i_3
 - $-i_3R_1 + v_B - (i_3 - i_1)R_2 = 0$

Supermeshes

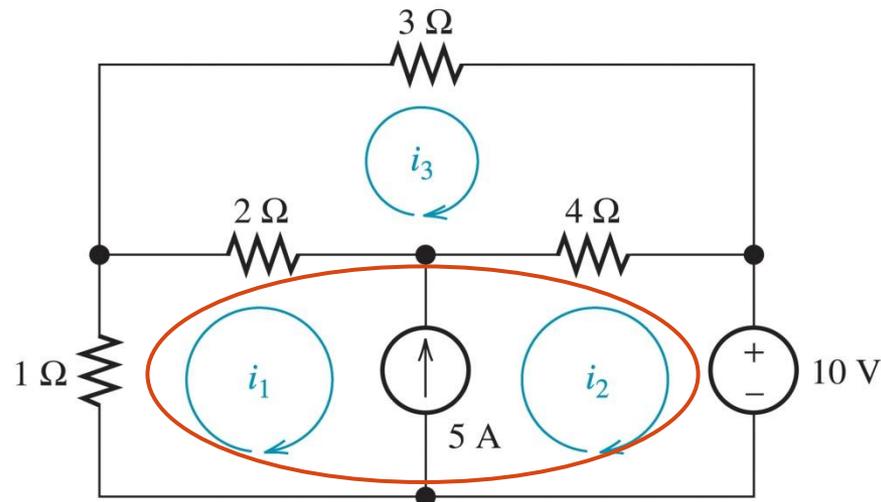- A combination of meshes useful for mesh-current analysis with shared current sources
 - Adjust KVL to get an equation around the supermesh
- Same idea as the supernode in node-voltage analysis




Example Controlled Supermesh

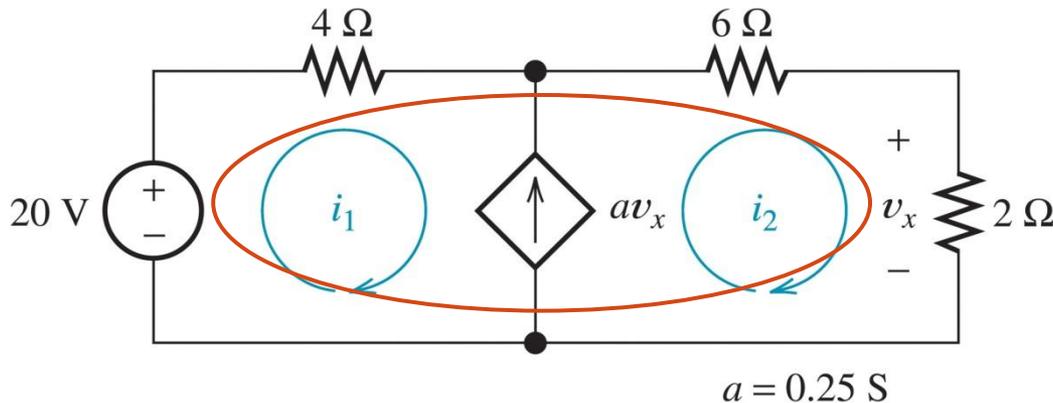

- 2 unknown mesh currents \rightarrow need 2 equations
- 1. Replace controlling variable v_x with mesh currents
 - $v_x = 2i_2$
- 2. Create supermesh because of shared current source
- 3. KVL around supermesh
 - $20 - 4i_1 - 6i_2 - 2i_2 = 0$

Example Controlled Supermesh

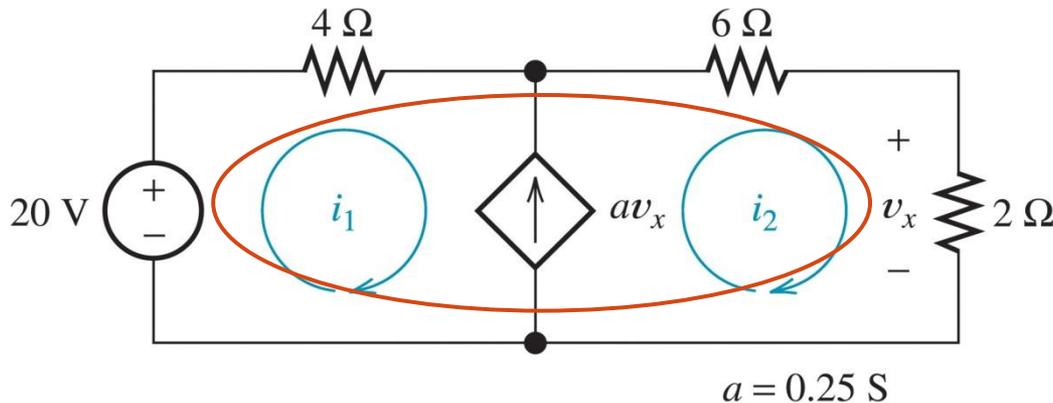


- 2 unknown mesh currents \rightarrow need 2 equations
- 4. Write (mesh) expression for the current source
 - $av_x = a(2i_2) = i_2 - i_1$
 - $(2a - 1)i_2 = -i_1$
 - $i_1 = 0.5i_2$
- 5. Plug back into KVL equation
 - $20 - 4i_1 - 6i_2 - 2i_2 = 0$
 - $20 - 4i_2/2 - 6i_2 - 2i_2 = 0$
 - $10i_2 = 20$
 - $i_2 = 2 \text{ A}$ and $i_1 = 1 \text{ A}$

Superposition Principle

- Given a circuit with multiple independent sources, the total response is the sum of the responses to each individual source
 - Requires linear dependent sources
- Analyze each independent source individually
 - Must zero out independent sources, but keep dependent sources
 - A voltage source becomes a short circuit
 - A current source becomes an open circuit




Superposition Example

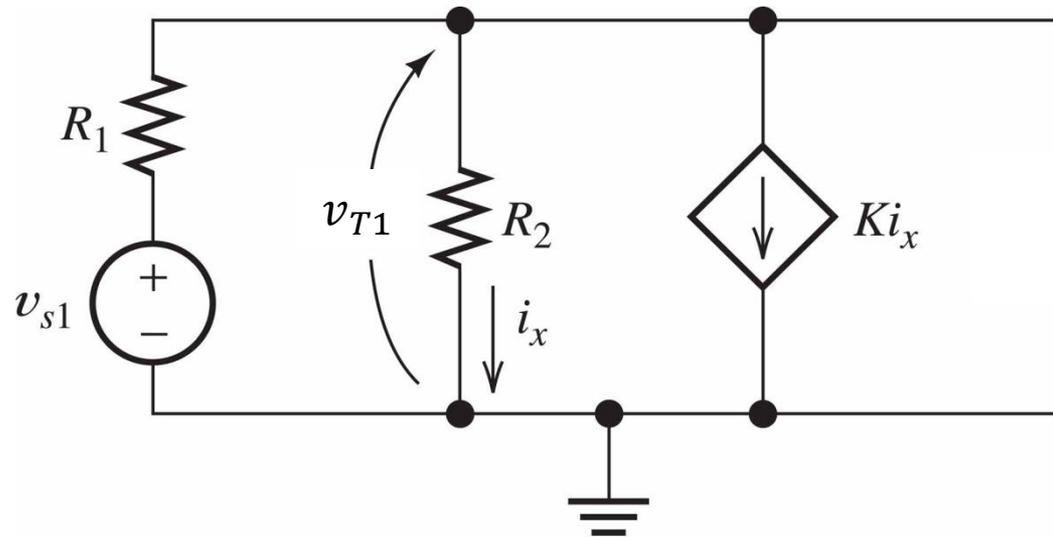


- 2 independent sources
 - Response is sum of each source response
 - $v_T = v_{T1} + v_{T2}$

Superposition Example

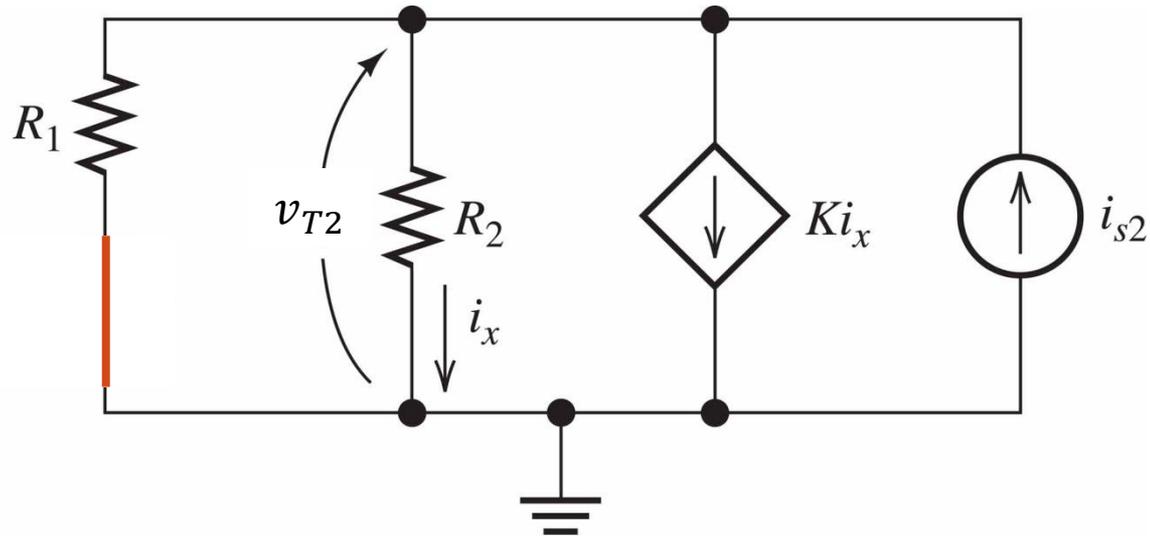


- 2 independent sources
 - Response is sum of each source response
 - $v_T = v_{T1} + v_{T2}$

Thevenin Equivalent Circuit

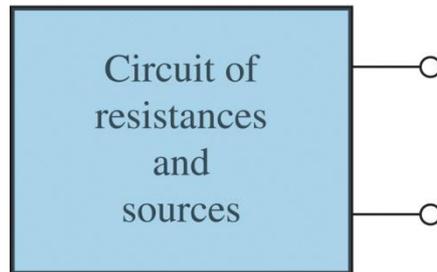

- Equivalent circuit consisting of a voltage source in series with a resistance
 - View the circuit from two terminals
- We care about three things
 - Open circuit voltage
 - Short circuit current
 - Equivalent resistance


Open Circuit Voltage

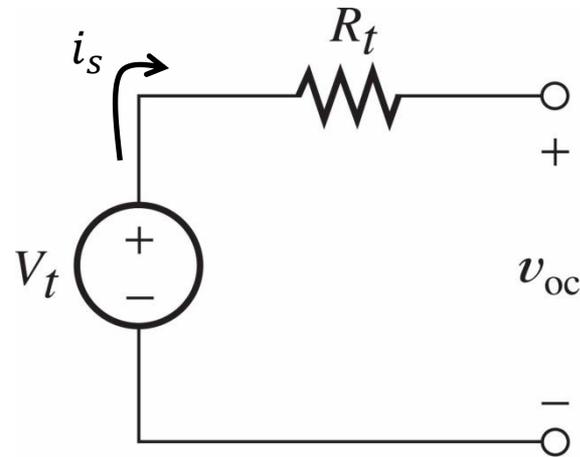

Copyright © 2011, Pearson Education, Inc.

- Open circuit means terminal unconnected
 - No current flows through R_t
- Using KVL
 - $V_t - i_s R_t - v_{oc} = 0$
 - $i_s = 0$
 - $V_t = v_{oc}$

Short Circuit Current

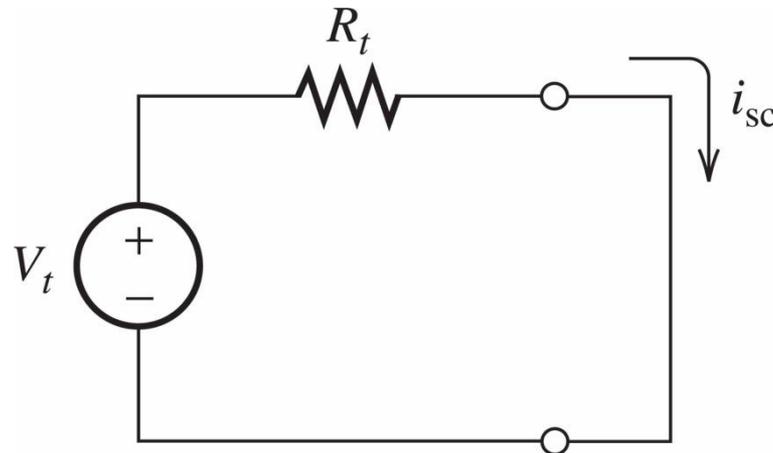

Copyright © 2011, Pearson Education, Inc.

- Short circuit uses a wire to connect the terminals
 - Current flows through series resistor
- Current is a function of Thevenin source voltage and resistance
 - $i_{sc} = \frac{V_t}{R_t}$


Thevenin Equivalent Resistance

- Equivalent resistance is computed using Ohm's Law
 - Use the open source voltage and short circuit voltage
 - $R_t = \frac{v_{oc}}{i_{sc}} = \frac{V_t}{i_{sc}}$
- Find two of v_{oc} , i_{sc} , or R_t to define the Thevenin equivalent circuit

Compute R_t Directly


- Possible only when there are no dependent sources present in network
- Steps:
 1. Zero out independent sources
 - Short voltage sources
 - Open current sources
 2. Compute R_t by series/parallel equivalent steps

Example

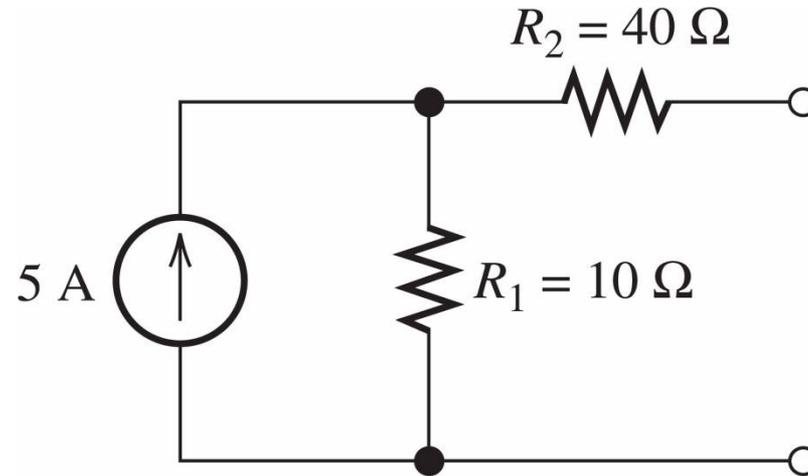


- Find Thevenin equivalent
 1. Find short circuit current
 2. Find open circuit voltage
 3. Solve for equivalent resistance

Example: Short Circuit Current

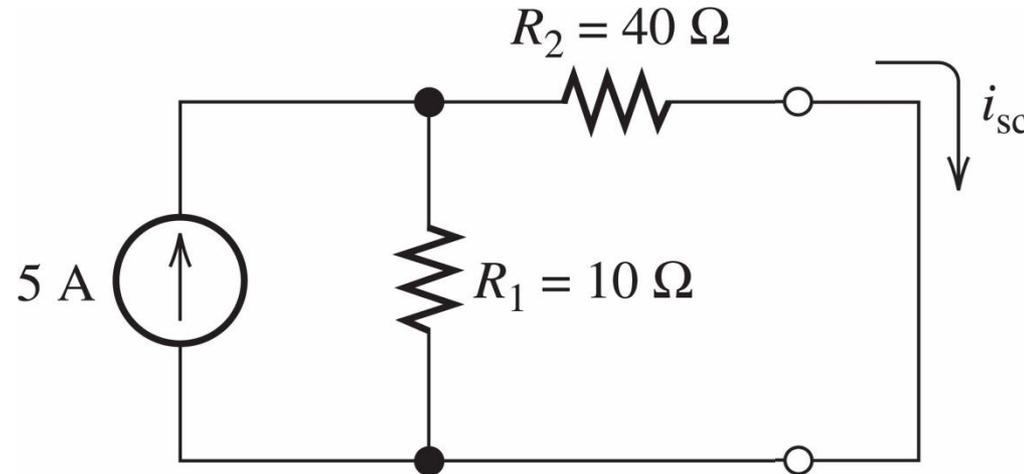


1. Find short circuit current i_{sc}
 - Notice this is a parallel current divider
 - Opposite resistor over sum of resistances
 - $i_{sc} = i_s \left(\frac{R_1}{R_1 + R_2} \right)$
 - $i_{sc} = 5 \left(\frac{10}{10 + 40} \right) = 1 \text{ A}$

Example: Open Circuit Voltage

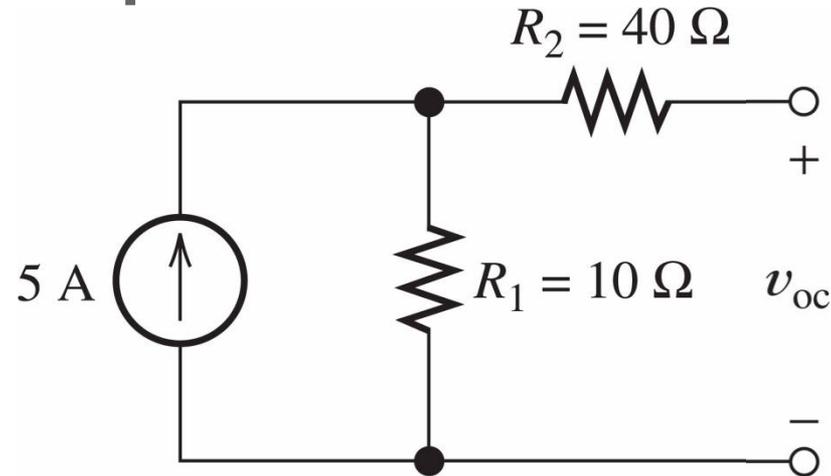


2. Find open circuit voltage v_{oc}
 - Notice there is no current through R_2
 - $v_{oc} = i_s R_1$
 - $v_{oc} = 5 \cdot 10 = 50 \text{ V}$

Example: Thevenin Resistance

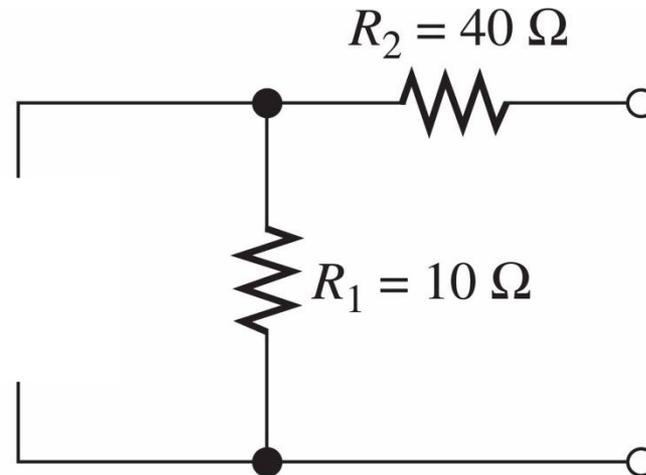


3. Solve for equivalent resistance R_t
 - Ohm's Law
 - $R_t = \frac{v_{oc}}{i_{sc}} = \frac{50}{1} = 50\ \Omega$
- Direct calculation of equivalent resistance
 - Zero sources \rightarrow open current source
 - Notice series connection
 - $R_t = R_1 + R_2 = 50\ \Omega$

Example: Thevenin Equivalent

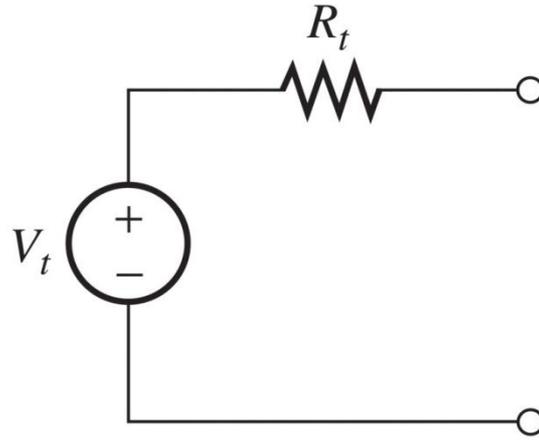

- Replace original circuit with equivalent
 - $v_{oc} = 50 \text{ V}$
 - $R_t = 50 \Omega$

Norton Equivalent Circuit

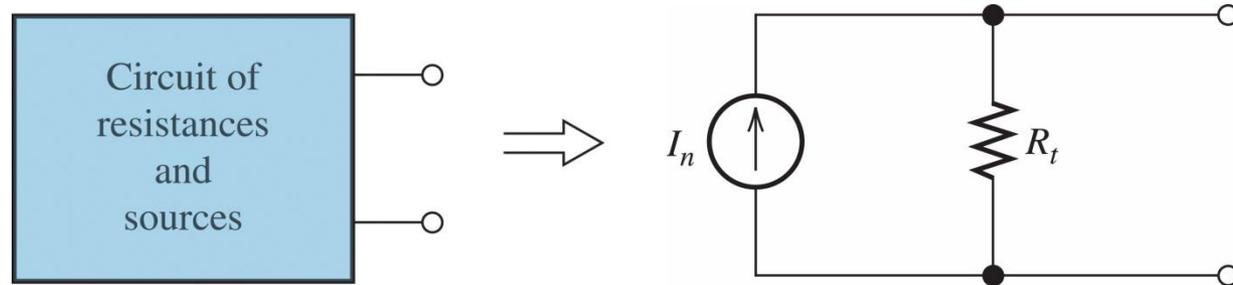


- Equivalent circuit consisting of a current source in parallel with a resistance
- The same idea as Thevenin
 - Open circuit voltage
 - Short circuit current
 - Equivalent resistance


$$v_{oc} = I_n R_t$$

$$i_{sc} = I_n$$

$$R_t = \frac{v_{oc}}{i_{sc}}$$

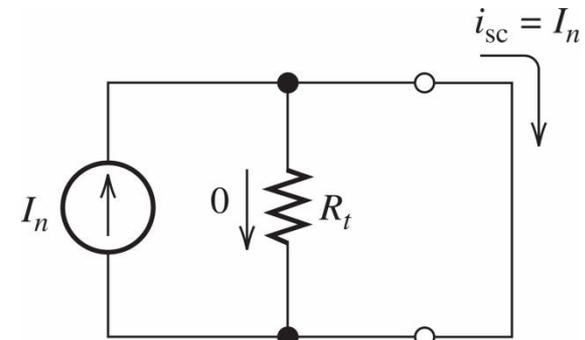


Example: Norton Equivalent

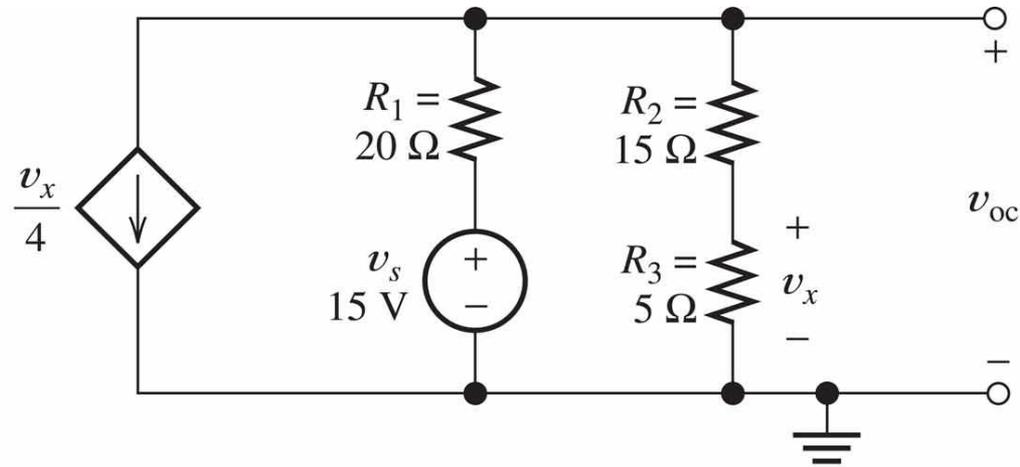


- Need to find v_{oc} and i_{sc}
 - Cannot get the equivalent Norton resistance directly because of the dependent source

Example: Norton Open Circuit

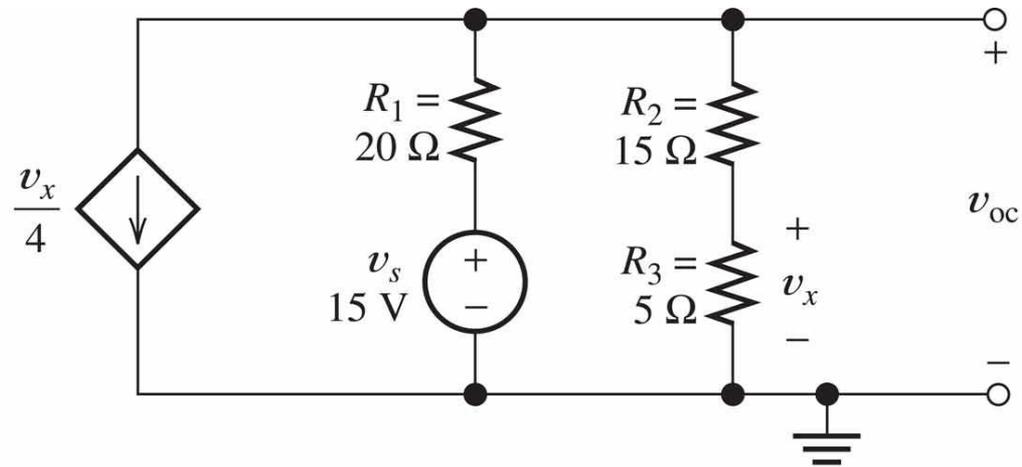


- Express dependent source in terms of voltages
 - Notice the voltage divider
 - $v_x = v_{oc} \left(\frac{R_3}{R_2 + R_3} \right) = v_{oc} \left(\frac{5}{15 + 5} \right) = \frac{v_{oc}}{4}$
- Find v_{oc} with KCL @ top of circuit (node-voltage)
 - $\frac{v_x - 0}{4} + \frac{v_{oc} - v_s}{R_1} + \frac{v_{oc} - 0}{R_2 + R_3} = 0$

Example: Norton Open Circuit

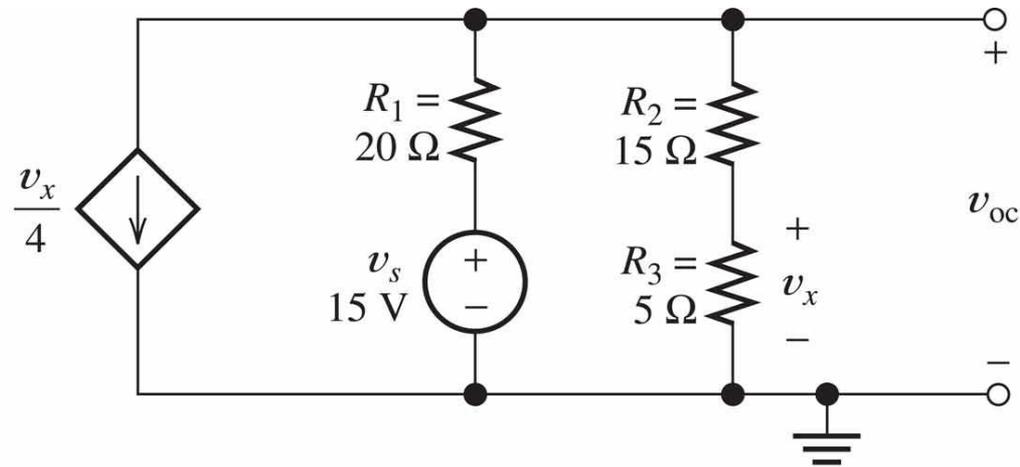


- Find v_{oc} with KCL @ top of circuit (node-voltage)
 - $\frac{v_x - 0}{4} + \frac{v_{oc} - v_s}{R_1} + \frac{v_{oc} - 0}{R_2 + R_3} = 0$
 - $\frac{v_{oc}/4}{4} + \frac{v_{oc} - 15}{20} + \frac{v_{oc}}{20} = 0$
- After rearranging
 - $v_{oc} = \frac{60}{13} \text{ V}$

Example: Norton Short Circuit

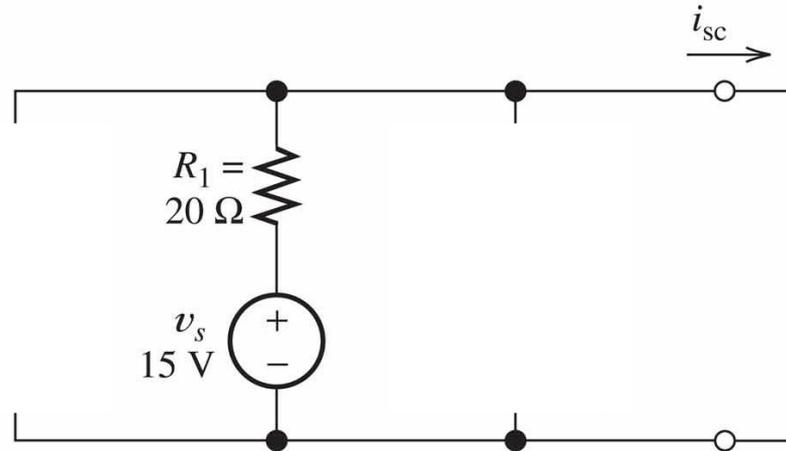

- Find i_{sc} with KCL @ top of circuit (node-voltage)
 - No current through $R_2 + R_3$
 - $v_x = 0$
 - Dependent source is zero \rightarrow open circuit
 - $i_{sc} = \frac{v_s}{R_1} = \frac{15}{20} = \frac{3}{4}\ A$

Example: Norton Equivalent Resistance

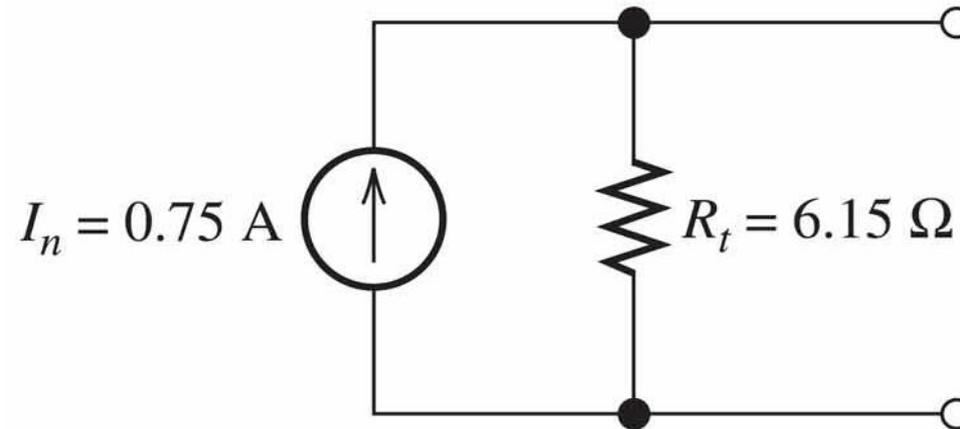

- Find Norton equivalent resistance R_t
 - Ohm's Law
 - $R_t = \frac{v_{oc}}{i_{sc}} = \frac{60}{13} \left(\frac{4}{3} \right) = \frac{240}{39} = 6.15 \Omega$

Chapter 3: Inductance & Capacitance

- Inductors, capacitors are energy-storage devices.
- They are passive elements because they don't generate energy
 - Only energy put in can be later extracted.
- **Capacitance:** circuit property to deal with energy in electric fields
- **Inductance:** circuit property to deal with energy in magnetic fields