

EE292: Fundamentals of ECE

Fall 2012

TTh 10:00-11:15 SEB 1242

Lecture 7

120918

ENGINEERING TUTORING

Courses tutored include:

CEE – CPE – CS –EE –ME
courses + much more

MATH: 181, 182, 283, 431

PHYS: 151, 152, 180, 181

Staff

UNLV graduate & undergraduate engineering majors

*Accepting applications for new tutors this semester *


General information:

- Free drop-in lab * no appt needed
- TBE – A 207L * Next door to the advising center
- Mon-Fri 12 - 5:00pm
- Sept. 4 – Dec 7, 2012
- (702) 774-4623
- UNLV student ID required

Outline

- Review Thevenin/Norton Equivalent Circuits
- Capacitance
- Inductance

Thevenin/Norton Equivalent Circuit

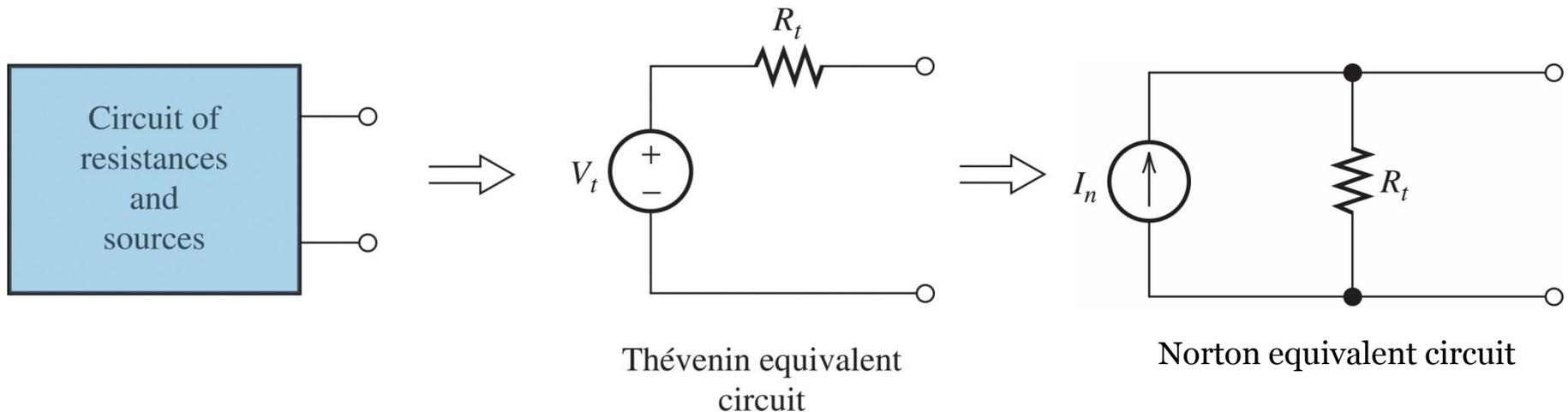



- View circuit from two terminals
 - Thevenin equivalent circuit consists of a voltage source in series with a resistance
 - Norton equivalent circuit consists of a current source in parallel with a resistance
- We care about three things
 - Open circuit voltage
 - Short circuit current
 - Equivalent resistance (same value for both)
- It is possible to switch between Thevenin and Norton easily

Chapter 3: Inductance & Capacitance

- Inductors, capacitors are energy-storage devices.
- They are passive elements because they don't generate energy
 - Only energy put in can be later extracted.
- **Capacitance:** circuit property to deal with energy in electric fields
- **Inductance:** circuit property to deal with energy in magnetic fields

Capacitance

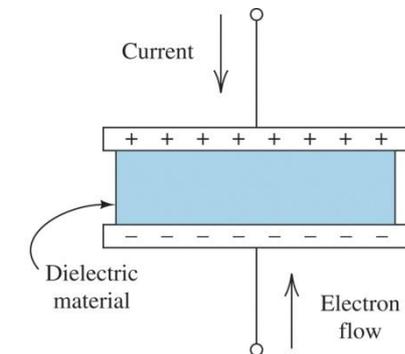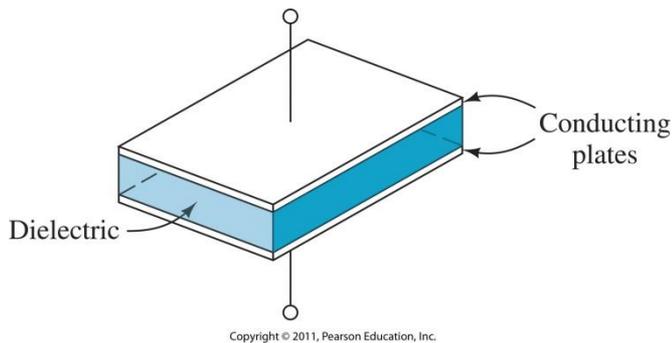- Capacitors are two conductors separated by a dielectric
 - Dielectric – an insulator which does not allow charge to flow through like a conductor



(a) As current flows through a capacitor, charges of opposite signs collect on the respective plates

- Charge accumulates on either side of the capacitor and creates an electric field in the dielectric.
 - A voltage forms across dielectric

Charge/Voltage Relationship

- The stored charge in a capacitor is proportional to voltage

$$q = Cv$$

$$\underbrace{\hspace{10em}}_{\text{Capacitance with units Farads } (F) = \frac{C}{V}}$$

- Normal range we encounter is:

$$F = [1pF, \quad 0.01 F]$$

Current/Voltage Relationship

- Since $i = \frac{dq}{dt}$ and $q = Cv$


$$\frac{dq}{dt} = \frac{d}{dt} Cv \quad \Rightarrow \quad i = C \frac{dv}{dt}$$

↑ ↑
Not a function of time

Constant voltage → no current → “open” circuit

Passive Reference Configuration

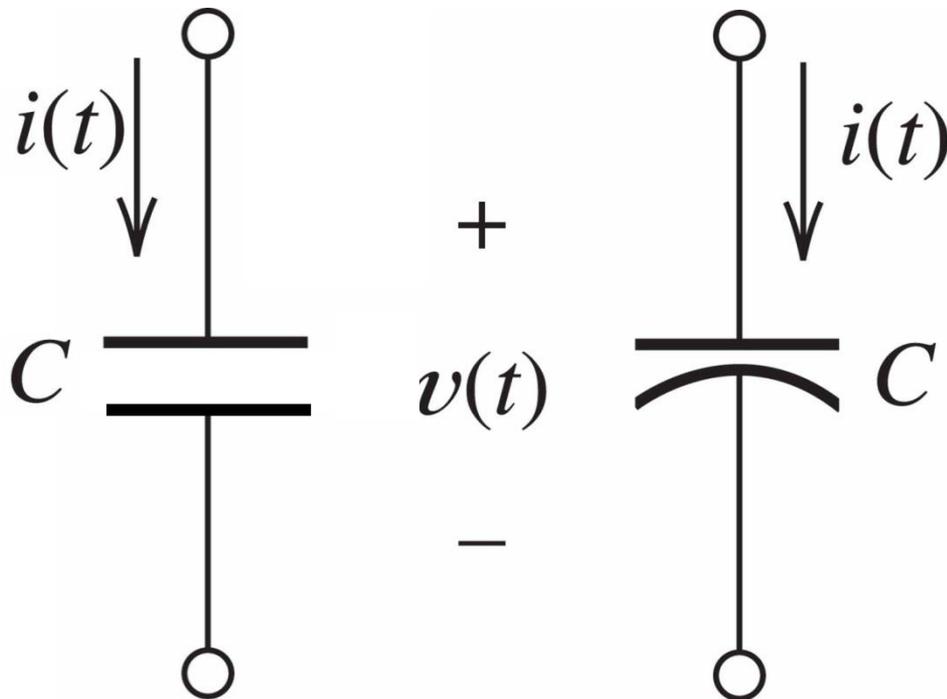
- Circuit symbol of capacitor
 - Sometimes with flat plates and other times with a curve



Curved capacitor is used for electrolytic capacitors which have explicit terminal polarity

- Flat = positive
- Curved = negative

Non-Passive Reference

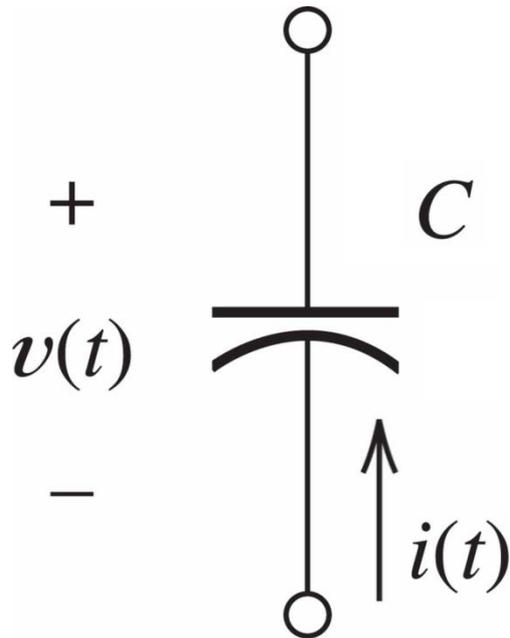

Current into negative terminal

$$\rightarrow i = -C \frac{dv}{dt}$$

Voltage from Current

- Since $i = \frac{dq}{dt}$ and $q = Cv$

- $q(t) = \int i(t) dt = Cv$

$$\Rightarrow v = \frac{1}{C} \int i(t) dt$$

$$= \frac{1}{C} \int_{t_0}^t i(t) dt + \underbrace{v(t_0)}$$

Initial voltage a time t_0

If $v(t_0) = 0 \Rightarrow$ capacitor uncharged

Power/Energy in a Capacitor

- In passive configuration (current into positive terminal)


- Power

- $p(t) = v(t) i(t)$
 - $= v(t) C \frac{dv}{dt}$

- Energy


- $w(t) = \int_{t_0}^t p(t) dt = \int_{t_0}^t C v(t) \frac{dv}{dt} dt$
 - $= \int_0^{v(t)} C v(t) dv$
 - $= \frac{1}{2} C v^2(t) \quad \leftarrow \text{for initially charged capacitor}$

Capacitances in Parallel

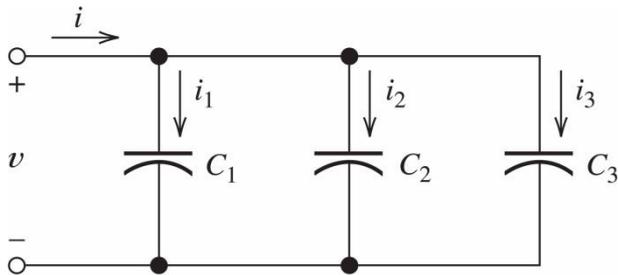

- By KCL


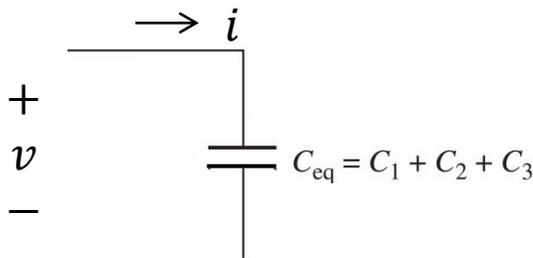
$$\begin{aligned}
 \square \quad i &= i_1 + i_2 + i_3 \\
 \square \quad &= C_1 \frac{dv}{dt} + C_2 \frac{dv}{dt} + C_3 \frac{dv}{dt} \\
 \square \quad &= \underbrace{(C_1 + C_2 + C_3)}_{C_{eq}} \frac{dv}{dt} = C_{eq} \frac{dv}{dt}
 \end{aligned}$$



Capacitance adds in parallel

Capacitances in Series

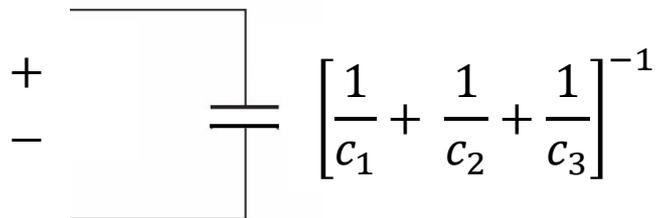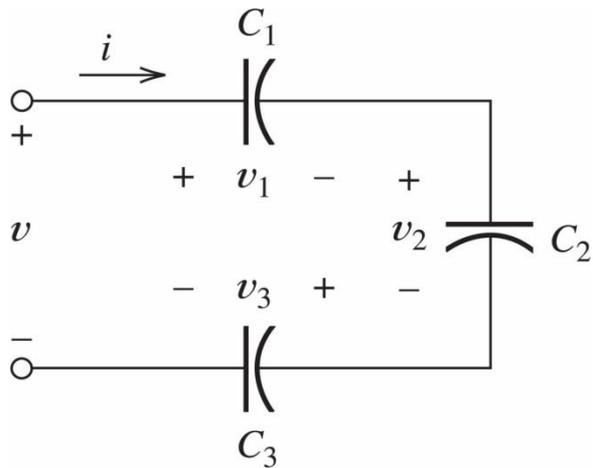- Series connection so i flows through each capacitor



KVL


$$v - v_1 - v_2 - v_3 = 0$$

$$\begin{aligned} i &= C_{eq} \frac{d}{dt} (v_1 + v_2 + v_3) \\ &= C_{eq} \left(\frac{dv_1}{dt} + \frac{dv_2}{dt} + \frac{dv_3}{dt} \right) \\ &= C_{eq} \left(\frac{i}{c_1} + \frac{i}{c_2} + \frac{i}{c_3} \right) \\ &= i C_{eq} \left(\frac{1}{c_1} + \frac{1}{c_2} + \frac{1}{c_3} \right) \end{aligned}$$


$$\Rightarrow C_{eq} = \frac{1}{\frac{1}{c_1} + \frac{1}{c_2} + \frac{1}{c_3}}$$

Inductance

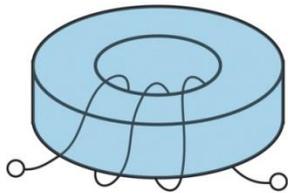
- Device to store energy in a magnetic field
 - Often made from wire wrapped around a magnetic material
 - Current through the coil induces a magnetic field in the material



(a) Toroidal inductor

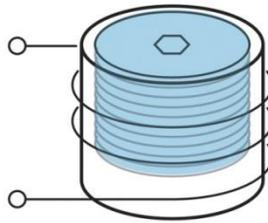


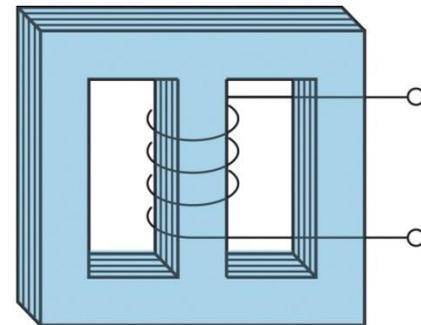(b) Coil with an iron-oxide slug that can be screwed in or out to adjust the inductance



(c) Inductor with a laminated iron core

Inductor

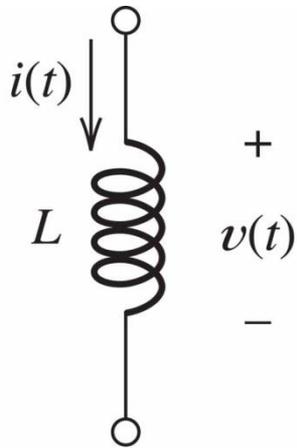

$$v(t) = L \frac{di}{dt}$$

- $v(t) = L \frac{di}{dt}$ passive reference configuration

- Has units of henries [$H = V \text{ sec}/A$]
- In range μH to H

Current in terms of Voltage

- $i(t) = \frac{1}{L} \int_{t_0}^t v(t) dt + \underbrace{i(t_0)}$
 - Initial current
 - If $i(t_0) = 0 \Rightarrow$ inductor stores no energy

Power/Energy in an inductor


- Power

- $p(t) = v(t) i(t)$
 - $= L \frac{di}{dt} i(t)$

- Energy

- $w(t) = \int_{t_0}^t p(t) dt = \int_{t_0}^t Li(t) \frac{di}{dt} dt$
 - $= \int_0^{i(t)} Li(t) di$
 - $= \frac{1}{2} Li^2(t) \quad \leftarrow \text{for no initial energy}$

Inductors in Series

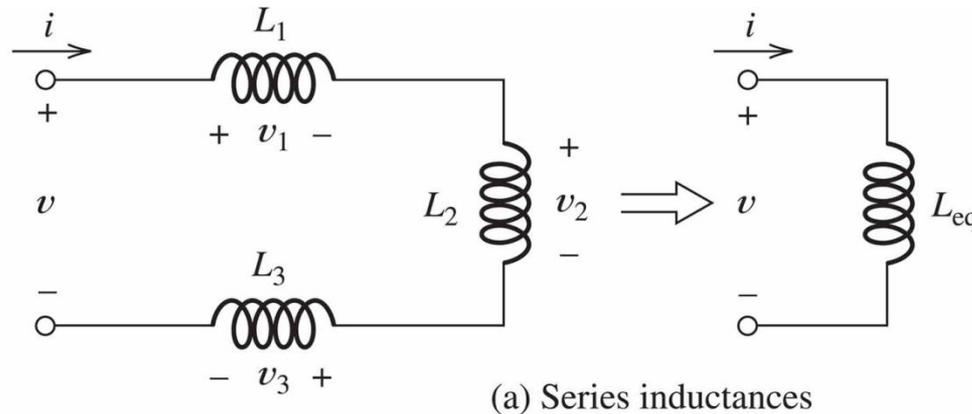

- Using KVL


- $v - v_1 - v_2 - v_3 = 0$

- $v = L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + L_3 \frac{di}{dt}$

- $= \underbrace{(L_1 + L_2 + L_3)}_{L_{eq}} \frac{di}{dt} = L_{eq} \frac{di}{dt}$

Inductors add in series (like resistors)

Inductors in Parallel

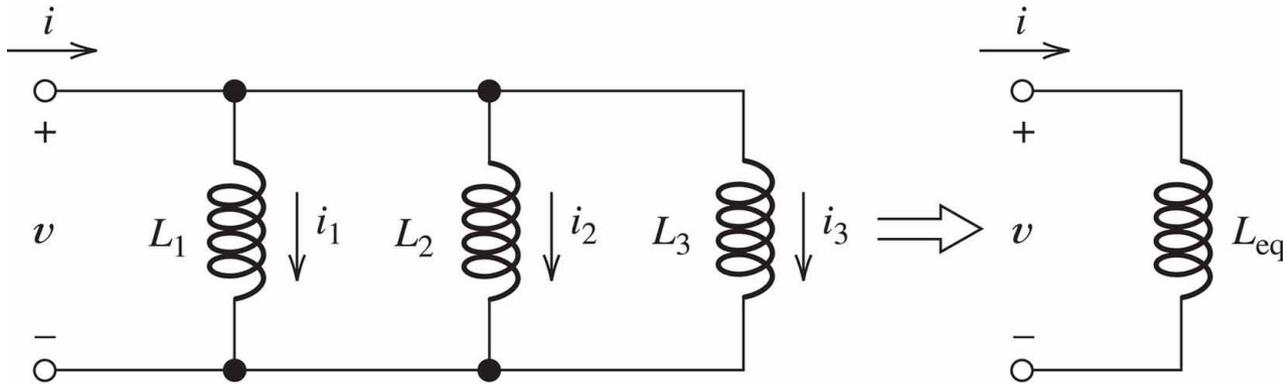

(b) Parallel inductances

$$i = i_1 + i_2 + i_3$$

$$v = L_1 \frac{di_1}{dt} = L_2 \frac{di_2}{dt} = L_3 \frac{di_3}{dt}$$

$$\begin{aligned} v &= L_{eq} \frac{di}{dt} = L_{eq} \frac{d}{dt} (i_1 + i_2 + i_3) \\ &= L_{eq} \left(\frac{di_1}{dt} + \frac{di_2}{dt} + \frac{di_3}{dt} \right) \\ &= L_{eq} \left(\frac{i}{vL_1} + \frac{i}{vL_2} + \frac{i}{vL_3} \right) \\ &= vL_{eq} \left(\frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} \right) \end{aligned}$$

$$\Rightarrow L_{eq} = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}}$$