

# EE292: Fundamentals of ECE

Fall 2012

TTh 10:00-11:15 SEB 1242

Lecture 16

121018

<http://www.ee.unlv.edu/~b1morris/ee292/>

# Outline

- Review
  - 1<sup>st</sup>-Order Transients
  - General Sources
  - 2<sup>nd</sup>-Order Circuits

# General 1<sup>st</sup>-Order Solution

- Both the current and voltage in an 1<sup>st</sup>-order circuit has an exponential form
  - RC and LR circuits


- The general solution for current/voltage is:

$$x(t) = x_f + [x(t_0^+) - x_f] e^{-(t-t_0)/\tau}$$

- $x$  – represents current or voltage
  - $t_0$  – represents time when source switches
  - $x_f$  - final (asymptotic) value of current/voltage
  - $\tau$  – time constant ( $RC$  or  $\frac{L}{R}$ )
- Find values and plug into general solution
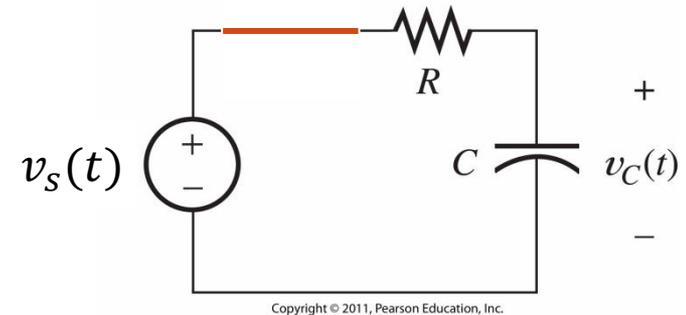
# RC/RL Circuits with General Sources

- Previously,
  - $RC \frac{dv_c(t)}{dt} + v_c(t) = V_s$
- What if  $V_s$  is not constant
  - $RC \frac{dv_c(t)}{dt} + v_c(t) = v_s(t)$
  - Now have a general source that is a function of time
- The solution is a differential equation of the form
  - $\tau \frac{dx(t)}{dt} + x(t) = f(t)$
  - Where  $f(t)$  is known as the forcing function (the circuit source)



# General Differential Equations

- General differential equation
  - $\tau \frac{dx(t)}{dt} + x(t) = f(t)$
- The full solution to the diff equation is composed of two terms
  - $x(t) = x_p(t) + x_h(t)$
- $x_p(t)$  is the particular solution
  - The response to the particular forcing function
- $x_h(t)$  is the homogeneous solution
  - Another solution that is consistent with the differential equation for  $f(t) = 0$
  - The response to any initial conditions of the circuit

# Particular Solution



- $\tau \frac{dx_p(t)}{dt} + x_p(t) = f(t)$
- The solution  $x_p(t)$  is called the forced response because it is the response of the circuit to a particular forcing input  $f(t)$
- The solution  $x_p(t)$  will be of the same functional form as the forcing function
  - E.g.
  - $f(t) = e^{st} \rightarrow x_p(t) = Ae^{st}$
  - $f(t) = \cos(\omega t) \rightarrow x_p(t) = A\cos(\omega t) + B\sin(\omega t)$

# Homogeneous Solution

- $\tau \frac{dx_h(t)}{dt} + x_h(t) = 0$
- $x_h(t)$  is the solution to the differential equation when there is no forcing function
  - Does not depend on the sources
  - Dependent on initial conditions (capacitor voltage, current through inductor)
- $x_h(t)$  is also known as the natural response
- Solution is of the form
  - $x_h(t) = K e^{-t/\tau}$

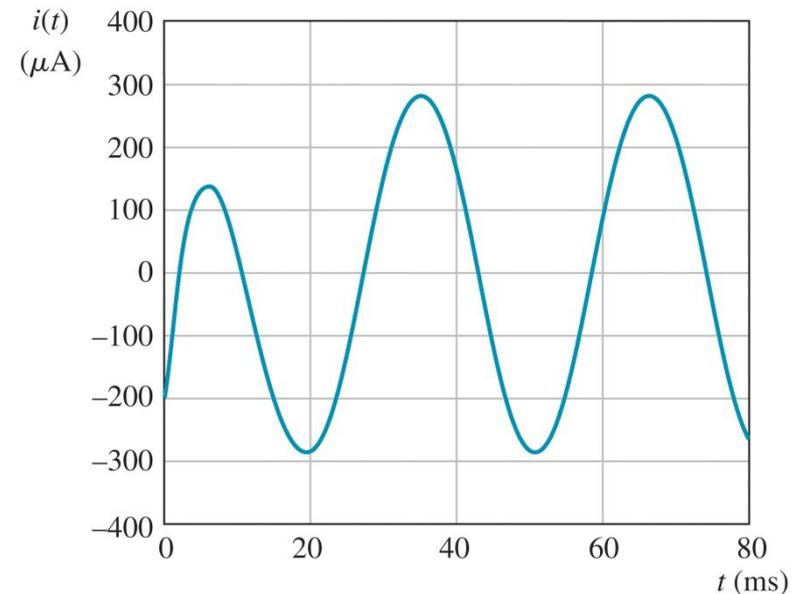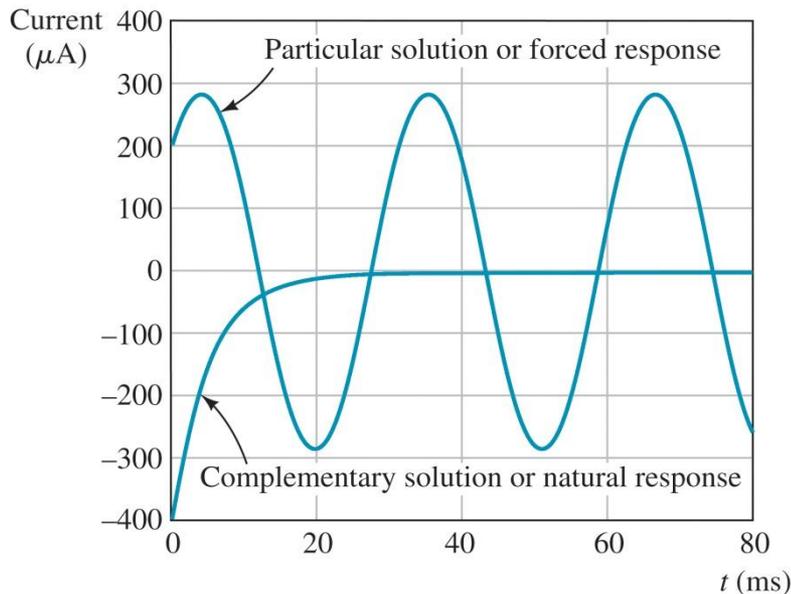
# General Differential Solution

- Notice the final solution is the sum of the particular and homogeneous solutions
  - $x(t) = x_p(t) + x_h(t)$
- It has an exponential term due to  $x_h(t)$  and a term  $x_p(t)$  that matches the input source



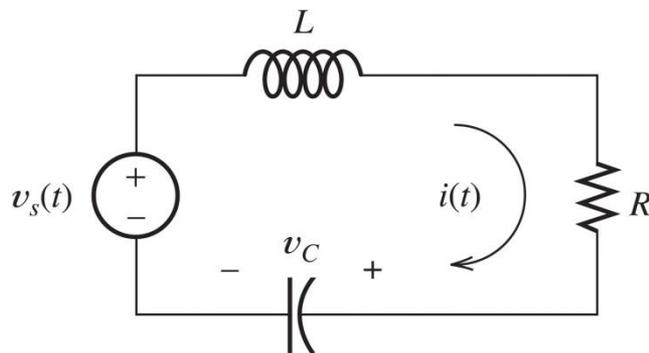
# Second-Order Circuits

- RLC circuits contain two energy storage elements
  - This results in a differential equation of second order (has a second derivative term)
- This is like a mass spring system from physics




(a) Electrical circuit

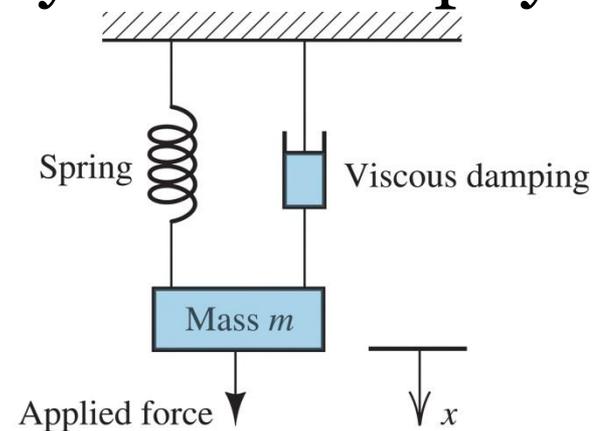

(b) Mechanical analog

# RLC Series Circuit

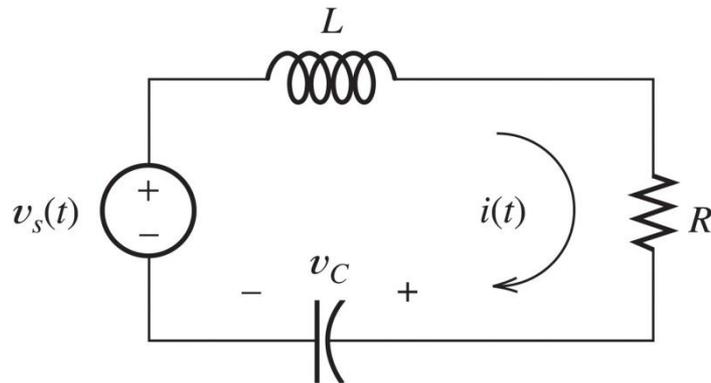

- KVL around loop
  - $v_s(t) - L \frac{di(t)}{dt} - i(t)R - v_c(t) = 0$
- Solve for  $v_c(t)$ 
  - $v_c(t) = v_s(t) - L \frac{di(t)}{dt} - i(t)R$
- Take derivative
  - $\frac{dv_c(t)}{dt} = \frac{dv_s(t)}{dt} - L \frac{d^2i(t)}{dt^2} - R \frac{di(t)}{dt}$

- Solve for current through capacitor

- $i(t) = C \frac{dv_c(t)}{dt}$

- $i(t) = C \left[ \frac{dv_s(t)}{dt} - L \frac{d^2i(t)}{dt^2} - R \frac{di(t)}{dt} \right]$


- $\frac{d^2i(t)}{dt^2} + \frac{R}{L} \frac{di(t)}{dt} + \frac{1}{LC} i(t) = \frac{1}{L} \frac{dv_s(t)}{dt}$

- The general 2<sup>nd</sup>-order constant coefficient equation

$$\frac{di^2(t)}{dt^2} + 2\alpha \frac{di(t)}{dt} + \omega_0^2 i(t) = f(t)$$

$$\alpha = \frac{R}{2L}, \quad \omega_0 = \frac{1}{\sqrt{LC}}, \quad f(t) = \frac{1}{L} \frac{dv_s(t)}{dt}$$

# Circuits with Parallel L and C

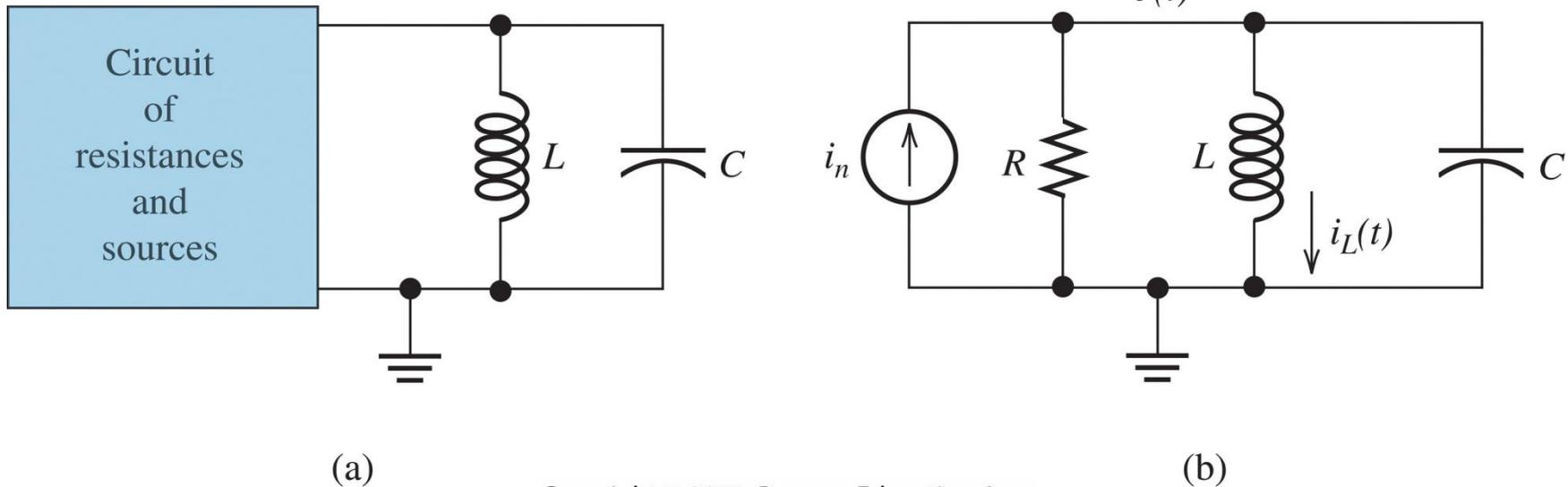

Copyright © 2011, Pearson Education, Inc.


- Given a circuit with a parallel capacitor and inductor
  - Use Norton equivalent to make a parallel circuit equivalent

# Circuits with Parallel L and C

- Find current in inductor  $i_L(t)$
- KCL @ top node
- $$i_n(t) = \frac{v(t)}{R} + i_L(t) + C \frac{dv(t)}{dt}$$
- $$i_n(t) = \frac{L}{R} \frac{di(t)}{dt} + i(t) + CL \frac{d^2i(t)}{dt^2}$$
- $$\frac{d^2i(t)}{dt^2} + \frac{1}{RC} \frac{di(t)}{dt} + \frac{1}{LC} i(t) = \frac{1}{CL} i_n(t)$$

$$\frac{di^2(t)}{dt^2} + 2\alpha \frac{di(t)}{dt} + \omega_0^2 i(t) = f(t)$$

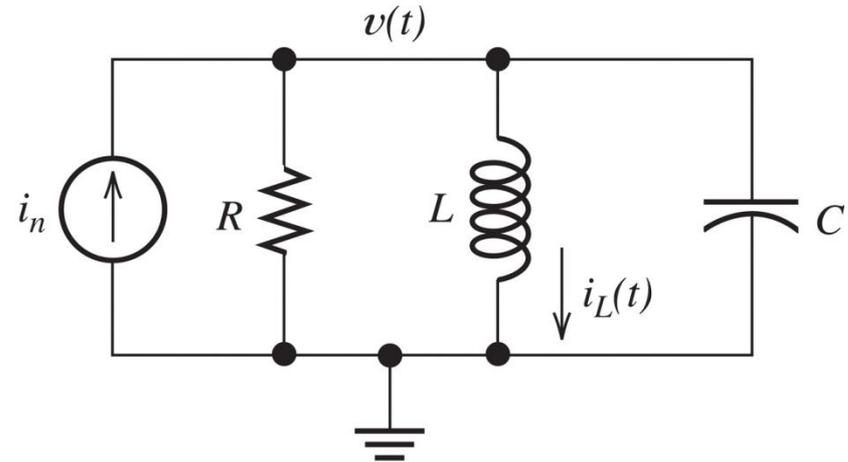
- $$f(t) = \frac{1}{LC} i_n(t)$$
- $$\alpha = \frac{1}{2RC}$$
- $$\omega_0 = \sqrt{\frac{1}{LC}}$$



- $$v(t) = L \frac{di(t)}{dt}$$
- $$\frac{dv(t)}{dt} = L \frac{d^2i(t)}{dt^2}$$
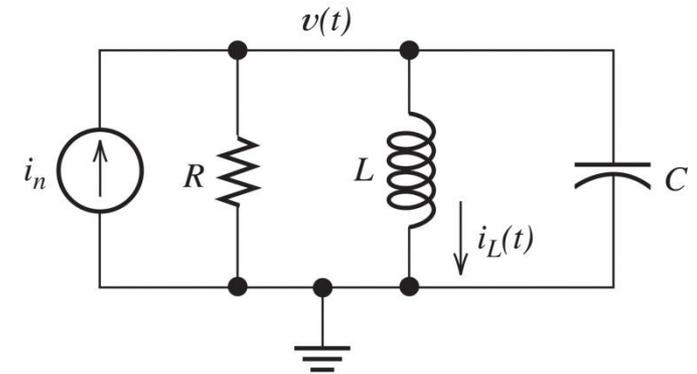
# Circuits with Parallel L and C

- Find parallel voltage  $v(t)$
- KCL @ top node
- $i_n(t) = \frac{v(t)}{R} + i_L(t) + C \frac{dv(t)}{dt}$
- $i_n(t) = \frac{v(t)}{R} + \frac{1}{L} \int_{t_0}^t v(t) dt + i(t_0) + C \frac{dv(t)}{dt}$
- Take derivative of both sides with respect to time



- $\frac{di_n(t)}{dt} = \frac{1}{R} \frac{dv(t)}{dt} + \frac{1}{L} v(t) + C \frac{d^2v(t)}{dt^2}$
- $\frac{d^2v(t)}{dt^2} + \frac{1}{RC} \frac{dv(t)}{dt} + \frac{1}{LC} v(t) = \frac{1}{C} \frac{di_n(t)}{dt}$
- $v(t) = L \frac{di(t)}{dt}$
- $i(t) = \frac{1}{L} \int_{t_0}^t v(t) dt + i(t_0)$

- $f(t) = \frac{1}{C} \frac{di_n(t)}{dt}$
- $\alpha = \frac{1}{2RC}$
- $\omega_0 = \sqrt{\frac{1}{LC}}$

$$\frac{di^2(t)}{dt^2} + 2\alpha \frac{di(t)}{dt} + \omega_0^2 i(t) = f(t)$$