

EE292: Fundamentals of ECE

Fall 2012

TTh 10:00-11:15 SEB 1242

Lecture 17

121023

<http://www.ee.unlv.edu/~b1morris/ee292/>

Outline

- Review
 - 1st-Order Transients
 - General Sources
 - 2nd-Order Circuits
- Steady-State Sinusoidal Analysis
- Root-Mean-Square Values
- Complex Number Review
- Phasors

General 1st-Order Solution

- Both the current and voltage in an 1st-order circuit has an exponential form
 - RC and LR circuits

- The general solution for current/voltage is:

$$x(t) = x_f + [x(t_0^+) - x_f] e^{-(t-t_0)/\tau}$$



- x – represents current or voltage
 - t_0 – represents time when source switches
 - x_f - final (asymptotic) value of current/voltage
 - τ – time constant (RC or $\frac{L}{R}$)
- Find values and plug into general solution

General Differential Equations

- General differential equation
 - $\tau \frac{dx(t)}{dt} + x(t) = f(t)$
- The full solution to the diff equation is composed of two terms
 - $x(t) = x_p(t) + x_h(t)$
- $x_p(t)$ is the particular solution
 - The response to the particular forcing function
 - Solution has the same form as the forcing function
- $x_h(t)$ is the homogeneous solution (natural response)
 - Another solution that is consistent with the differential equation for $f(t) = 0$
 - The response to any initial conditions of the circuit
 - Exponential form for the solution
 - $x_h(t) = Ke^{-t/\tau}$

General Differential Solution

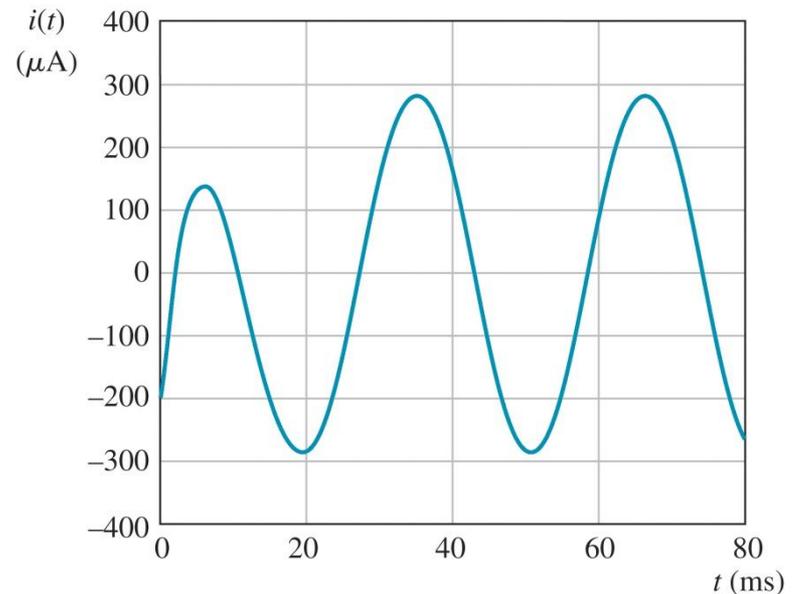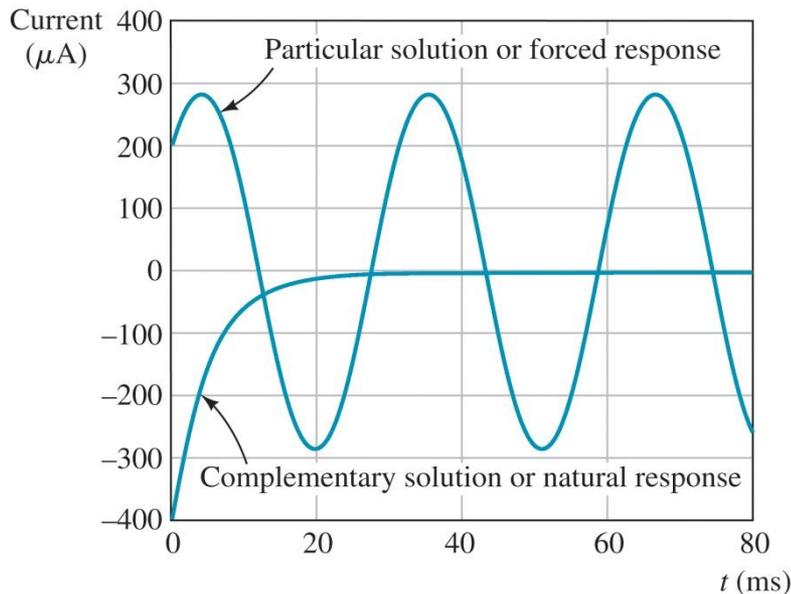- Notice the final solution is the sum of the particular and homogeneous solutions
 - $x(t) = x_p(t) + x_h(t)$
- It has an exponential term due to $x_h(t)$ and a term $x_p(t)$ that matches the input source



Second-Order Circuits

- RLC circuits contain two energy storage elements
 - This results in a differential equation of second order (has a second derivative term)

- Differential equation is of the form

$$\frac{dx^2(t)}{dt^2} + 2\alpha \frac{dx(t)}{dt} + \omega_0^2 x(t) = f(t)$$

- Use KVL, KCL and I/V characteristics of inductance and capacitance to put equation into standard form

Chapter 5 - Steady-State Sinusoidal Analysis


- Sinusoidal sources have many applications
 - Power distribution (current and voltages) in homes
 - Radio communications
 - Fourier analysis – signals can be comprised of linear combinations of sinusoids

Steady-State Sinusoidal Analysis

- In Chapter 4, transient analysis, we saw response of circuit network had two parts
 - $x(t) = x_p(t) + x_h(t)$
- Natural response $x_h(t)$ had an exponential form that decays to zero
- Forced response $x_p(t)$ was the same form as forcing function
 - Sinusoidal source \rightarrow sinusoidal output
 - Output persists with the source \rightarrow at steady-state there is no transient so it is important to study the sinusoid response

Sinusoidal Currents and Voltages

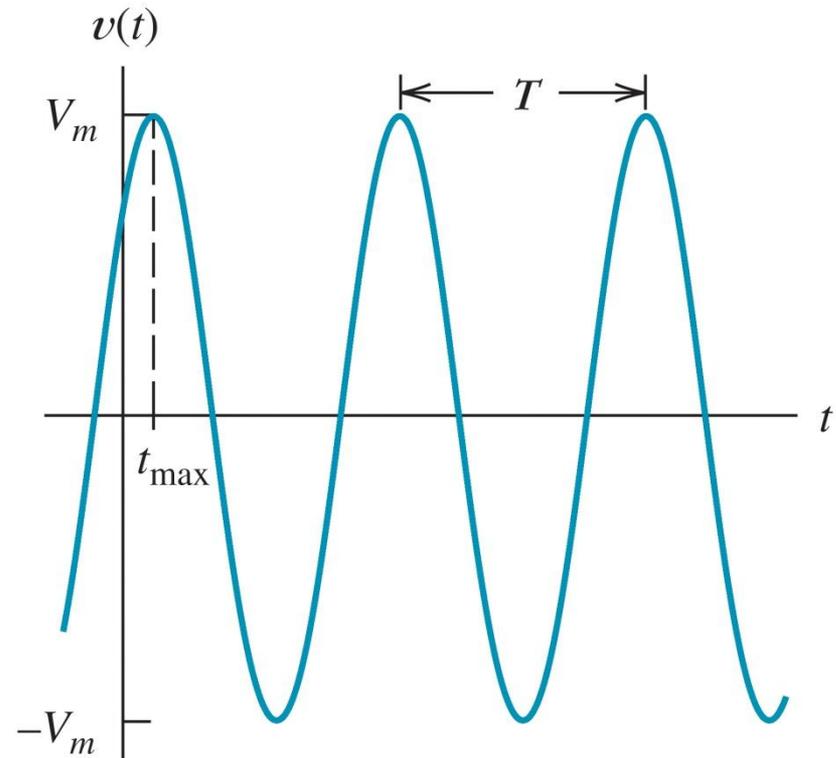- Sinusoidal voltage
 - $v(t) = V_m \cos(\omega_0 t + \theta)$
 - V_m - peak value of voltage
 - ω_0 - angular frequency in radians/sec
 - θ - phase angle in radians
- This is a periodic signal described by
 - T - the period in seconds
 - $\omega_0 = \frac{2\pi}{T}$
 - f - the frequency in Hz = 1/sec
 - $\omega_0 = 2\pi f$



Copyright © 2011, Pearson Education, Inc.

- Note: Assuming that θ is in degrees, we have
 - $t_{\max} = -\theta/360 \times T$.

Sinusoidal Currents and Voltages

- For consistency/uniformity always express a sinusoid as a cosine
- Convert between sine and cosine
- In Degrees
 - $\sin(x) = \cos(x - 90^\circ)$
- In Radians
 - $\sin(x) = \cos\left(x - \frac{\pi}{2}\right)$
- $v(t) = 10\sin(200t + 30^\circ)$
- $v(t) = 10\cos(200t + 30^\circ - 90^\circ)$
- $v(t) = 10\cos(200t - 60^\circ)$

Root-Mean-Square Values

- Apply a sinusoidal source to a resistance
- Power absorbed
 - $p(t) = \frac{v^2(t)}{R}$
- Energy in a single period
 - $E_T = \int_0^T p(t) dt$
- Average power (power absorbed in a single period)
 - $P_{avg} = \frac{E_T}{T} = \frac{1}{T} \int_0^T p(t) dt = \frac{1}{T} \int_0^T \frac{v^2(t)}{R} dt$
 - $P_{avg} = \frac{\left[\sqrt{\frac{1}{T} \int_0^T v^2(t) dt} \right]^2}{R}$

Root-Mean-Square Values

- $$P_{avg} = \frac{\left[\sqrt{\frac{1}{T} \int_0^T v^2(t) dt} \right]^2}{R}$$

- Define rms voltage

- $$V_{rms} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$$

$$P_{avg} = \frac{V_{rms}^2}{R}$$

- Similarly define rms current

- $$I_{rms} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt}$$

$$P_{avg} = I_{rms}^2 R$$

RMS Value of a Sinusoid

- Given a sinusoidal source

- $v(t) = V_m \cos(\omega_0 t + \theta)$

- $$V_{rms} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$$

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T V_m^2 \cos^2(\omega_0 t + \theta) dt}$$

using $\cos^2(x) = 1/2 + 1/2 \cos(2x)$

$$= \sqrt{\frac{V_m^2}{2T} \int_0^T [1 + \cos(2\omega_0 t + 2\theta)] dt}$$

⋮

$$= \frac{V_m}{\sqrt{2}}$$



- The rms value is an “effective” value for the signal

- E.g. in homes we have 60Hz 115 V rms power

- $V_m = \sqrt{2} \cdot V_{rms} = 163 V$

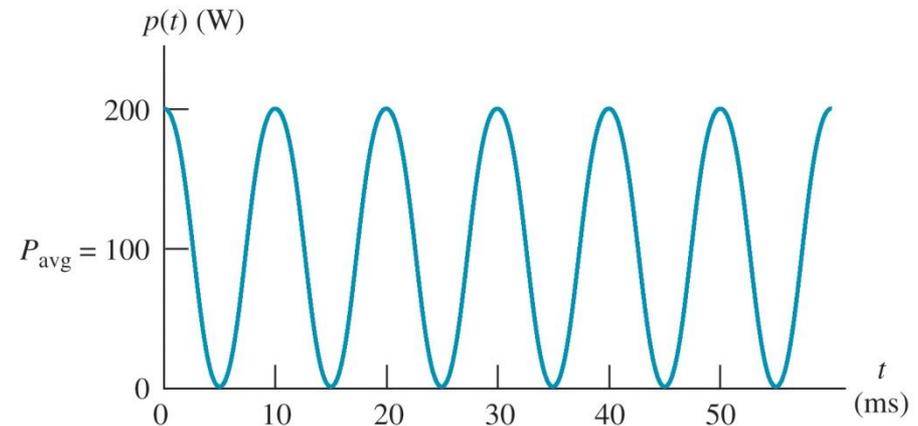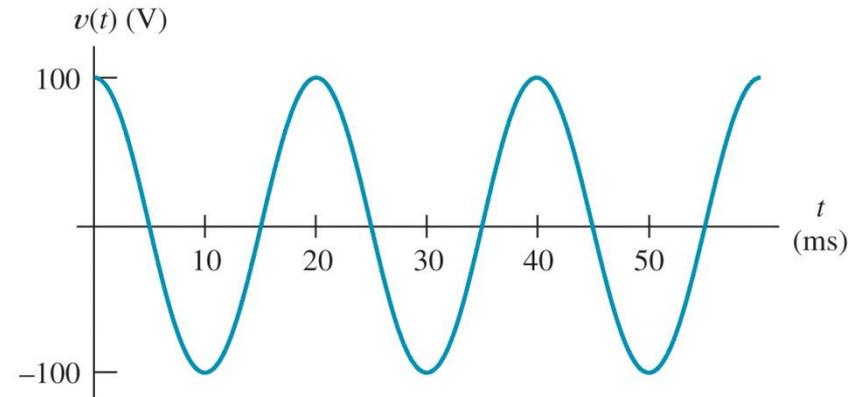Example 5.1

- Voltage
 - $v(t) = 100\cos(100\pi t)$ V
- Applied to a 50Ω resistance
- Find the rms voltage and average power and plot power
- $\omega_0 = 100\pi$
- $f = \frac{\omega}{2\pi} = 50$ Hz
- $T = \frac{1}{f} = \frac{1}{50} = 20$ msec
- $p(t) = \frac{v^2(t)}{R} = \frac{1}{50} 100^2 \cos^2(100\pi t) = 200\cos^2(100\pi t)$ W
- $V_{rms} = \frac{V_m}{\sqrt{2}} = \frac{100}{\sqrt{2}} = 70.71$ V
- $P_{avg} = \frac{V_{rms}^2}{R} = \frac{70.71^2}{50} = 100$ W




Appendix A - Complex Numbers

- Complex numbers involve the imaginary number $j = \sqrt{-1}$
 - Not i as used in math because we know that i is already used for currents in circuits

Complex Numbers in Rectangular Form

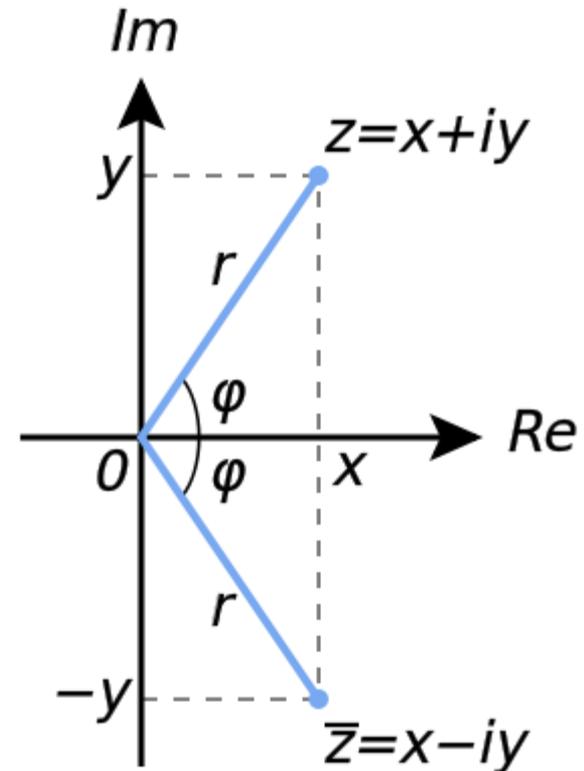- A complex number in rectangular form
$$z = x + jy$$
 - x – real part
 - y – imaginary part
- A vector in the complex plane with
 - x – horizontal coordinate
 - y – vertical coordinate



Complex Arithmetic in Rectangular Form

- $z_1 = 5 + j5, \quad z_2 = 3 - j4$
- Summation
 - Add the real and complex parts separately
- $z_1 + z_2 = (5 + j5) + (3 - j4)$
- $z_1 + z_2 = (8 + j)$
- $z_1 - z_2 = (5 + j5) - (3 - j4)$
- $z_1 - z_2 = (2 + j9)$
- Multiplication
 - Use $j^2 = -1$
- $z_1 z_2 = (5 + j5)(3 - j4)$
- $= 15 - j20 + j15 - j^2 20$
- $= 15 - j5 - (-1)20$
- $= 35 - j5$
- Division
 - Multiply num/den by complex conjugate term to remove imaginary term in denominator
- $\frac{z_1}{z_2} = \frac{(5+j5)}{(3-j4)}$

Complex Arithmetic in Rectangular Form


- Division
 - Multiply num/den by complex conjugate term to remove imaginary term in denominator

$$\begin{aligned}\frac{z_1}{z_2} &= \frac{5 + j5}{3 - j4} \cdot \frac{z_2^*}{z_2^*} \\ &= \frac{5 + j5}{3 - j4} \cdot \frac{3 + j4}{3 + j4} \\ &= \frac{15 + j20 + j15 + j^2(20)}{9 - j12 + j12 - j^2(16)} \\ &= \frac{-5 + j35}{25} \\ &= -0.2 + j1.4\end{aligned}$$

Complex Numbers in Polar Form

- Number represented by magnitude and phase
- Magnitude – the length of the complex vector
- Phase – the angle between the real axis and the vector

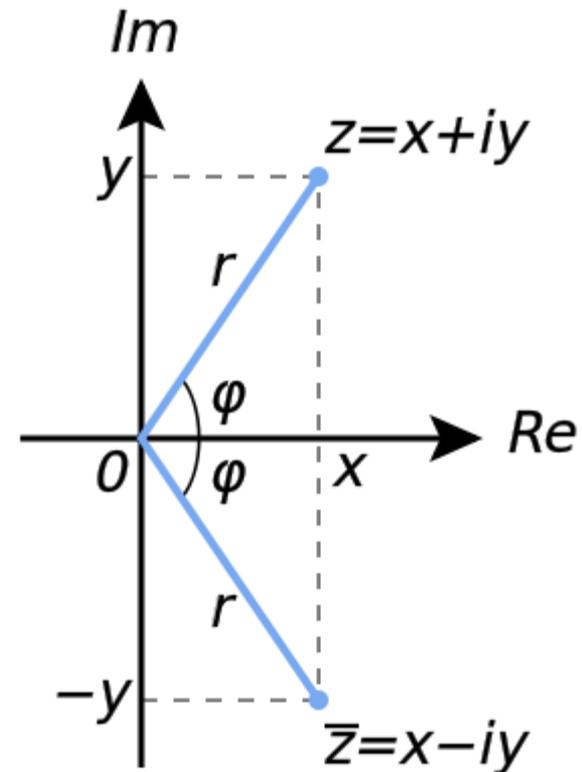- Polar notation
- $z = r e^{j\theta}$
- Phasor notation
- $z = r \angle \theta$



Conversion Between Forms

- Rectangular to polar form
- $r^2 = x^2 + y^2$
- $\tan\theta = \frac{y}{x}$
- Polar to rectangular form
- $x = r\cos\theta$
- $y = r\sin\theta$
- Convert to polar form
- $z = 4 - j4$
- $r = \sqrt{4^2 + 4^2} = 4\sqrt{2}$
- $\theta = \arctan\left(\frac{y}{x}\right) = \arctan(-1) = -\frac{\pi}{4}$
- $z = 4\sqrt{2}e^{-j\pi/4}$

