

# EE292: Fundamentals of ECE

Fall 2012

TTh 10:00-11:15 SEB 1242

Lecture 20

121101

<http://www.ee.unlv.edu/~b1morris/ee292/>


# Outline

- Chapters 1-3
  - Circuit Analysis Techniques
- Chapter 10 – Diodes
  - Ideal Model
  - Offset Model
  - Zener Diodes
- Chapter 4 – Transient Analysis
  - Steady-State Analysis
  - 1<sup>st</sup>-Order Circuits
- Chapter 5 – Steady-State Sinusoidal Analysis
  - RMS Values
  - Phasors
  - Complex Impedance
  - Circuit Analysis with Complex Impedance


# Chapter 10 - Diodes
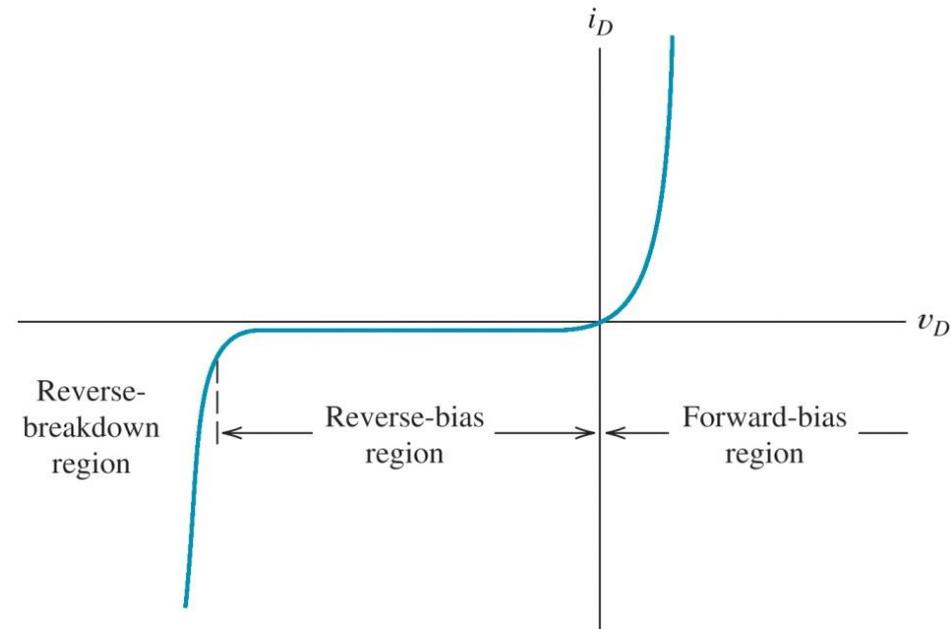
# Diode Voltage/Current Characteristics

- Forward Bias (“On”)
  - Positive voltage  $v_D$  supports large currents
  - Modeled as a battery (0.7 V for offset model)
- Reverse Bias (“Off”)
  - Negative voltage  $\rightarrow$  no current
  - Modeled as open circuit
- Reverse-Breakdown
  - Large negative voltage supports large negative currents
  - Similar operation as for forward bias




(b) Volt–ampere characteristic

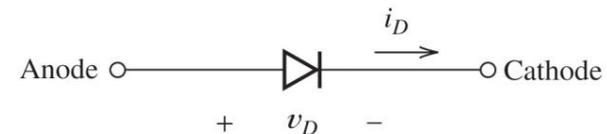


(a) Circuit symbol
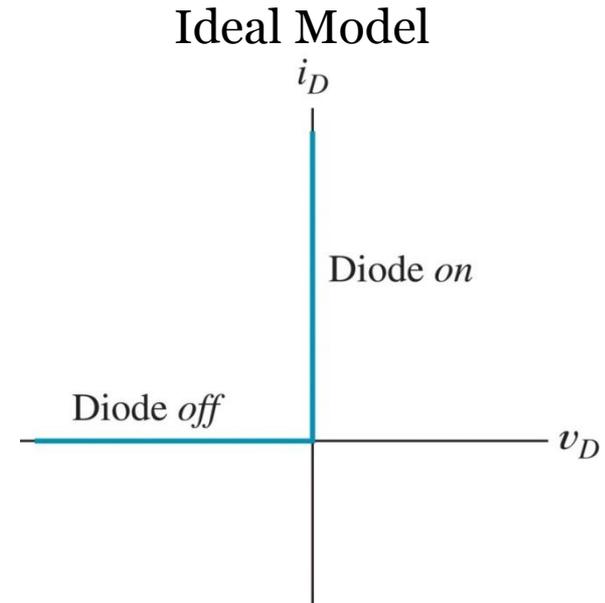
# Diode Models

- Ideal model – simple
- Offset model – more realistic
  
- Two state model
- “On” State
  - Forward operation
  - Diode conducts current
    - Ideal model → short circuit
    - Offset model → battery
- “Off” State
  - Reverse biased
  - No current through diode → open circuit



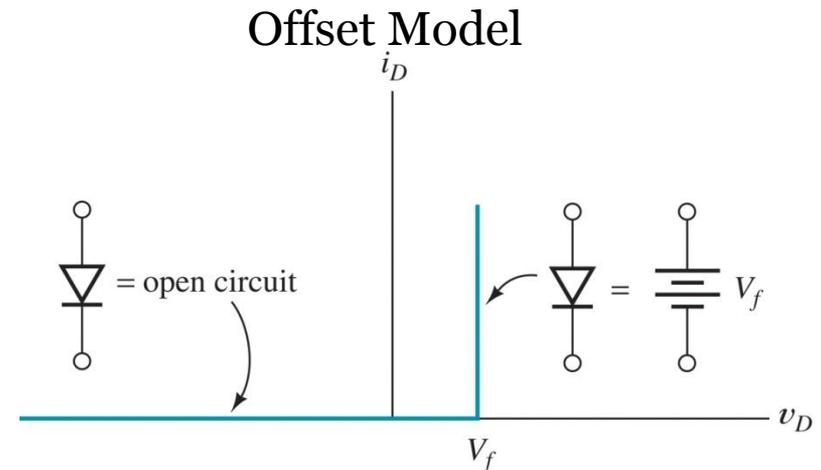Copyright © 2011, Pearson Education, Inc.




Copyright © 2011, Pearson Education, Inc.

# Circuit Analysis with Diodes

- Assume state {on, off} for each ideal diode and check if the initial guess was correct
  - $i_d > 0$  positive for “on” diode
  - $v_d < v_{on}$  for “off” diode
    - These imply a correct guess
  - Otherwise adjust guess and try again
- Exhaustive search is daunting
  - $2^n$  different combinations for  $n$  diodes
- Will require experience to make correct guess
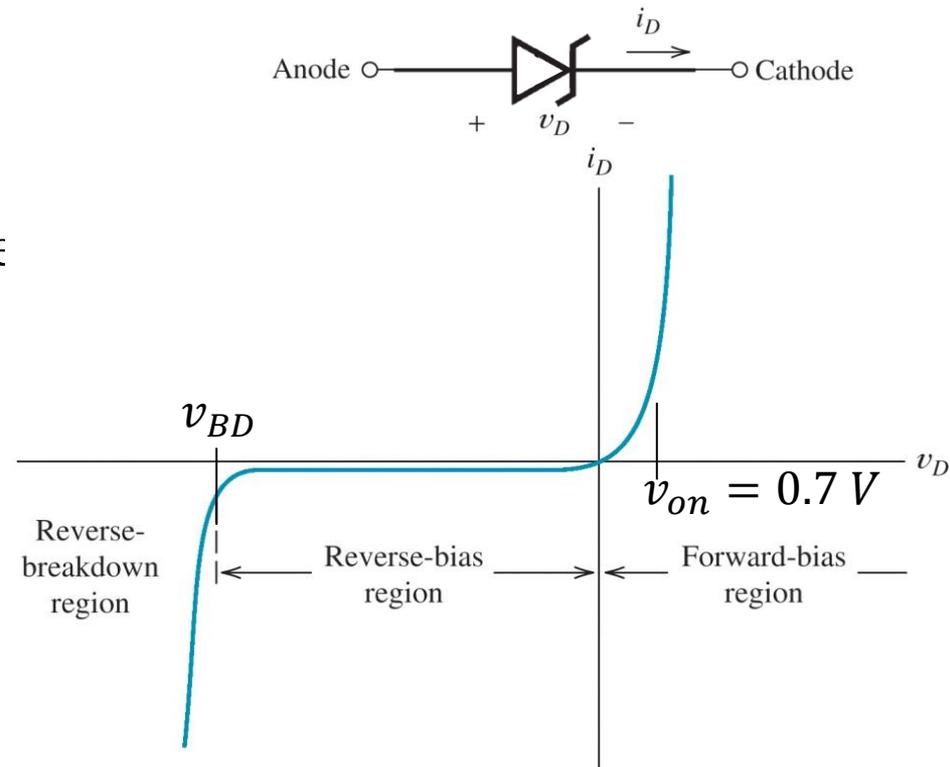
# Zener Diode

- Diode intended to be operated in breakdown
  - Constant voltage at breakdown
- Three state diode
  1. On – 0.7 V forward bias
  2. Off – reverse bias
  3. Breakdown  
 $v_{BD}$  reverse breakdown voltage



(b) Volt-ampere characteristic

# Chapter 4 - Transient Analysis

# DC Steady-State Analysis

- Analysis of C, L circuits in DC operation
  - Steady-state – non-changing sources
- Capacitors  $i = C \frac{dv}{dt}$ 
  - Voltage is constant  $\rightarrow$  no current  $\rightarrow$  open circuit
- Inductors  $v = L \frac{di}{dt}$ 
  - Current is constant  $\rightarrow$  no voltage  $\rightarrow$  short circuit
- Use steady-state analysis to find initial and final conditions for transients

# General 1<sup>st</sup>-Order Solution


- Both the current and voltage in an 1<sup>st</sup>-order circuit has an exponential form
  - RC and LR circuits

- The general solution for current/voltage is:

$$x(t) = x_f + [x(t_0^+) - x_f] e^{-(t-t_0)/\tau}$$


- $x$  – represents current or voltage
  - $t_0$  – represents time when source switches
  - $x_f$  - final (asymptotic) value of current/voltage
  - $\tau$  – time constant ( $RC$  or  $\frac{L}{R}$ )
    - Transient is essentially zero after  $5\tau$
- Find values and plug into general solution
  - Steady-state for initial and final values
  - Two-port equivalents for  $\tau$

# Example Two-Port Equivalent

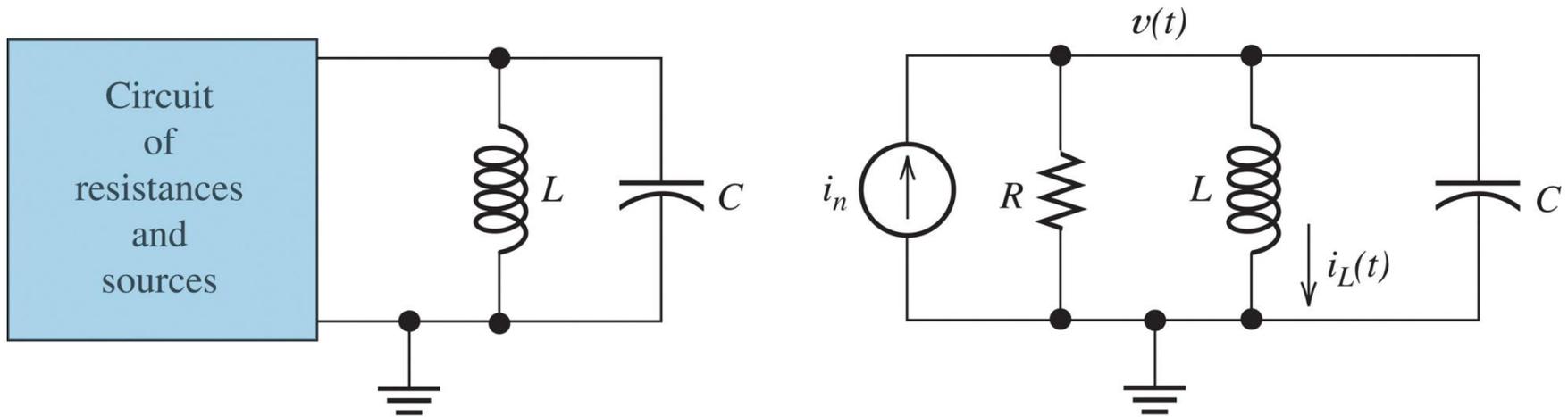

- Given a circuit with a parallel capacitor and inductor
  - Use Norton equivalent to make a parallel circuit equivalent
- Remember:
  - Capacitors add in parallel
  - Inductors add in series

# RC/RL Circuits with General Sources

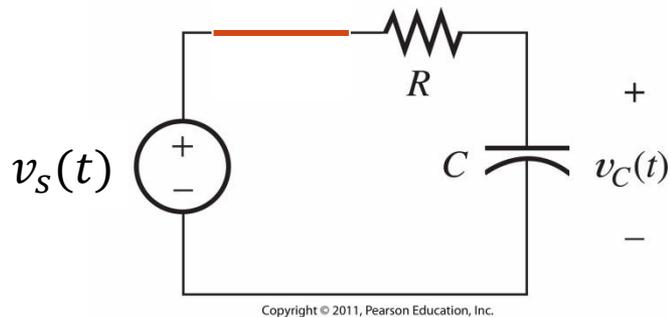

- $RC \frac{dv_c(t)}{dt} + v_c(t) = v_s(t)$
  - The solution is a differential equation of the form
    - $\tau \frac{dx(t)}{dt} + x(t) = f(t)$
    - Where  $f(t)$  the forcing function
  - The full solution to the diff equation is composed of two terms
    - $x(t) = x_p(t) + x_h(t)$
- $x_p(t)$  is the particular solution
    - The response to the particular forcing function
    - $x_p(t)$  will be of the same functional form as the forcing function
      - $f(t) = e^{st} \rightarrow x_p(t) = Ae^{st}$
      - $f(t) = \cos(\omega t) \rightarrow x_p(t) = A\cos(\omega t) + B\sin(\omega t)$
  - $x_h(t)$  is the homogeneous solution
    - “Natural” solution that is consistent with the differential equation for  $f(t) = 0$
    - The response to any initial conditions of the circuit
      - Solution of form
        - $x_h(t) = Ke^{-t/\tau}$

# Second-Order Circuits

- RLC circuits contain two energy storage elements
  - This results in a differential equation of second order (has a second derivative term)
- Use circuit analysis techniques to develop a general 2<sup>nd</sup>-order differential equation of the form

$$\frac{di^2(t)}{dt^2} + 2\alpha \frac{di(t)}{dt} + \omega_0^2 i(t) = f(t)$$

- Use KVL, KCL and I/V characteristics of inductance and capacitance to put equation into standard form
- Must identify  $\alpha$ ,  $\omega_0$ ,  $f(t)$

# Useful I/V Relationships

- Inductor

- $v(t) = L \frac{di(t)}{dt}$

- $i(t) = \frac{1}{L} \int_{t_0}^t v(t) dt + i(t_0)$

- Capacitor

- $i(t) = C \frac{dv(t)}{dt}$

- $v(t) = \frac{1}{C} \int_{t_0}^t i(t) dt + v(t_0)$


# Chapter 5 - Steady-State Sinusoidal Analysis

# Steady-State Sinusoidal Analysis

- In Transient analysis, we saw response of circuit network had two parts
  - $x(t) = x_p(t) + x_h(t)$
- Natural response  $x_h(t)$  had an exponential form that decays to zero
- Forced response  $x_p(t)$  was the same form as forcing function
  - Sinusoidal source  $\rightarrow$  sinusoidal output
  - Output persists with the source  $\rightarrow$  at steady-state there is no transient so it is important to study the sinusoid response
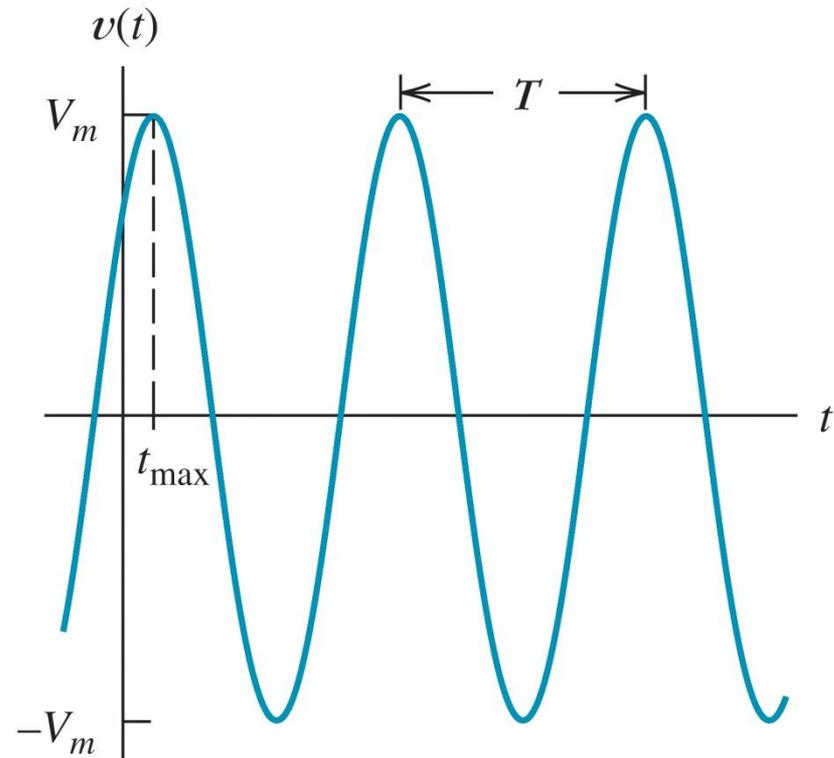
# Sinusoidal Currents and Voltages

- Sinusoidal voltage
  - $v(t) = V_m \cos(\omega_0 t + \theta)$
  - $V_m$  - peak value of voltage
  - $\omega_0$  - angular frequency in radians/sec
  - $\theta$  - phase angle in radians
- This is a periodic signal described by
  - $T$  - the period in seconds
    - $\omega_0 = \frac{2\pi}{T}$
  - $f$  - the frequency in Hz = 1/sec
    - $\omega_0 = 2\pi f$



Copyright © 2011, Pearson Education, Inc.

- Note: Assuming that  $\theta$  is in degrees, we have
  - $t_{\max} = -\theta/360 \times T$ .

# Root-Mean-Square Values

- $$P_{avg} = \frac{\left[ \sqrt{\frac{1}{T} \int_0^T v^2(t) dt} \right]^2}{R}$$

- Define rms voltage

- $$V_{rms} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$$

$$P_{avg} = \frac{V_{rms}^2}{R}$$

- Similarly define rms current

- $$I_{rms} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt}$$

$$P_{avg} = I_{rms}^2 R$$

# RMS Value of a Sinusoid

- Given a sinusoidal source

- $v(t) = V_m \cos(\omega_0 t + \theta)$

- $$V_{rms} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$$

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T V_m^2 \cos^2(\omega_0 t + \theta) dt}$$

using  $\cos^2(x) = 1/2 + 1/2 \cos(2x)$

$$= \sqrt{\frac{V_m^2}{2T} \int_0^T [1 + \cos(2\omega_0 t + 2\theta)] dt}$$

⋮

$$= \frac{V_m}{\sqrt{2}}$$

- The rms value is an “effective” value for the signal


- E.g. in homes we have 60Hz 115 V rms power

- $V_m = \sqrt{2} \cdot V_{rms} = 163 V$

# Conversion Between Forms

- Rectangular to polar form
- $r^2 = x^2 + y^2$
- $\tan\theta = \frac{y}{x}$
- Polar to rectangular form
- $x = r\cos\theta$
- $y = r\sin\theta$
- Convert to polar form
- $z = 4 - j4$
- $r = \sqrt{4^2 + 4^2} = 4\sqrt{2}$
- $\theta = \arctan\left(\frac{y}{x}\right) = \arctan(-1) = -\frac{\pi}{4}$
- $z = 4\sqrt{2}e^{-j\pi/4}$

$x$ (degrees)	$x$ (radians)	$\sin(x)$	$\cos(x)$	$\tan(x)$
0	0	0	1	0
15	$\frac{\pi}{12}$	$\frac{-1 + \sqrt{3}}{2\sqrt{2}}$	$\frac{1 + \sqrt{3}}{2\sqrt{2}}$	$2 - \sqrt{3}$
30	$\frac{\pi}{6}$	$\frac{1}{2}$	$\frac{\sqrt{3}}{2}$	$\frac{1}{\sqrt{3}}$
45	$\frac{\pi}{4}$	$\frac{1}{\sqrt{2}}$	$\frac{1}{\sqrt{2}}$	1
60	$\frac{\pi}{3}$	$\frac{\sqrt{3}}{2}$	$\frac{1}{2}$	$\sqrt{3}$
75	$\frac{5\pi}{12}$	$\frac{1 + \sqrt{3}}{2\sqrt{2}}$	$\frac{-1 + \sqrt{3}}{2\sqrt{2}}$	$2 + \sqrt{3}$
90	$\frac{\pi}{2}$	1	0	<i>NaN</i>

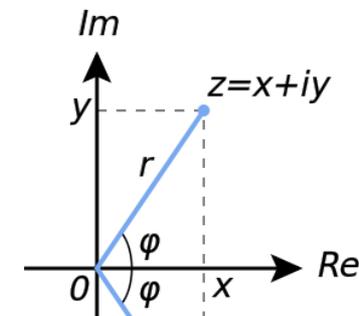


Source: Wikipedia

# Phasors

- A representation of sinusoidal signals as vectors in the complex plane
  - Simplifies sinusoidal steady-state analysis
- Given
  - $v_1(t) = V_1 \cos(\omega t + \theta_1)$
- The phasor representation is
  - $\mathbf{V}_1 = V_1 \angle \theta_1$
- For consistency, use only cosine for the phasor
  - $v_2(t) = V_2 \sin(\omega t + \theta_2) = V_2 \cos(\omega t + \theta_2 - 90^\circ)$
  - $\mathbf{V}_2 = V_2 \angle (\theta_2 - 90^\circ)$

- Phasor diagram

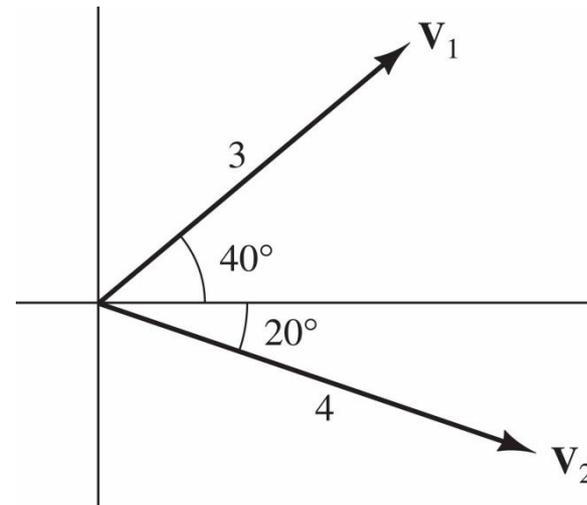

Copyright © 2011, Pearson Education, Inc.

- $\mathbf{V}_1 = 3 \angle (40^\circ)$
- $\mathbf{V}_2 = 4 \angle (-20^\circ)$
- Phasors rotate counter clockwise
  - $\mathbf{V}_1$  leads  $\mathbf{V}_2$  by  $60^\circ$
  - $\mathbf{V}_2$  lags  $\mathbf{V}_1$  by  $60^\circ$

# Complex Impedance

- Impedance is the extension of resistance to AC circuits
  - Extend Ohm's Law to an impedance form for AC signals
    - $V = ZI$
- Inductors oppose a change in current
  - $Z_L = \omega L \angle \left(\frac{\pi}{2}\right) = j\omega L$
  - Current lags voltage by  $90^\circ$
- Capacitors oppose a change in voltage
  - $Z_C = \frac{1}{\omega C} \angle \left(-\frac{\pi}{2}\right) = -j \frac{1}{\omega C} = \frac{1}{j\omega C}$
  - Current leads voltage by  $90^\circ$
- Resistor impedance the same as resistance
  - $Z_R = R$

# Circuit Analysis with Impedance

- KVL and KCL remain the same
  - Use phasor notation to setup equations
- Replace sources by phasor notation
- Replace inductors, capacitors, and resistances by impedance value
  - This value is dependent on the source frequency  $\omega$
- Use your favorite circuit analysis techniques to solve for voltage or current
  - Reverse phasor conversion to get sinusoidal signal in time