

EE292: Fundamentals of ECE

Fall 2012

TTh 10:00-11:15 SEB 1242

Lecture 23

121120

Outline

- Review
 - Combinatorial Logic
- Sequential Logic

Combinatorial Logic Circuits


- Combine logical variable inputs to produce a logic-variable output
- Logic can be specified by enumerating the output for all possible input combinations in a truth table
- Considered memoryless circuits
 - The output at a given time instant are only dependent on the input at the same time instant

Basic Logic Gates

- Inverter – NOT operation or complement of a variable
 - $\text{NOT}(A) = \bar{A}$

A	\bar{A}
0	1
1	0

(a) Truth table

 


(b) Symbol for an inverter

Copyright © 2011, Pearson Education, Inc.

- AND - computes the logical multiplication of input variables
 - $\text{AND}(A, B) = AB$

A	B	$C = AB$
0	0	0
0	1	0
1	0	0
1	1	1

(a) Truth table

 


(b) Symbol for two-input AND gate

Copyright © 2011, Pearson Education, Inc.

- OR - computes the logical addition of input variables
 - $\text{OR}(A, B) = A + B$

A	B	$C = A + B$
0	0	0
0	1	1
1	0	1
1	1	1

(a) Truth table

 


(b) Symbol for two-input OR gate

Copyright © 2011, Pearson Education, Inc.


More Logic Gates

- In silicon chips, other gates are simpler to implement
- Buffer = NOT followed by NOT
 - Returns the same value
- NAND = AND followed by NOT
- NOR = OR followed by NOT
- XOR is the exclusive-OR gate
 - $\text{XOR}(A, B) = A \oplus B$


A	B	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

 


(d) Buffer

 

(a) NAND gate

 

(b) NOR gate

 


(c) XOR gate

Boolean Algebra

- Mathematical theory of logical variables
- Use basic AND, OR, and NOT relationships to prove a Boolean expression
 - Can generate a truth table to specify the output relationship for all possible input values
- De Morgan's Laws
 - Provides a way to convert an AND relationship into an OR relationship and vice versa
 - $ABC = \overline{\overline{A} + \overline{B} + \overline{C}}$
 - $(A + B + C) = \overline{\overline{A}\overline{B}\overline{C}}$

Implementation of Boolean Expressions

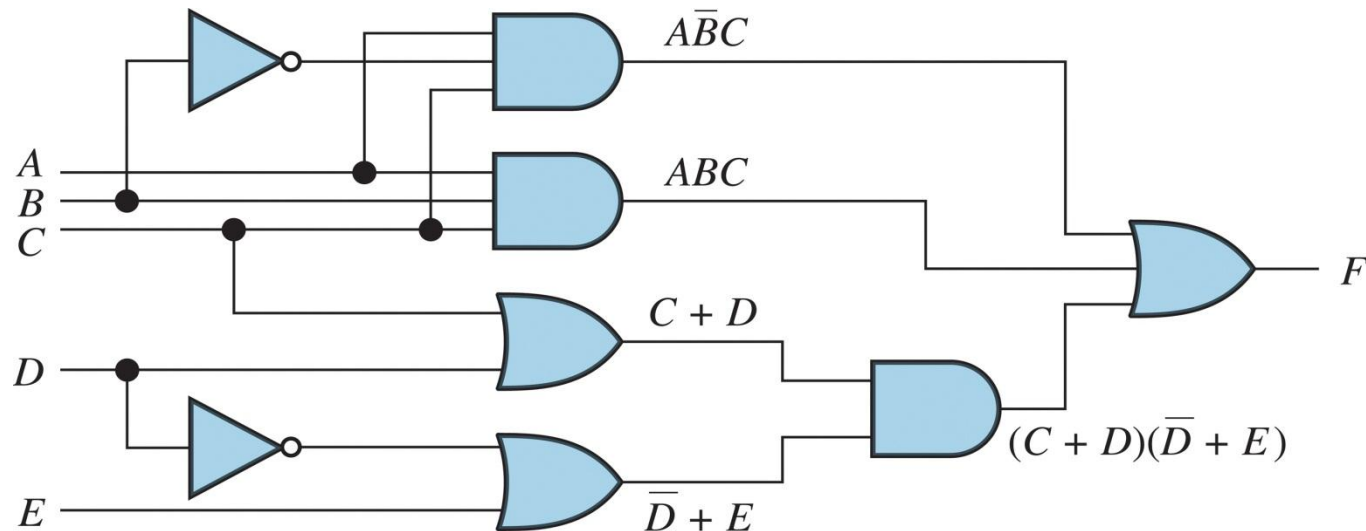- A logical variable can be composed of Boolean relationships
 - AND, OR, NOT, etc.
- Gate level implementation is straightforward
- Example
- $F = A\bar{B}C + ABC + (C + D)(\bar{D} + E)$



Simplifying Boolean Expression

- Find simpler equivalent expressions by manipulation of equation and Boolean relations
- Example
- $F = A\bar{B}C + ABC + (C + D)(\bar{D} + E)$
- $F = A\bar{B}C + ABC + (C\bar{D} + CE + D\bar{D} + DE)$
- $F = A\bar{B}C + ABC + (C\bar{D} + CE + 0 + DE)$
- $F = AC(\bar{B} + B) + (C\bar{D} + CE + 0 + DE)$
- $F = AC(1) + (C\bar{D} + CE + 0 + DE)$
- $F = C(A + \bar{D} + E) + DE$

Synthesis of Logic

- Require methods to convert logic circuit specifications into a practical gate level implementation
 - Often the logic is specified in a natural language
- Example: automatic windshield wipers
 - When it is raining (input 1) and cloudy (input 2) the wipers should be on (output)
- Example: 3 Logical variable input and 1 output
 - Enumerate all possible input values and specify the corresponding output
 - A, B, C input and D output

A	B	C	D
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Sum-of-Products Implementation

- Find all output rows that have a 1 output
 - Determine AND relationship between inputs
- OR the AND terms from each row

<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>		AND Term
0	0	0	1		$\bar{A}\bar{B}\bar{C}$
0	0	1	0		
0	1	0	1		$\bar{A}B\bar{C}$
0	1	1	0		
1	0	0	0		
1	0	1	0		
1	1	0	1		$AB\bar{C}$
1	1	1	1		ABC

$$D = \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + AB\bar{C} + ABC$$

Product-of-Sums Implementation

- Find all output rows that have a 0 output
 - Determine OR relationship between inputs
- AND the OR terms from each row

<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>		OR Term
0	0	0	1		
0	0	1	0		$A + B + \bar{C}$
0	1	0	1		
0	1	1	0		$A + \bar{B} + \bar{C}$
1	0	0	0		$\bar{A} + B + C$
1	0	1	0		$\bar{A} + B + \bar{C}$
1	1	0	1		
1	1	1	1		


$$D = (A + B + \bar{C})(A + \bar{B} + \bar{C})(\bar{A} + B + C)(\bar{A} + B + \bar{C})$$

Sequential Logic

- Combinatorial logic output is only dependent on input at the given time
- Sequential logic has outputs that are dependent not only on current input but past input as well
 - The circuits have “memory”
- Often times sequential circuits use a clock signal to regulate when the output should change
 - These are called synchronous circuits
 - Asynchronous circuits are able to change as soon as inputs change (no clock signal is required)

The Flip-Flop

 - This is the basic building block for sequential circuits
- A flip-flop has two allowable “states” of operation
 - It is able to store a bit of information
- When Q is high
 - \bar{Q} will be low
- When Q is low
 - \bar{Q} will be high
- Coupled inverter configuration ensures the state does not change




Copyright © 2011, Pearson Education, Inc.

- Once Q is set, it does not change
- How can we set the flip-flop state?

SR Flip-Flops

 - Set-reset (SR) flip-flop allows control of the state
- When R and S are low
 - This behaves as the coupled inverters
 - Remains in “set state” (Q set stays high)
- When S is high and R is low
 - Top NOR is an inverter and Q is forced high and \bar{Q} low
- When R is high and S is low
 - Bottom NOR is an inverter and \bar{Q} is forced high and Q is low



- R and S cannot both be set at the same time


SR Flip-Flop Truth Table

- S = Set
- R = Reset

- Truth Table

R	S	Q_n
0	0	Q_{n-1}
0	1	1
1	0	0
1	1	Not allowed

(a) Truth table

 


(b) Circuit symbol


- The circuit remember what was the last input
- Q_n - represents the output at a time n
- Q_{n-1} - represents the output at an earlier time $n - 1$
 - Time $n - 1$ is the time when either S or R was last high
- Notice that set and reset inputs are not allowed to be high at the same time
 - Circuit cannot operate in this condition

Debouncing a Switch

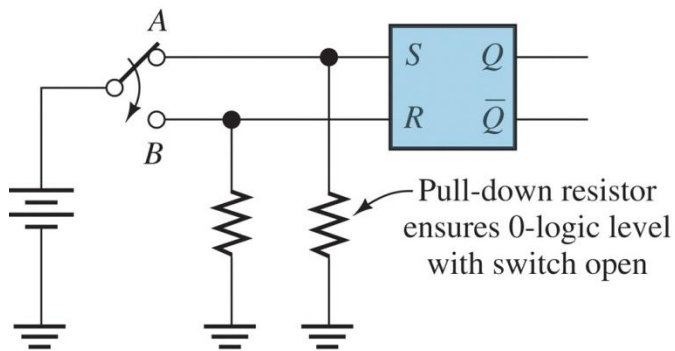
- Physical switches do not make perfect contact when moving from one position to another
 - The voltage across the switch is said to bounce
- An SR flip-flop can be used to debounce the switch
 - Make a “good” contact and prevent voltage from bouncing



(a) Circuit diagram

 


- Debounced output

 

 
(b) Waveforms

Clocked SR Flip-Flop

- The previous SR flip-flop state changes as soon as either S or R is set
- Often we would like to have control on when the state is allowed to change
 - Want a synchronous circuit
- Add a clock signal to the flip-flop
 - Only when the clock is high the output allowed to change



(c) Circuit symbol

 

(a) Circuit diagram


- AND gates prevent R or S from reaching the flip-flop unless the clock C is high

R	S	C	Q_n
0	0	×	Q_{n-1}
0	1	1	1
1	0	1	0
1	1	1	Not allowed
×	×	0	Q_{n-1}

 (b) Truth table

Clocked SR with Asynchronous Input


- Clocked set and reset functionality with asynchronous set and reset as well



(a) Circuit diagram

Pr	Cl	R	S	C	Q_n
0	0	0	0	×	Q_{n-1}
0	0	0	1	1	1
0	0	1	0	1	0
×	×	1	1	1	Not allowed
0	1	×	×	×	0
1	0	×	×	×	1
1	1	×	×	×	Not allowed

(b) Truth table

 


(c) Circuit symbol

- Add OR gates at $Q\bar{Q}$ outputs to automatically set or reset
 - Notice that the clocked S and R cannot be high at the same time and neither can the asynchronous preset Pr and clear Cl


Edge-Triggered Circuits

 - The clocked SR flip-flop uses the clock signal as an enable signal
 - When the clock is high the circuit is allowed to change
- Edge-triggered circuits only respond at the time when the clock changes between low and high
 - Positive-edge-triggered – low to high transition
 - Known as the leading edge
 - Negative-edge-triggered – high to low transition
 - Known as the trailing edge



D Flip-Flop

 - The delay (D) flip-flop is edge-triggered to take make the output the same as the input right before the clock transition



(a) Circuit symbol

C	D	Q_n
0	\times	Q_{n-1}
1	\times	Q_{n-1}
\uparrow	0	0
\uparrow	1	1


(b) Truth table

indicates a transition
from low to high

- The triangle by the clock signal C indicates it is positive-edge-triggered
 - Up arrow in truth table indicates rising edge


Example: D Flip-Flop

- Positive-edge-triggered

 

JK Flip-Flop

 - Similar operation to the SR flip-flop
 - Except when J and K are both high, the output state Q will toggle



(a) Circuit symbol

C	J	K	Q_n	Comment
0	\times	\times	Q_{n-1}	Memory
1	\times	\times	Q_{n-1}	Memory
↓	0	0	Q_{n-1}	Memory
↓	0	1	0	Reset
↓	1	0	1	Set
↓	1	1	\bar{Q}_{n-1}	Toggle


(b) Truth table

indicates a transition
from low to high

- Notice this is a negative-edge-triggered
 - Triangle with a preceding invert bubble


Registers

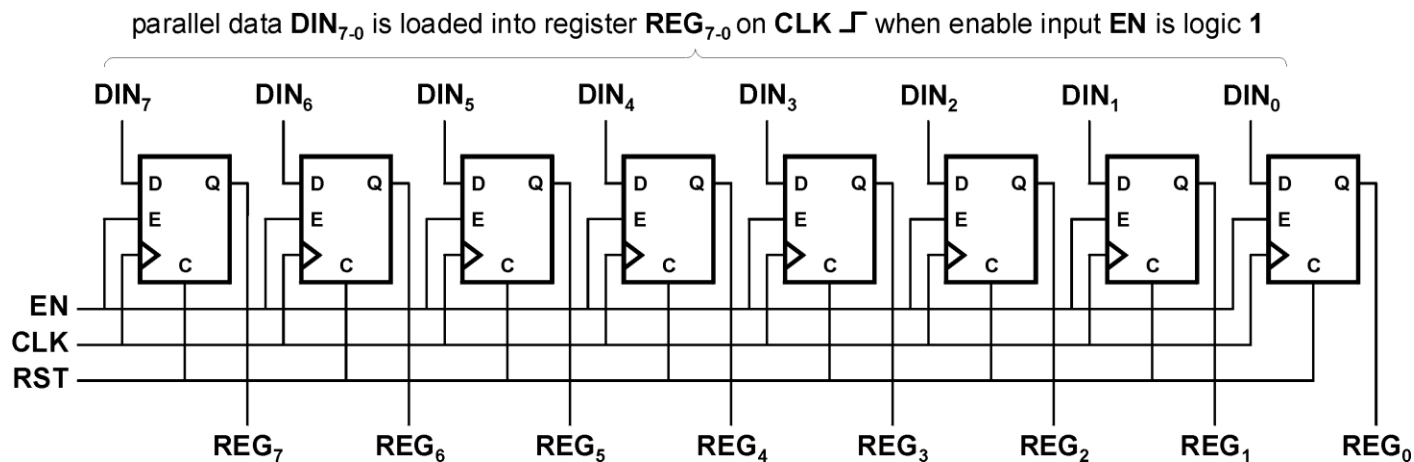- A flip-flop is able to store a single bit
- A register is an array of flip-flops used to store a digital word
 - A hexadecimal number requires 4 bits so 4 flip-flops are required to internally store the hex number




Serial-In Parallel-Out Shift Register

 - Serial-in – implies bit are presented to the register one at a time (in a sequence)
- Parallel-out – implies the contents of the register (all the bits) can be accessed at the same time




Serial-In Parallel-Out Operation

 - Data is presented to a single input at the “front” of the word
- At each clock transition the data is shifted from one flip-flop to the next
- After 4 clock cycles, the full word is available to be read in the register



Parallel-In Serial Out Shift Register

 
- Parallel data is provided as input and the output is serial data
 - E.g. transmission of data on a telephone line
- The register can be cleared asynchronously to initialize the register
- Data is set on inputs and a parallel enable signal asynchronously loads the data
- The output is serially transmitted from the last flip-flop stage



Copyright © 2011, Pearson Education, Inc.

Counters

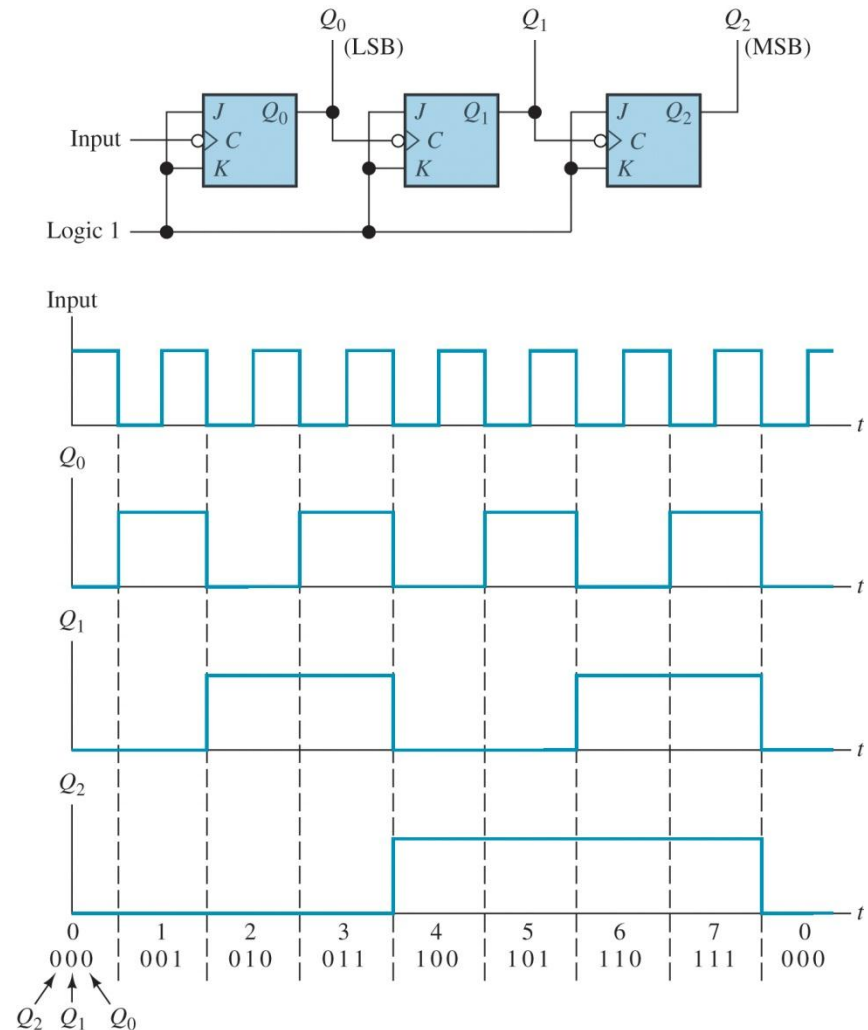- Circuit used to count the pulses in an input signal
 - Often the number of clocks are the signal of interest
- Inputs of JK flip-flop are tied together and high
 - Causes the output state to toggle with each clock cycle
 - Notice this is negative-edge-triggered
- Output of one JK flip-flop is the clock input of the next stage
 - The word $Q_2Q_1Q_0$ is the binary representation of the count



Minimization of Logic Circuits

- We saw you can minimize logic variable representations using Boolean algebra but this can be tedious and prone to error
- The Karnaugh map (K-map) (Ch 7.5) is a principled method for determining the minimum representation
 - This method is usually only practical for 4 variables (maybe 5 or 6)
 - We will not cover this in class but it is an interesting read