

BASIC CONCEPTS

Yahia Baghzouz

**Electrical & Computer Engineering
Department**




INSTANTANEOUS VOLTAGE, CURRENT AND POWER, RMS VALUES

$$v(t) = V_m \cos(\omega t + \theta_v)$$

$$i(t) = I_m \cos(\omega t + \theta_i)$$

$$p(t) = v(t) i(t)$$

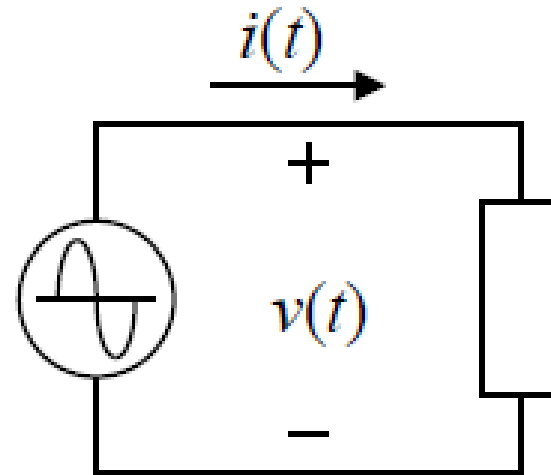

$$\theta = \theta_v - \theta_i \quad V_m = \sqrt{2} |V| \quad I_m = \sqrt{2} |I|$$

$$p(t) = \underbrace{|V| |I| \cos \theta \{1 + \cos 2(\omega t + \theta_v)\}}_{\text{energy flow into the circuit}} + \underbrace{|V| |I| \sin \theta \sin 2(\omega t + \theta_v)}_{\text{energy borrowed and returned by the circuit}}$$

energy flow into
the circuit

energy borrowed and
returned by the circuit

AVERAGE (REAL) POWER, REACTIVE POWER, APPARENT POWER, POWER FACTOR

$$p(t) = |V| |I| \{1 + \cos 2(\omega t + \theta_v)\} \cos \theta + |V| |I| \sin 2(\omega t + \theta_v) \sin \theta$$

$$p_R(t) = |V| |I| \{1 + \cos 2(\omega t + \theta_v)\} \cos \theta = \bar{P} \{1 + \cos 2(\omega t + \theta_v)\}$$

$$p_X(t) = |V| |I| \sin 2(\omega t + \theta_v) \sin \theta = S \sin \theta \sin 2(\omega t + \theta_v)$$






$$\bar{P} = |V| |I| \cos \theta$$

$$S = |V| |I|$$

$$Q \equiv S \sin \theta = |V| |I| \sin \theta$$

$$pf = \cos \theta = \frac{\bar{P}}{|V| |I|}$$

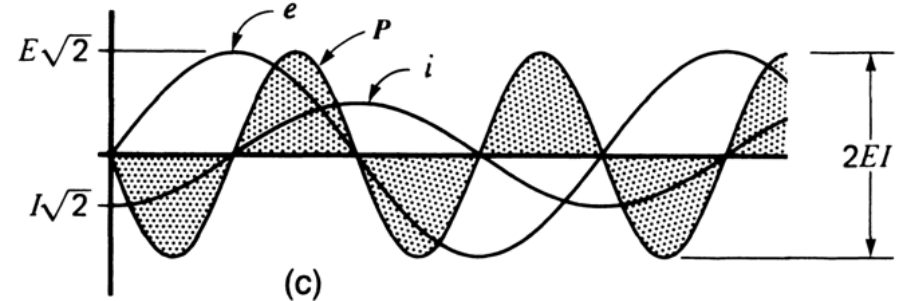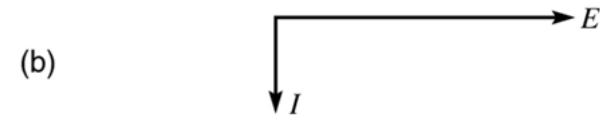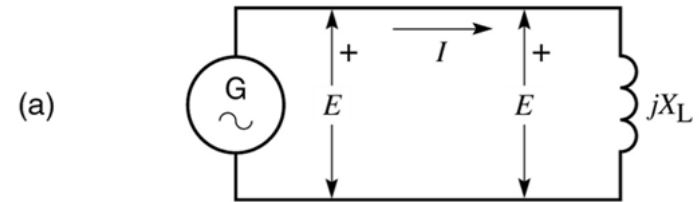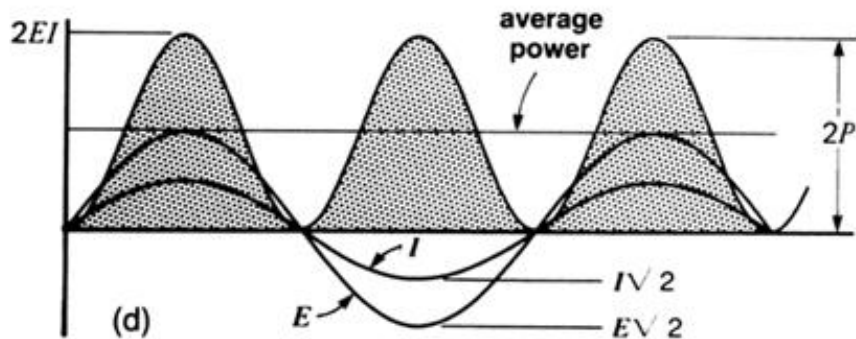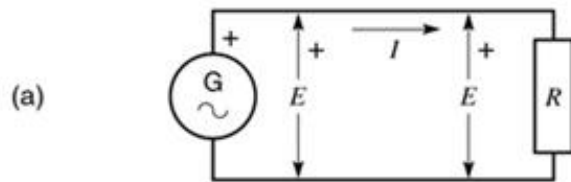INSTANTANEOUS POWER IN PURE RESISTIVE AND INDUCTIVE CIRCUITS







PHASOR NOTATION, IMPEDANCE AND ADMITTANCE

Transformation of a sinusoidal signal to and from the time domain to the phasor domain:







$$\begin{array}{ccc} v(t) = \sqrt{2}|V| \cos(\omega t + \theta_v) & \longleftrightarrow & V = |V| \angle \theta_v \\ \text{(time domain)} & & \text{(phasor domain)} \end{array}$$

Element	Impedance	Admittance
R	$Z = R$	$Y = \frac{1}{R}$
L	$Z = j\omega L$	$Y = \frac{1}{j\omega L}$
C	$Z = -j\frac{1}{\omega C}$	$Y = j\omega C$

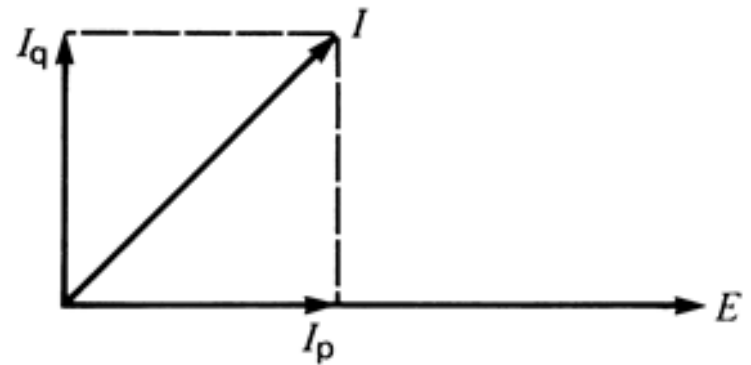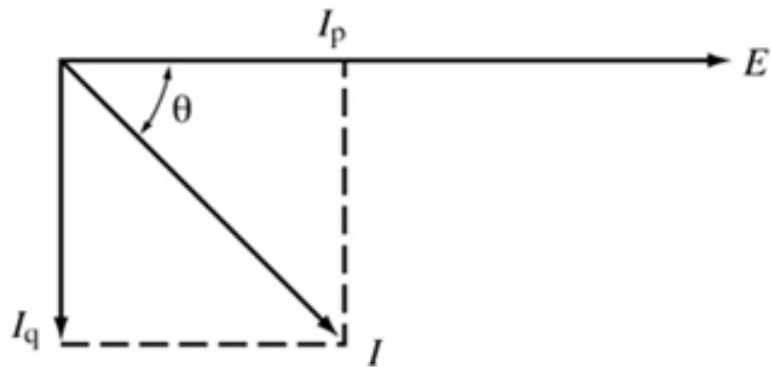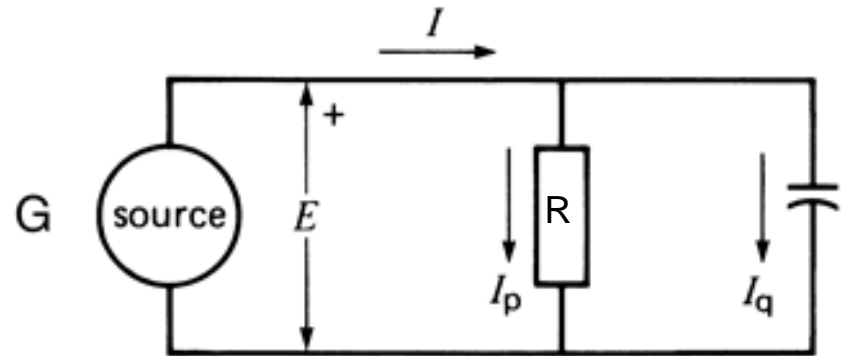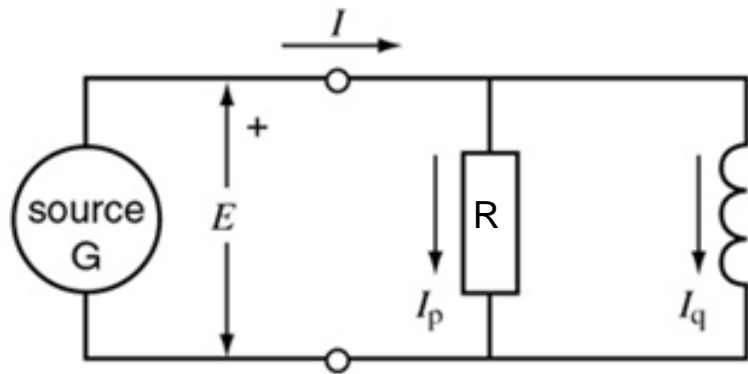RESISTIVE-INDUCTIVE, RESISTIVE-CAPACITIVE LOAD



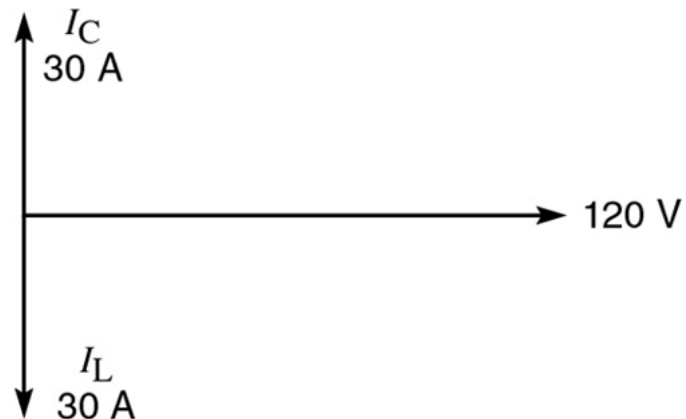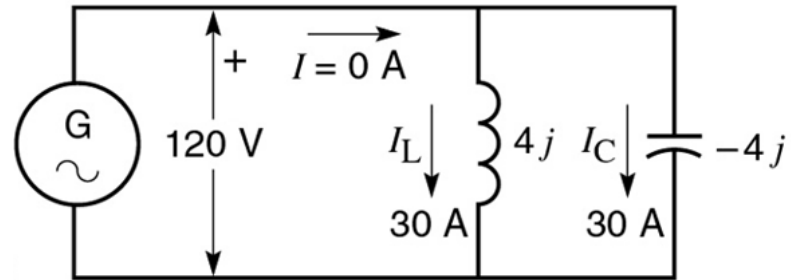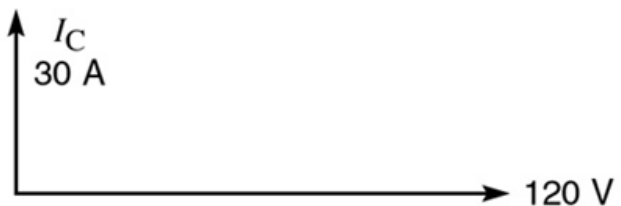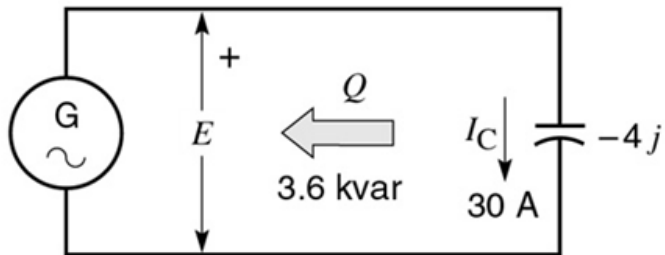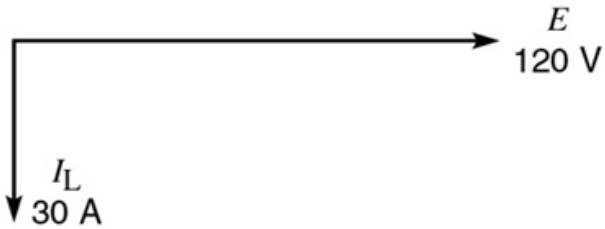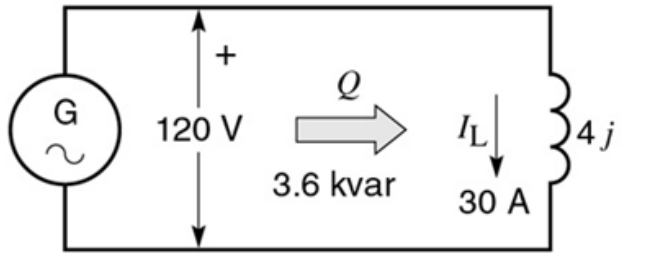POWER IN INDUCTIVE AND CAPACITIVE CIRCUITS




COMPLEX POWER, POWER TRIANGLE


$$V I^* = |V| |I| \angle(\theta_v - \theta_i) = |V| |I| \angle \theta = S$$

$$S = |V| |I| \cos \theta + j |V| |I| \sin \theta = P + jQ$$



$$|S| = \sqrt{P^2 + Q^2}$$

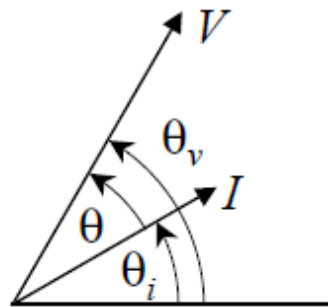

Lagging Power Factor

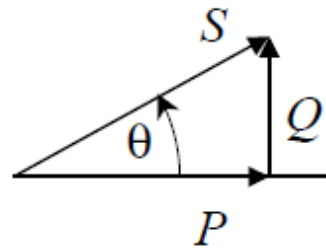


Leading Power Factor

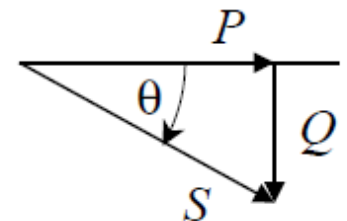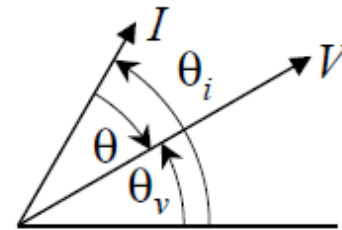

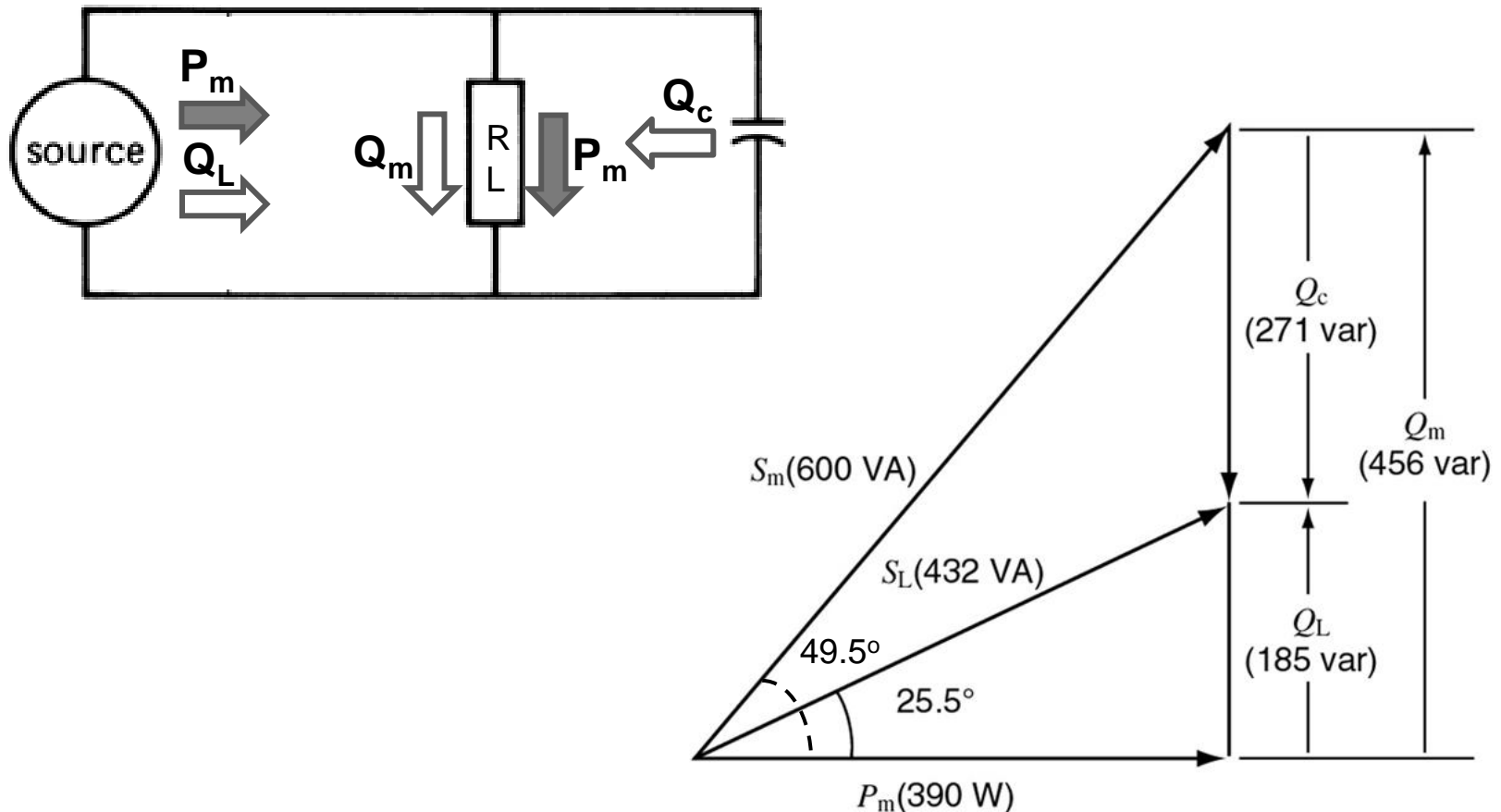EXAMPLE: POWER FACTOR CORRECTION

The power triangle below shows that the power factor is corrected by a shunt capacitor from 65% to 90% (lag).




CONSERVATION OF POWER

- At every node (bus) in the system,
 - the sum of real powers entering the node must be equal to the sum of real powers leaving that node.
 - The same applies for reactive power,
 - The same applies for complex power
 - The same **does not apply** for apparent power
- The above is a direct consequence of Kirchhoff's current law, which states that the sum of the currents flowing into a node must equal the sum of the currents flowing out of that node.

BALANCED 3 PHASE CIRCUITS

- ❑ Bulk power systems are almost exclusively 3-phase. Single phase is used primarily only in low voltage, low power settings, such as residential and some commercial customers.
- ❑ Some advantages of three-phase system:
 - Can transmit more power for the same amount of wire (twice as much as single phase)
 - Torque produced by 3 ϕ machines is constant, easy start.
 - Three phase machines use less material for same power rating

PHASE AND LINE VOLTAGES

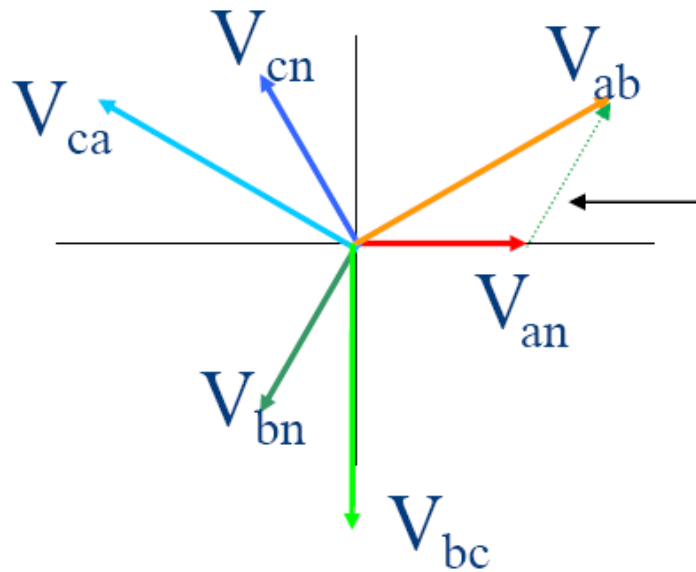

$$V_{an} = |V| \angle \alpha^\circ$$

$$V_{bn} = |V| \angle \alpha^\circ - 120^\circ$$

$$V_{cn} = |V| \angle \alpha^\circ + 120^\circ$$

($\alpha = 0$ in this case)

$$V_{ab} = V_{an} - V_{bn} = |V|(1 \angle \alpha - 1 \angle \alpha + 120^\circ)$$




$$= \sqrt{3} |V| \angle \alpha + 30^\circ$$

$$V_{bc} = \sqrt{3} |V| \angle \alpha - 90^\circ$$

$$V_{ca} = \sqrt{3} |V| \angle \alpha + 150^\circ$$


Line to line
voltages are
also balanced

NEUTRAL WIRE

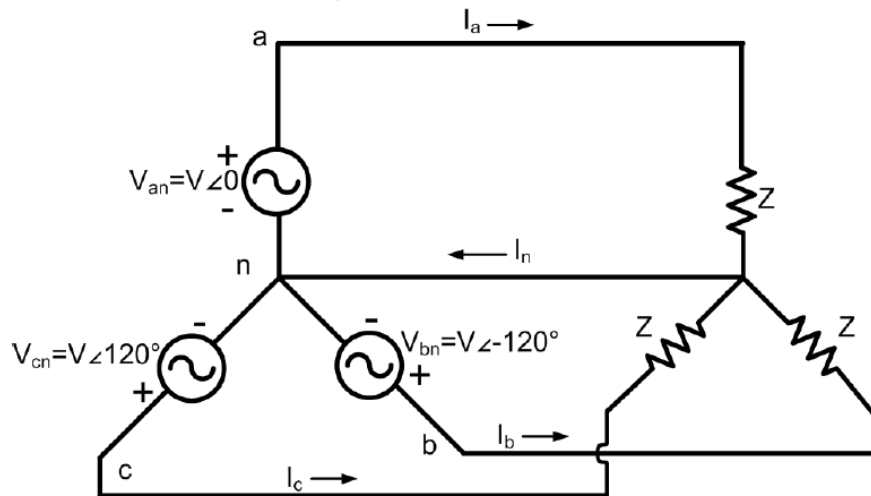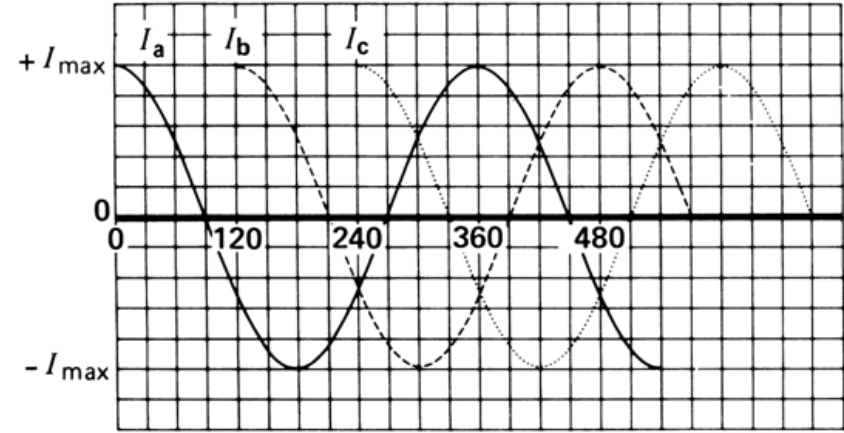
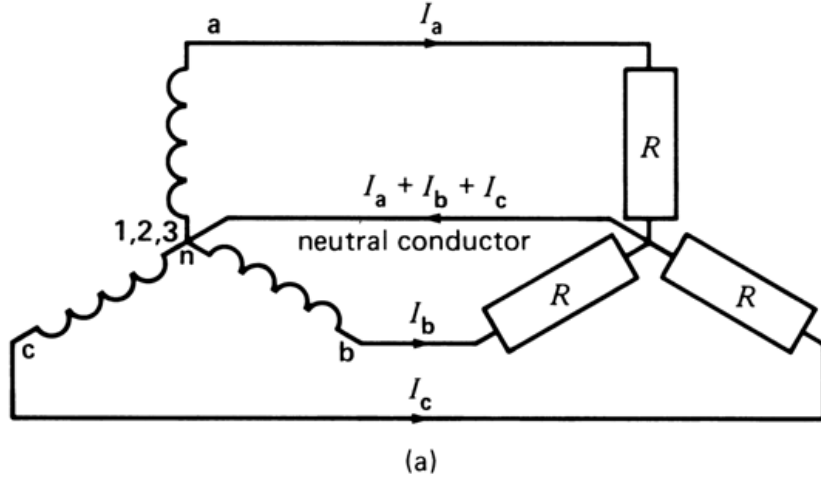


$$I_n = I_a + I_b + I_c$$
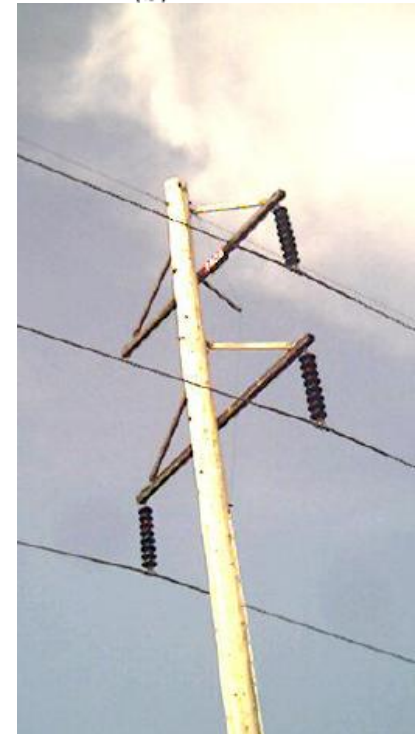
$$I_n = \frac{V}{Z}(1 \angle 0^\circ + 1 \angle -120^\circ + 1 \angle 120^\circ) = 0$$



Y- AND Δ-CONNECTED LOADS

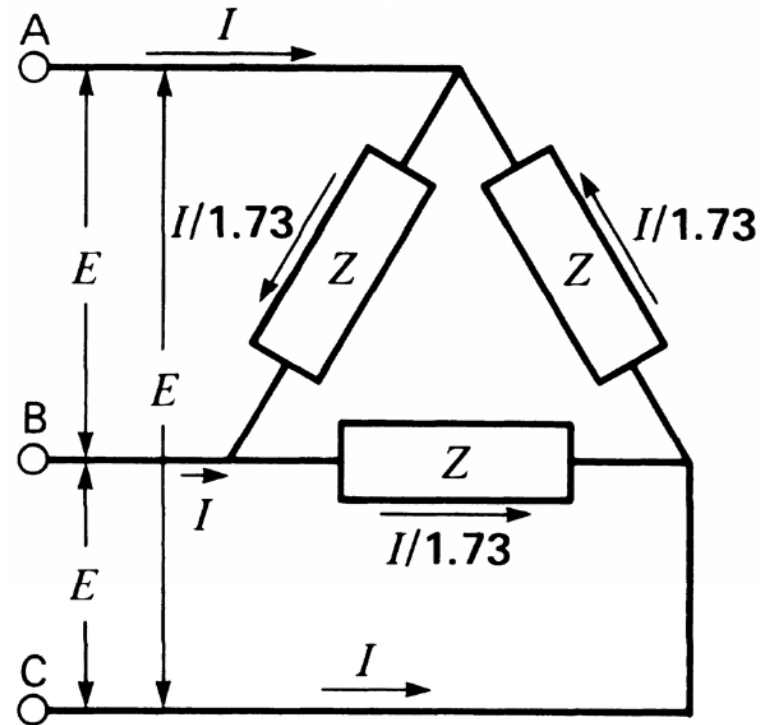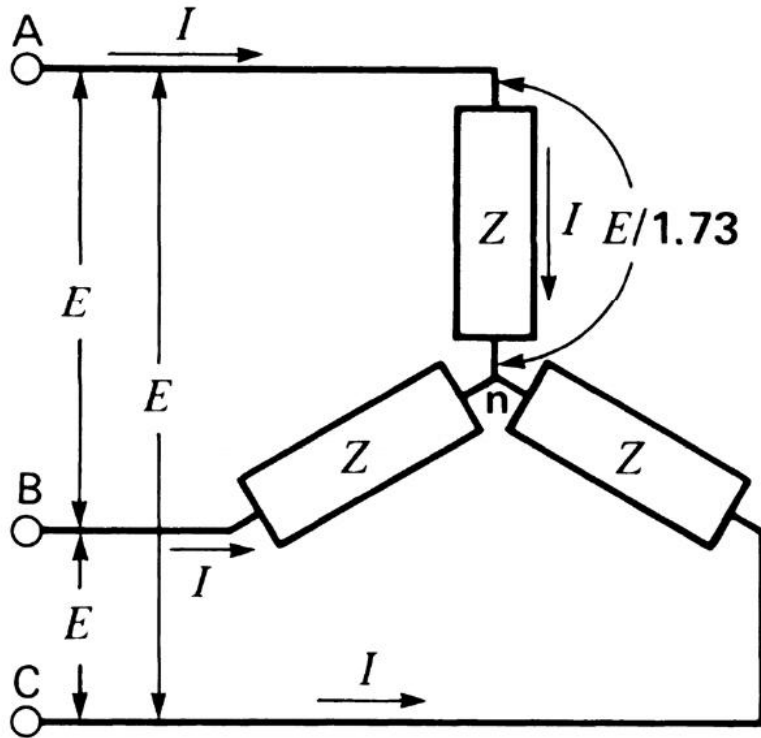

POWER IN BALANCED 3-PHASE CIRCUITS

The real power, reactive power, apparent power, complex power and power factor are the same in each phase.

$$P = 3V_p I \cos(\theta) = \sqrt{3}V_L I \cos(\theta)$$

$$Q = 3V_p I \sin(\theta) = \sqrt{3}V_L I \sin(\theta)$$


$$S = 3V_p I = \sqrt{3}V_L I$$

PER-PHASE ANALYSIS IN BALANCED 3-PHASE CIRCUITS


- Per phase analysis allows analysis of balanced 3 ϕ systems with the same effort as for a single phase system
- **To do per phase analysis**
 1. Convert all 3 ϕ load/sources to equivalent Y's
 2. Solve phase “a” independent of the other phases
 3. Total system power $S = 3 V_a I_a^*$
 4. If desired, phase “b” and “c” values can be determined by inspection (i.e., $\pm 120^\circ$ degree phase shifts)
 5. If necessary, go back to original circuit to determine line-line values or internal 3 ϕ values.

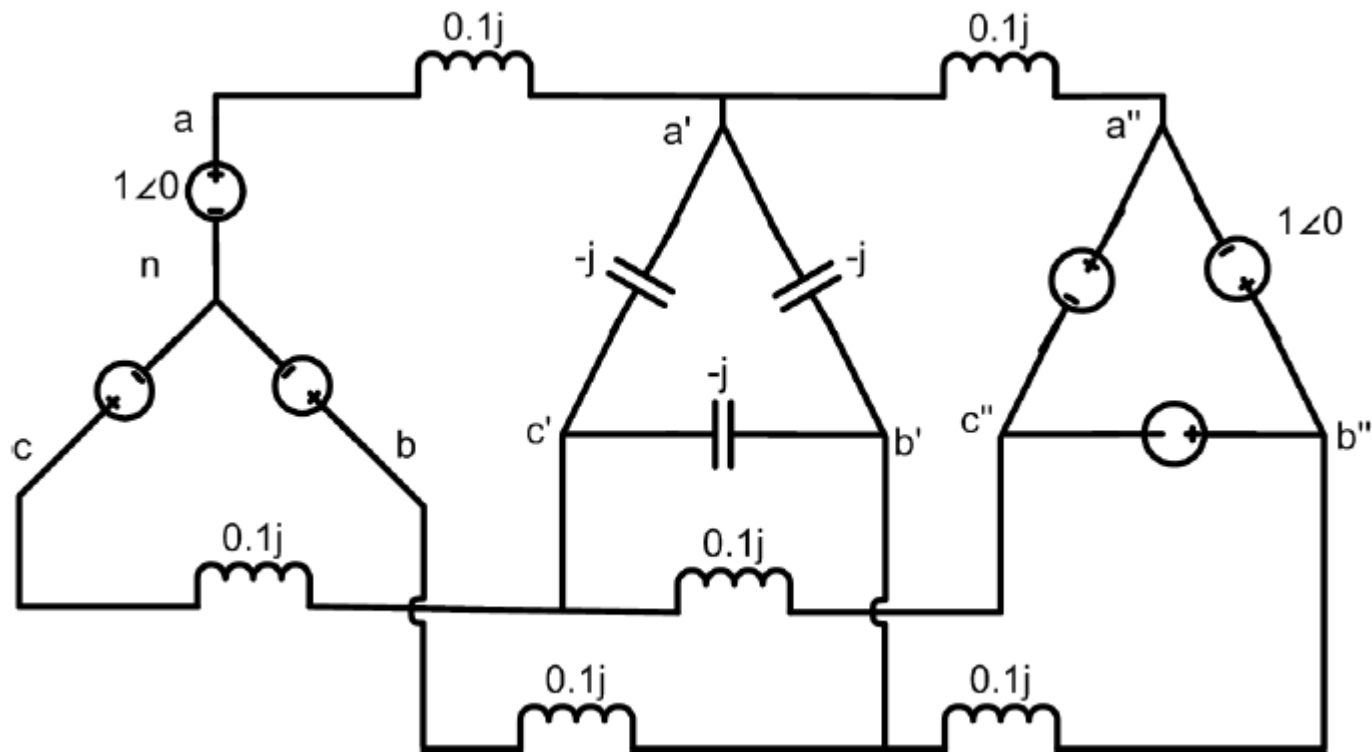EXAMPLE OF PER-PHASE ANALYSIS

Find the complex power supplied by each of the two sources.



SOLUTION

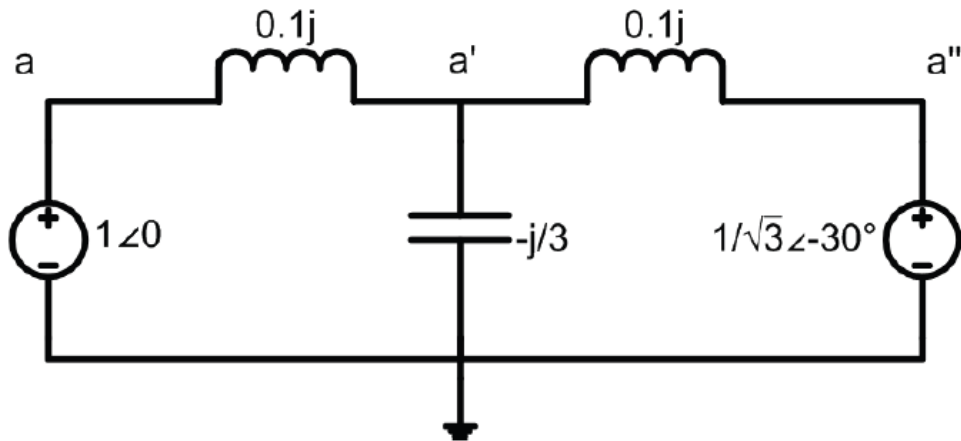

To solve the circuit, write the KCL equation at a'

$$(V'_a - 1\angle 0)(-10j) + V'_a(3j) + (V'_a - \frac{1}{\sqrt{3}}\angle -30^\circ)(-10j) = 0$$

$$(10j + \frac{10}{\sqrt{3}}\angle 60^\circ) = V'_a(10j - 3j + 10j)$$



$$V'_a = 0.9\angle -10.9^\circ \text{ volts} \quad V'_b = 0.9\angle -130.9^\circ \text{ volts}$$

$$V'_c = 0.9\angle 109.1^\circ \text{ volts} \quad V'_{ab} = 1.56\angle 19.1^\circ \text{ volts}$$

$$S_{Y_{gen}} = 3V_a I_a^* = V_a \left(\frac{V_a - V'_a}{j0.1} \right)^* = 5.1 + j3.5 \text{ VA}$$

$$S_{\Delta_{gen}} = 3V'_a \left(\frac{V''_a - V'_a}{j0.1} \right)^* = -5.1 - j4.7 \text{ VA}$$

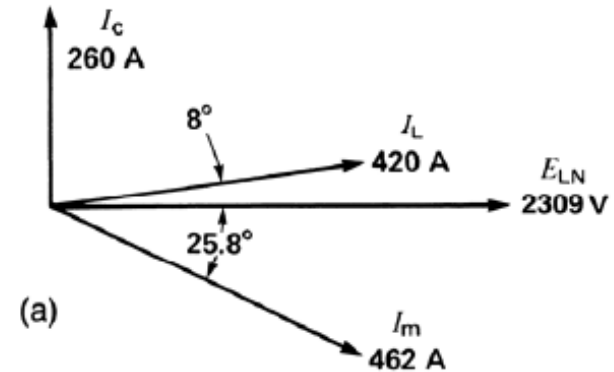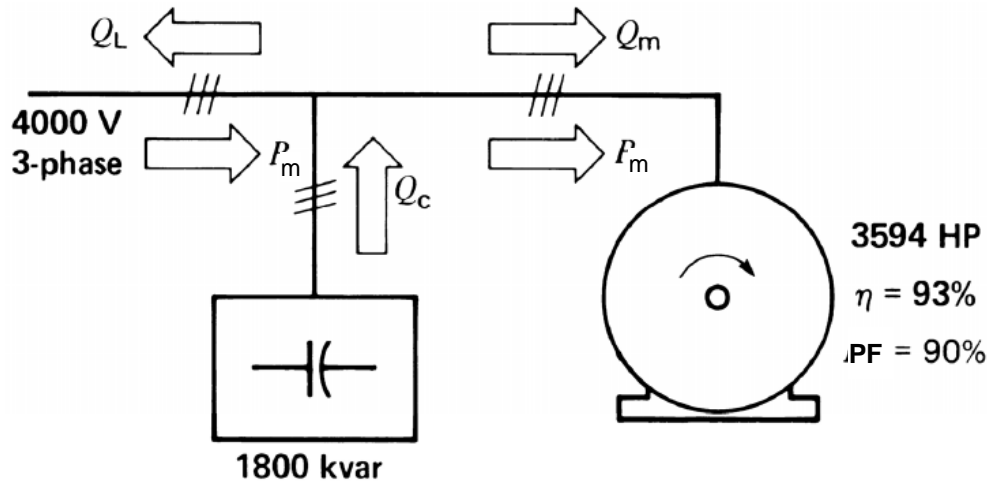EXAMPLE: POWER FACTOR CORRECTION IN THREE-PHASE CIRCUIT.




$$P_m = \sqrt{3} \times 4000 \times 0.462 \times \cos(25.8^\circ) = 2.88 \text{ MW}$$

$$Q_m = \sqrt{3} \times 4000 \times 0.462 \times \sin(25.8^\circ) = 1.39 \text{ MVAR}$$

$$Q_c = 1.8 \text{ MVAR}$$

$$Q_L = Q_m - Q_c = -0.41 \text{ MVAR}$$

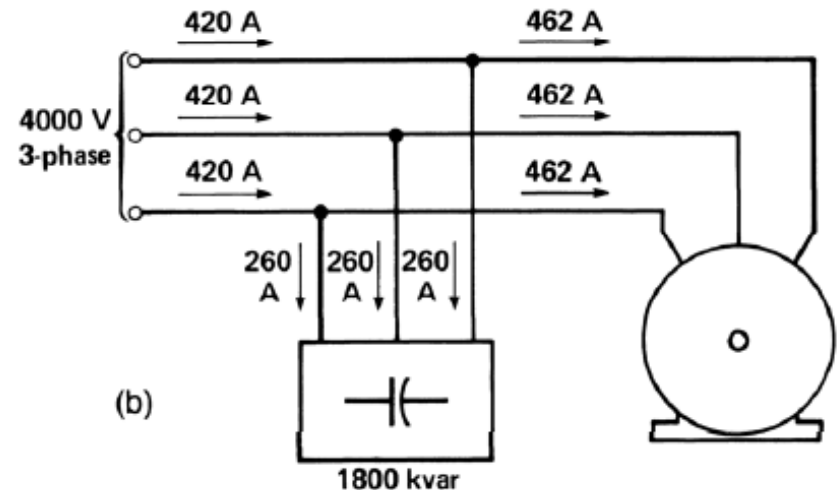

THE PER-UNIT SYSTEM

The voltages, currents, powers, impedances, and other electrical quantities are measured as fractions of some base level instead of conventional units.

$$\text{Quantity per unit} = \frac{\text{actual value}}{\text{base value of quantity}}$$

Usually, two base quantities are selected to define a given per-unit system. Often, such quantities are voltage and apparent power. In a single-phase circuit, once the base values of S and V are selected, all other base values can be computed from

$$P_{base}, Q_{base}, \text{ or } S_{base} = V_{base} I_{base}$$

$$Z_{base} = \frac{V_{base}}{I_{base}} = \frac{(V_{base})^2}{S_{base}}$$

$$Y_{base} = \frac{I_{base}}{V_{base}}$$

PER-UNIT SYSTEM

In a 3-phase circuit, given the base apparent power (3—phase) and base voltage (line-to-line), the base current and base impedance are given by

$$I_{base} = \frac{S_{3\phi,base}}{\sqrt{3}V_{LL,base}}$$


$$Z_{base} = \frac{V_{LL,base}}{\sqrt{3}I_{base}} = \frac{(V_{LL,base})^2}{S_{3\phi,base}}$$

PER-UNIT SYSTEM

The per-unit impedance may be transformed from one base to another as


$$\text{Per-unit } Z_{new} = \text{per-unit } Z_{old} \left(\frac{V_{old}}{V_{new}} \right)^2 \left(\frac{S_{new}}{S_{old}} \right)$$

ONE-LINE DIAGRAM (SIMPLE POWER SYSTEM)

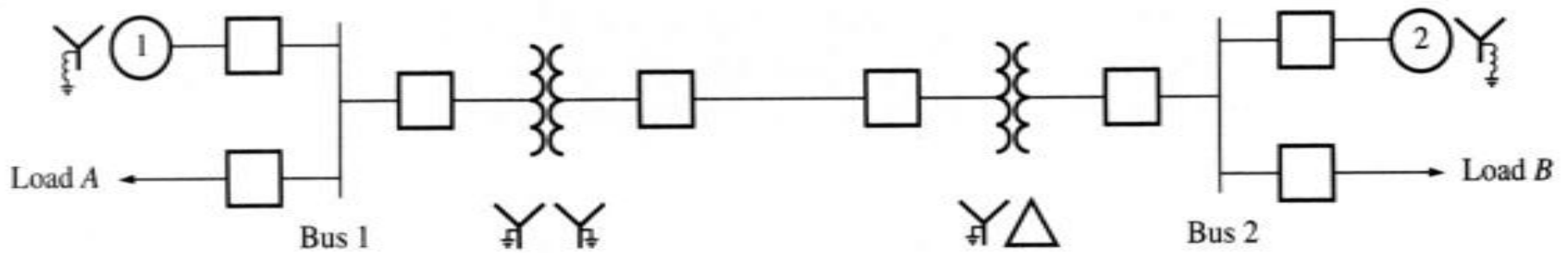

Machine ratings, impedances, consumed and/or supplied powers are usually included in the diagrams


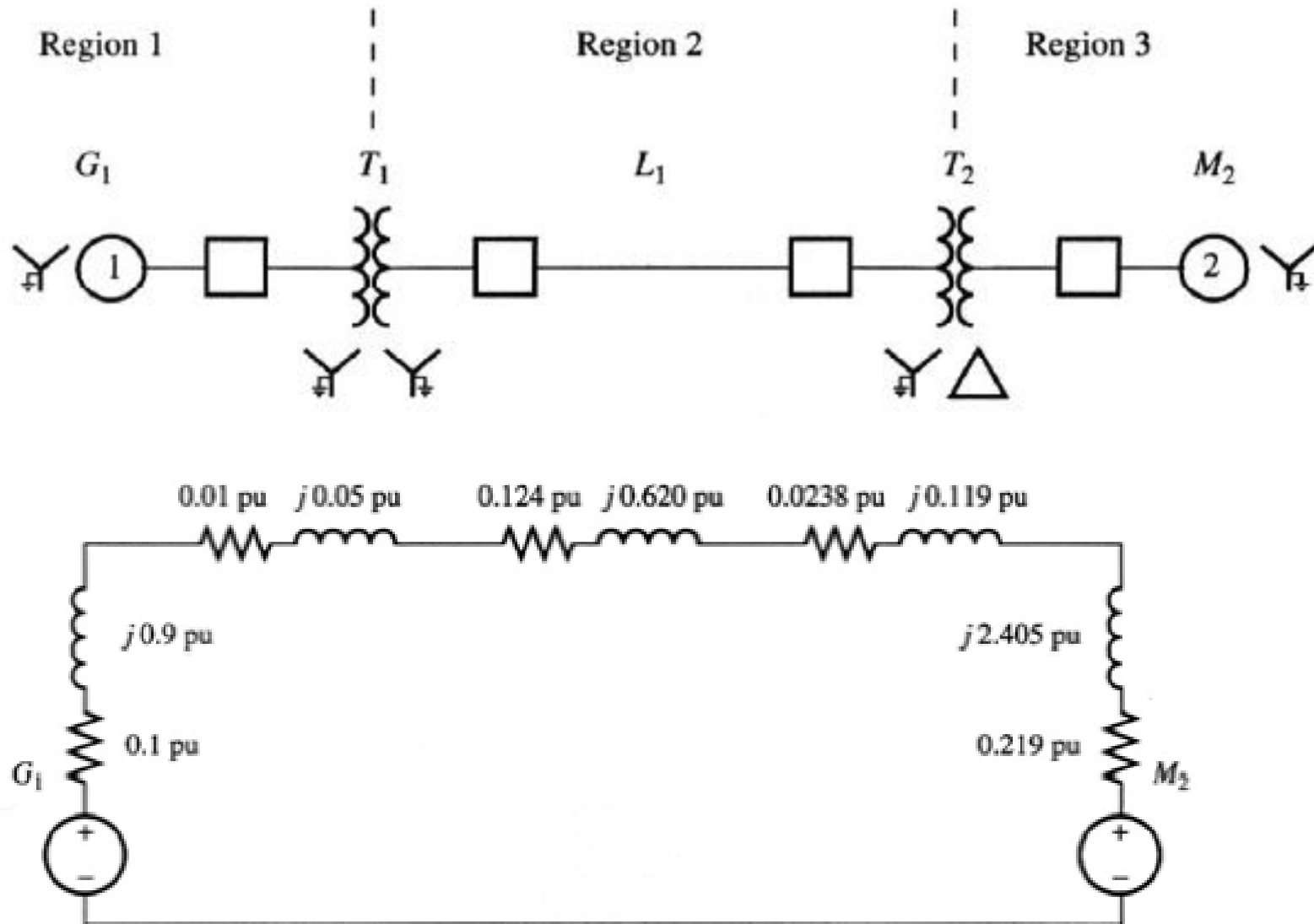
EXAMPLE OF CONVERSION OF ONE-LINE DIAGRAM TO IMPEDANCE DIAGRAM



NODE EQUATIONS

The most common technique used to solve circuit problems is nodal analysis. To simplify the equations,

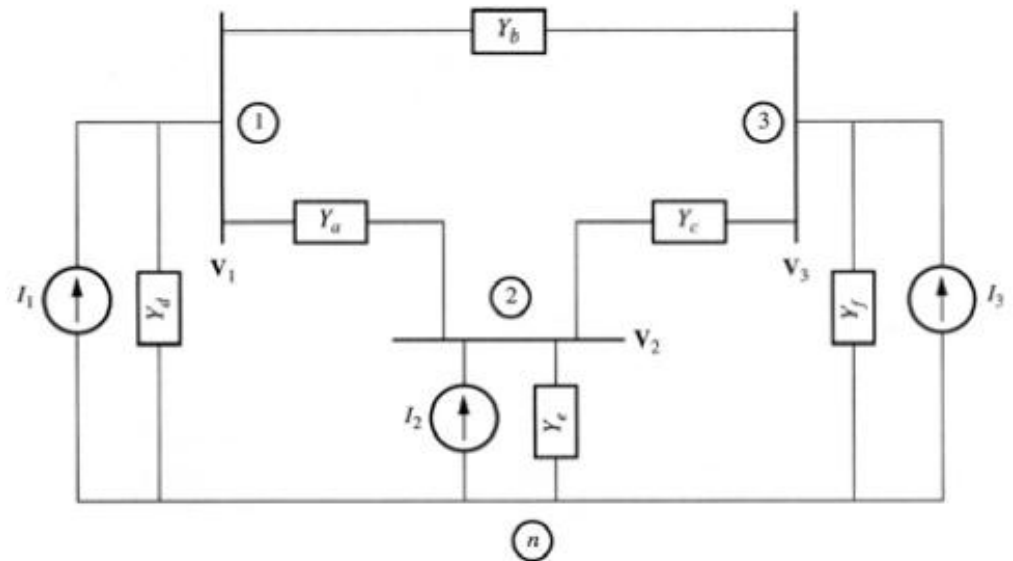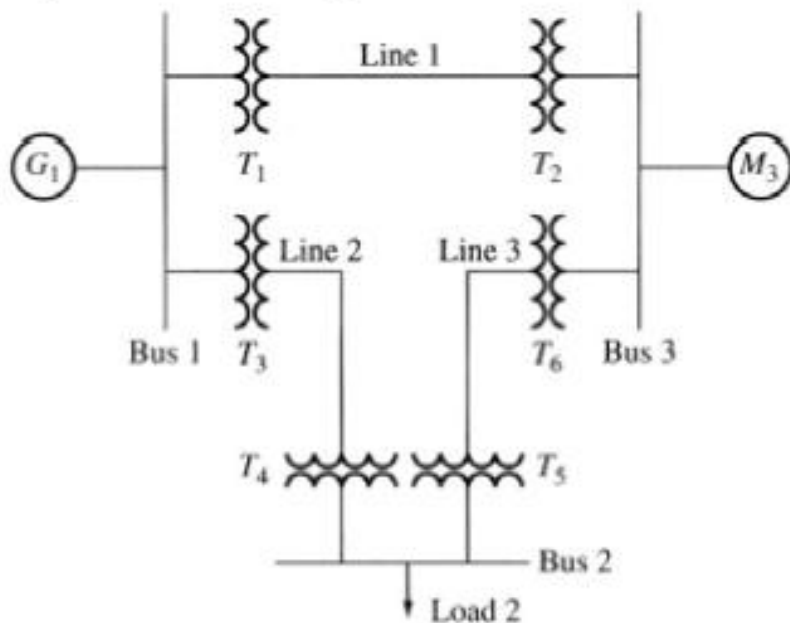- Replace the generators by their Norton equivalent circuits
- Replace the impedances by their equivalent admittances
- Represent the loads by the current they draw (for now)



NODE EQUATIONS

KCL is used to establish and solve a system of simultaneous equations with the unknown node voltages:

$$(V_1 - V_2)Y_a + (V_1 - V_3)Y_b + V_1Y_d = I_1$$

$$(V_2 - V_1)Y_a + (V_2 - V_3)Y_c + V_2Y_e = I_2$$

$$(V_3 - V_1)Y_b + (V_3 - V_2)Y_c + V_3Y_f = I_3$$

NODE EQUATIONS – THE Y_{BUS} MATRIX

In matrix from,

$$\begin{bmatrix} Y_a + Y_b + Y_d & -Y_a & -Y_b \\ -Y_a & Y_a + Y_c + Y_e & -Y_c \\ -Y_b & -Y_c & Y_b + Y_c + Y_f \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix}$$

Which is an equation of the form:

$$Y_{bus} V = I$$

where Y_{bus} is the bus admittance matrix of a system, which has the form:

$$Y_{bus} = \begin{bmatrix} Y_{11} & Y_{12} & Y_{13} \\ Y_{21} & Y_{22} & Y_{23} \\ Y_{31} & Y_{32} & Y_{33} \end{bmatrix}$$

Y_{bus} has a regular form that is easy to calculate:

- 1) The diagonal elements Y_{ii} equal the sum of all admittances connected to node i .
- 2) Other elements Y_{ij} equal to the negative admittances connected to nodes i and j .

The diagonal elements of Y_{bus} are called the self-admittance or driving-point admittances of the nodes; the off-diagonal elements are called the mutual admittances or transfer admittances of the nodes.

Y_{BUS} AND Z_{BUS} MATRICES

Inverting the bus admittance matrix Y_{bus} yields the bus impedance mat

$$Z_{bus} = Y_{bus}^{-1}$$




Then,

$$V = Y_{bus}^{-1} I$$

or

$$V = Z_{bus} I$$

EXAMPLE

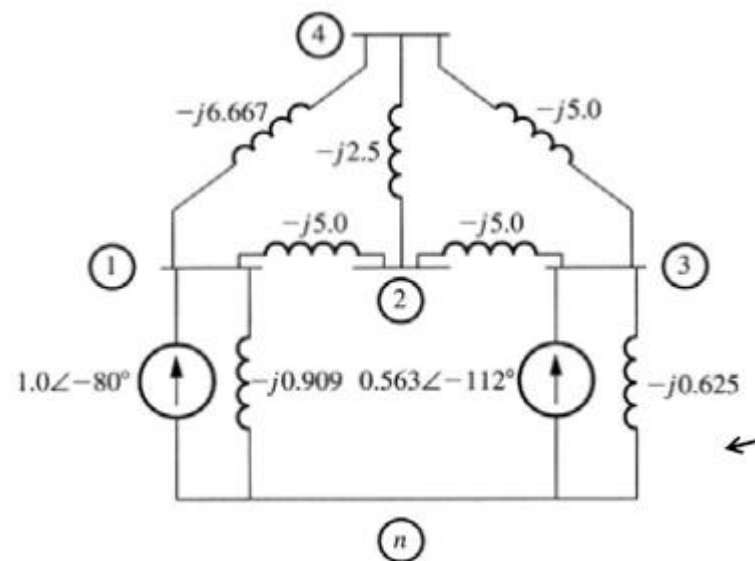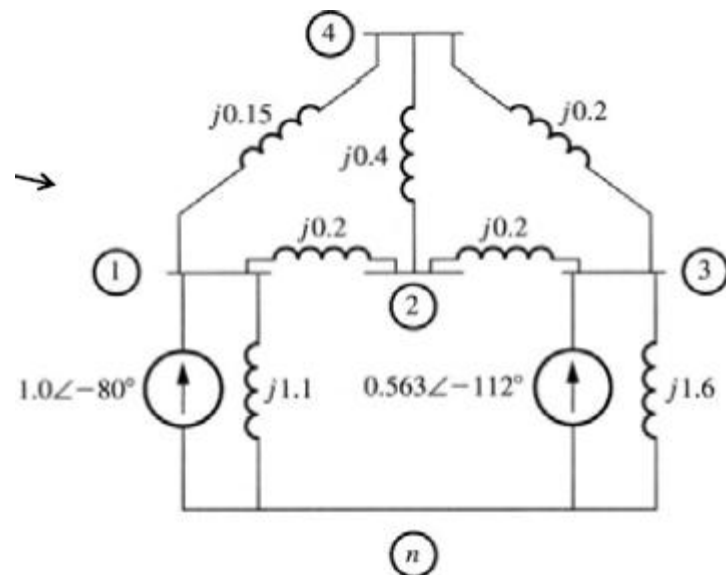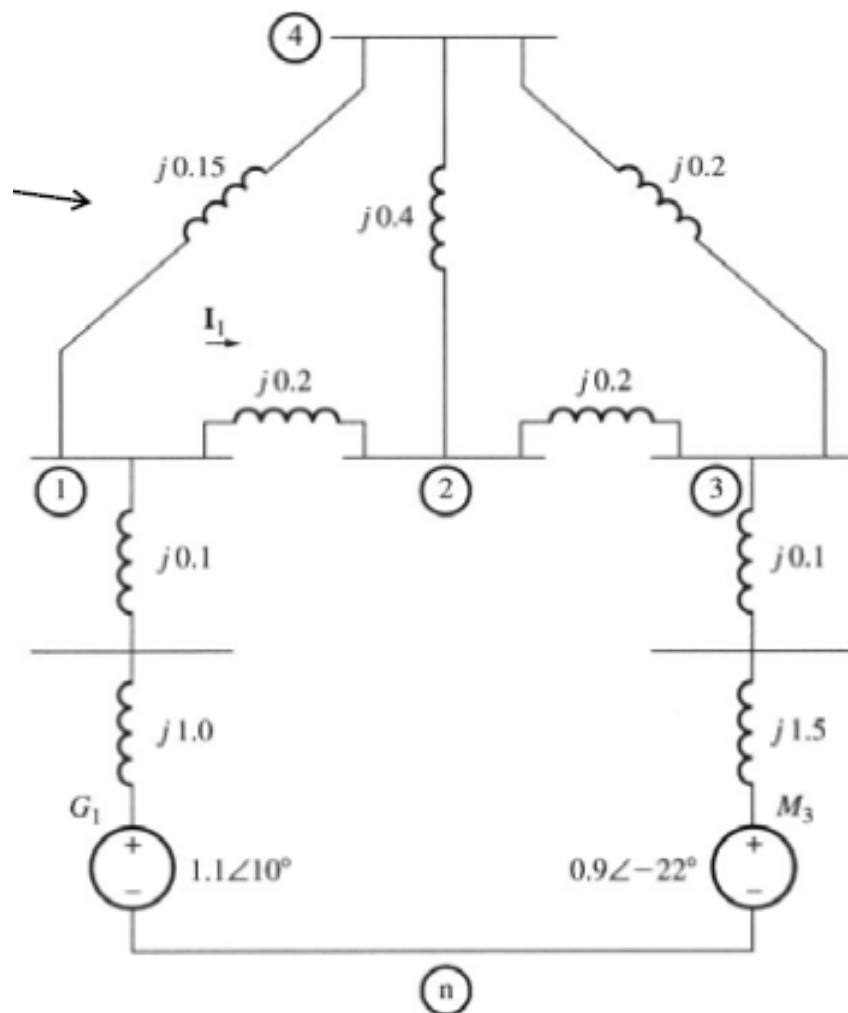

EXAMPLE (CONT.)

The resulting admittance matrix is:

$$Y_{bus} = \begin{bmatrix} -j12.576 & j5.0 & 0 & j6.667 \\ j5.0 & -j12.5 & j5.0 & j2.5 \\ 0 & j5.0 & -10.625 & j5.0 \\ j6.667 & j2.5 & j5.0 & -j14.167 \end{bmatrix}$$

The current vector for this circuit is:

$$I = \begin{bmatrix} 1.0 \angle -80^\circ \\ 0 \\ 0.563 \angle -112^\circ \\ 0 \end{bmatrix}$$

The solution to the system of equations will be

$$V = Y_{bus}^{-1} I = \begin{bmatrix} 0.989 \angle -0.60^\circ \\ 0.981 \angle -1.58^\circ \\ 0.974 \angle -2.62^\circ \\ 0.982 \angle -1.48^\circ \end{bmatrix} V$$

PROBLEMS FROM CHAP. 1:

7, 15, 19, 21, 26

END!

