

## Overview

- This chapter applies the circuit analysis introduced in the DC circuit analysis for AC circuit analysis.
- Nodal and mesh analysis are discussed.
- Superposition and source transformation for AC circuits are also covered.
- Applications in op-amps and oscillators are reviewed.

---

Henry Selvaraj

## Steps to Analyze an AC Circuit

- There are three steps to analyzing an AC circuit.
- They make use of the fact that frequency domain analysis is simpler because it can make use of the nodal and mesh techniques developed for DC

- 1.Transform the circuit to the phasor or frequency domain
- 2.Solve the problem using circuit techniques
- 3.Transform back to time domain.

---

Henry Selvaraj

## Nodal Analysis

- It is possible to use KCL to analyze a circuit in frequency domain.
- The first step is to convert a time domain circuit to frequency domain by calculating the impedances of the circuit elements at the operating frequency.
- Note that AC sources appear as DC sources with their values expressed as their amplitude.

---

Henry Selvaraj

## Nodal Analysis II


- Impedances will be expressed as complex numbers.
- Sources will have amplitude and phase noted.
- At this point, KCL analysis can proceed as normal.
- It is important to bear in mind that complex values will be calculated, but all other treatments are the same.

---

Henry Selvaraj


## Nodal Analysis Example

Find  $i_x$ .

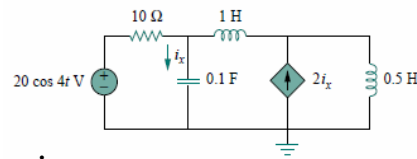

Transform to frequency domain.
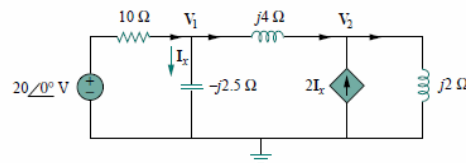
$$\begin{aligned} 20 \cos 4t &\Rightarrow 20 \angle 0^\circ, & \omega &= 4 \text{ rad/s} \\ 1 \text{ H} &\Rightarrow j\omega L = j4 \\ 0.5 \text{ H} &\Rightarrow j\omega L = j2 \\ 0.1 \text{ F} &\Rightarrow \frac{1}{j\omega C} = -j2.5 \end{aligned}$$



Henry Selvaraj

Applying KCL at node 1,

$$\frac{20 - V_1}{10} = \frac{V_1}{-j2.5} + \frac{V_1 - V_2}{j4}$$

or

$$(1 + j1.5)V_1 + j2.5V_2 = 20$$

At node 2,

$$2I_x + \frac{V_1 - V_2}{j4} = \frac{V_2}{j2}$$

But  $I_x = V_1 / -j2.5$ . Substituting this gives

$$\frac{2V_1}{-j2.5} + \frac{V_1 - V_2}{j4} = \frac{V_2}{j2}$$

By simplifying, we get

$$11V_1 + 15V_2 = 0$$

$$\begin{bmatrix} 1 + j1.5 & j2.5 \\ 11 & 15 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 20 \\ 0 \end{bmatrix}$$

We obtain the determinants as

$$\Delta = \begin{vmatrix} 1 + j1.5 & j2.5 \\ 11 & 15 \end{vmatrix} = 15 - j5$$

$$\Delta_1 = \begin{vmatrix} 20 & j2.5 \\ 0 & 15 \end{vmatrix} = 300, \quad \Delta_2 = \begin{vmatrix} 1 + j1.5 & 20 \\ 11 & 0 \end{vmatrix} = -220$$

$$V_1 = \frac{\Delta_1}{\Delta} = \frac{300}{15 - j5} = 18.97 \angle 18.43^\circ \text{ V}$$

$$V_2 = \frac{\Delta_2}{\Delta} = \frac{-220}{15 - j5} = 13.91 \angle 198.3^\circ \text{ V}$$

The current  $I_x$  is given by

$$I_x = \frac{V_1}{-j2.5} = \frac{18.97 \angle 18.43^\circ}{2.5 \angle -90^\circ} = 7.59 \angle 108.4^\circ \text{ A}$$


Transforming this to the time domain,

$$i_x = 7.59 \cos(4t + 108.4^\circ) \text{ A}$$

Henry Selvaraj
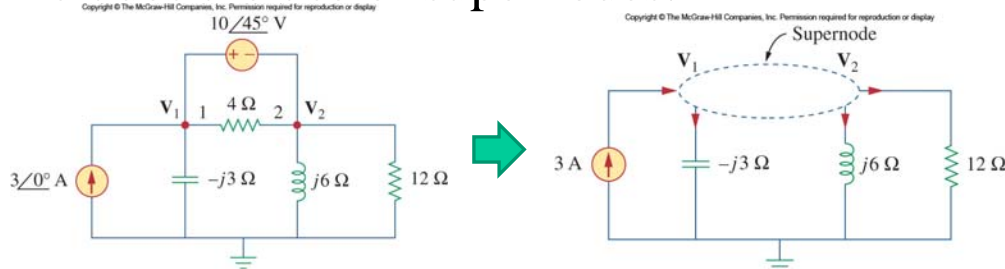
## Nodal Analysis III


- The final voltages and current calculated are the real component of the derived values.
- The equivalency of the frequency domain treatment compared to the DC circuit analysis includes the use of supernodes.



Henry Selvaraj
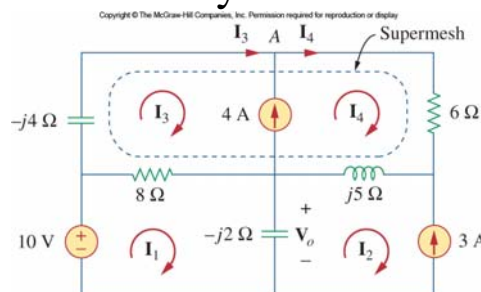
## Mesh Analysis


- Just as in KCL, the KVL analysis also applies to phasor and frequency domain circuits.
- The same rules apply: Convert to frequency domain first, then apply KVL as usual.
- In KVL, supermesh analysis is also valid.



Henry Selvaraj
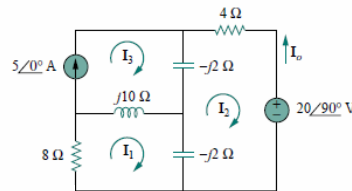
## Example Mesh Analysis:

- Determine current  $I_o$  in the circuit using mesh analysis.



Applying KVL to mesh 1, we obtain:

$$(8 + j10 - j2)I_1 - (-j2)I_2 - j10I_3 = 0$$

For mesh 2,

$$(4 - j2 - j2)I_2 - (-j2)I_1 - (-j2)I_3 + 20\angle 90^\circ = 0$$

For mesh 3,  $I_3 = 5$ .

$$(8 + j8)I_1 + j2I_2 = j50$$

$$j2I_1 + (4 - j4)I_2 = -j20 - j10$$

$$\begin{bmatrix} 8 + j8 & j2 \\ j2 & 4 - j4 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} j50 \\ -j30 \end{bmatrix}$$

from which we obtain the determinants

$$\Delta = \begin{vmatrix} 8 + j8 & j2 \\ j2 & 4 - j4 \end{vmatrix} = 32(1 + j)(1 - j) + 4 = 68$$

$$\Delta_2 = \begin{vmatrix} 8 + j8 & j50 \\ j2 & -j30 \end{vmatrix} = 340 - j240 = 416.17\angle -35.22^\circ$$

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{416.17\angle -35.22^\circ}{68} = 6.12\angle -35.22^\circ \text{ A}$$

The desired current is

$$I_o = -I_2 = 6.12\angle 144.78^\circ \text{ A}$$

Henry Selvaraj

## Superposition

- Since AC circuits are linear, it is also possible to apply the principle of superposition.
- This becomes particularly important if the circuit has sources operating at different frequencies.
- The complication is that each source must have its own frequency domain equivalent circuit.


Henry Selvaraj

## Superposition II


- The reason for this is that each element has a different impedance at different frequencies.
- Also, the resulting voltages and current must be converted back to time domain before being added.
- This is because there is an exponential factor  $e^{j\omega t}$  implicit in sinusoidal analysis.

Henry Selvaraj

## Superposition Example

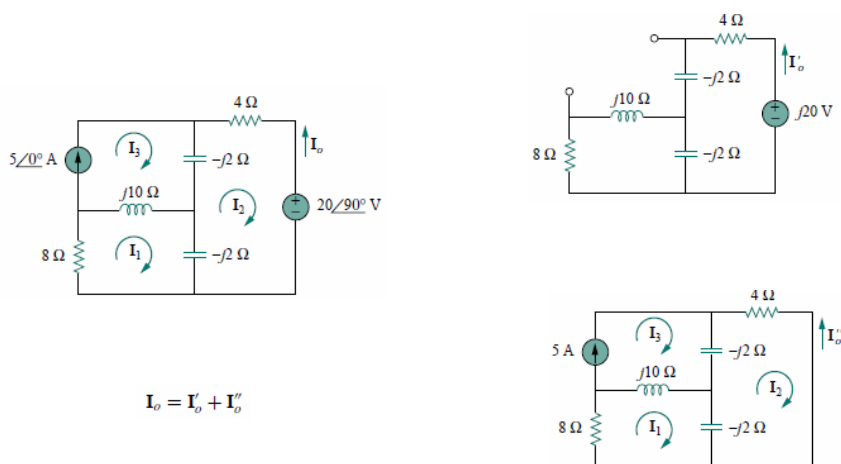

Henry Selvaraj

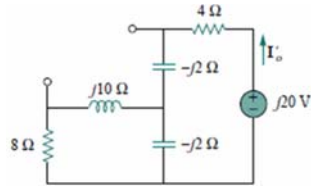


$$Z = \frac{-j2(8 + j10)}{-2j + 8 + j10} = 0.25 - j2.25$$

and current  $I_o'$  is

$$I_o' = \frac{j20}{4 - j2 + Z} = \frac{j20}{4.25 - j4.25}$$

or

$$I_o' = -2.353 + j2.353$$

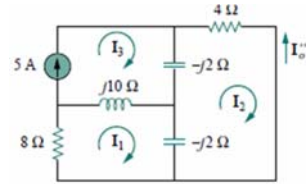

For mesh 1,  $(8 + j8)I_1 - j10I_3 + j2I_2 = 0$

For mesh 2,

$$(4 - j4)I_2 + j2I_1 + j2I_3 = 0$$

For mesh 3,

$$I_3 = 5$$

$$(4 - j4)I_2 + j2I_1 + j10 = 0$$

Expressing  $I_1$  in terms of  $I_2$  gives

$$I_1 = (2 + j2)I_2 - 5$$

$$(8 + j8)[(2 + j2)I_2 - 5] - j50 + j2I_2 = 0$$

or

$$I_2 = \frac{90 - j40}{34} = 2.647 - j1.176$$

Current  $I_o''$  is obtained as

$$I_o'' = -I_2 = -2.647 + j1.176$$

$$I_o = I_o' + I_o'' = -5 + j3.529 = 6.12 \angle 144.78^\circ \text{ A}$$

Henry Selvaraj